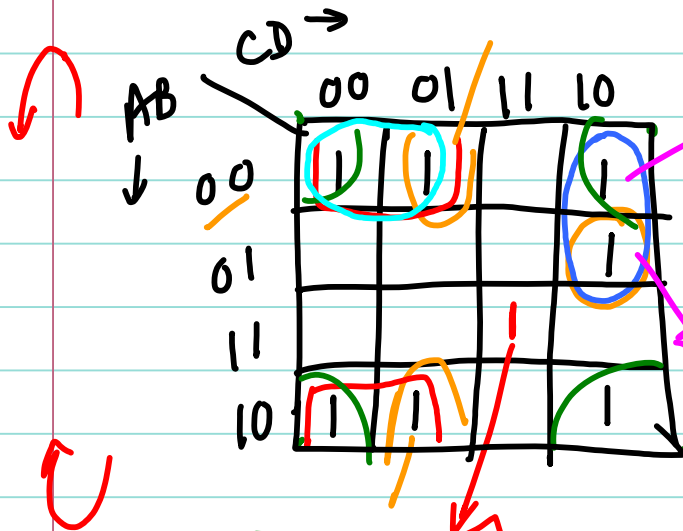


Lec-32

$$F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D}$$



$$\bar{A}\bar{B}C\bar{D} \checkmark$$


$$\bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}C\bar{D}$$

$$\bar{A}BC\bar{D} \checkmark$$

$$\bar{B}C + \bar{B}\bar{D} + \bar{A}BC\bar{D}$$


$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}BC\bar{D}$$
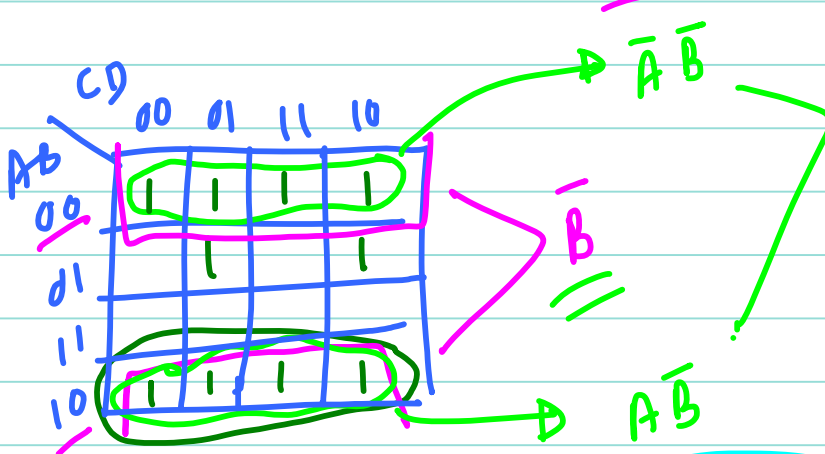
$$= \bar{A}\bar{C}\bar{D}(\bar{B} + B) = \bar{A}\bar{C}\bar{D} \cdot (1)$$



$$\bar{A}\bar{B} + A\bar{B}$$

$$= \bar{B}(A + \bar{A}) = \bar{B}$$

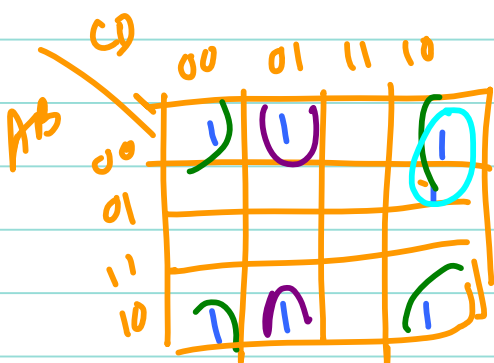

$$\bar{B}\bar{D} + \bar{B}\bar{C}D + \bar{A}\bar{C}\bar{D}$$

$$\begin{matrix} 2 \\ 4 \\ 8 \\ 16 \\ 32 \end{matrix} \quad (2^n)$$

		B	
		0	1
A	0	0	1
	1	1	0

$$F = \bar{A}B + A\bar{B}$$

$$F = A \oplus B$$

$$F = \bar{A}B$$


$$\bar{F} = \overline{\bar{A}B} = \bar{\bar{A}} + \bar{B} = A + \bar{B}$$

NOT implementation as Homel work




NAND and NOR gates:

AND
OR
NOT


Universal gates.

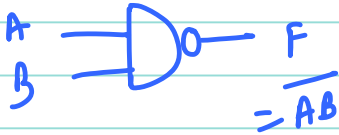

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

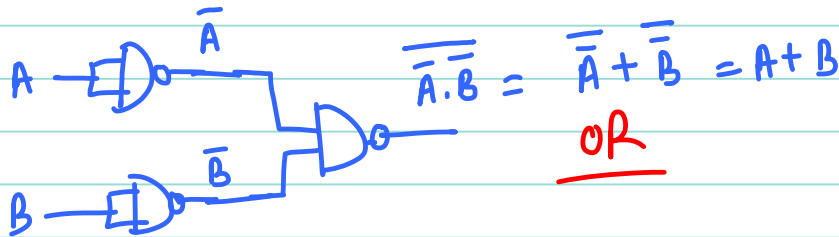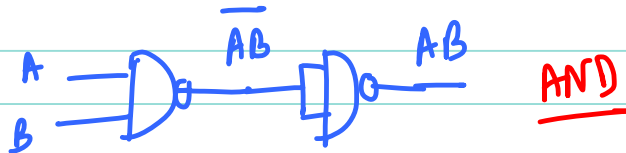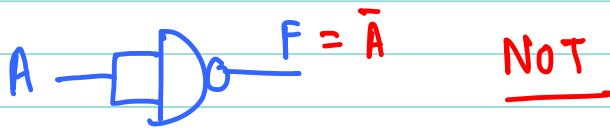


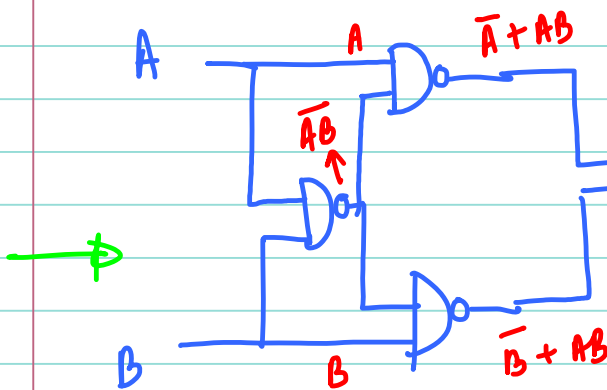
Ex-OR $A \oplus B$ using NAND gates.
($\overline{AB} + A\overline{B}$)



Ex-OR

$$\begin{aligned}
 & \overline{(\overline{A} + AB) \cdot (\overline{B} + AB)} \\
 &= \overline{\overline{A} + AB + \overline{B} + AB} \\
 &= \overline{\overline{A} \cdot \overline{AB} + \overline{B} \cdot \overline{AB}} \\
 &= \overline{A \cdot \overline{AB} + B(\overline{AB})} \\
 &= \overline{A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B})} \\
 &= \overline{A\overline{B} + \overline{A}B} \\
 &= \underline{\underline{A \oplus B}}
 \end{aligned}$$

$$F = ()$$

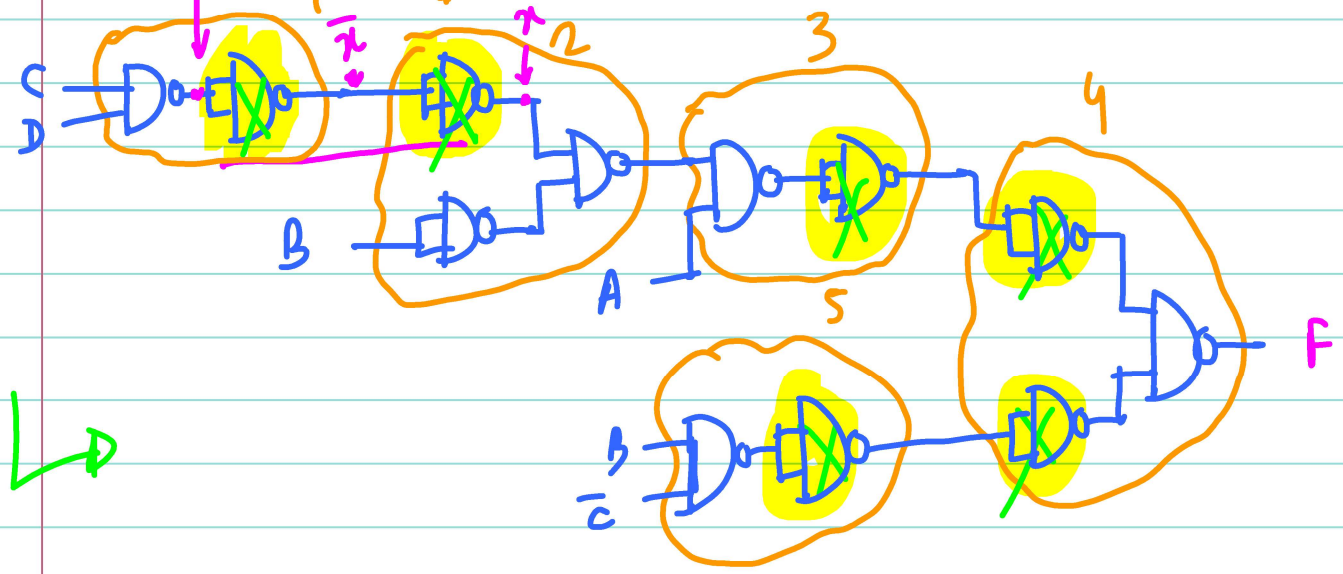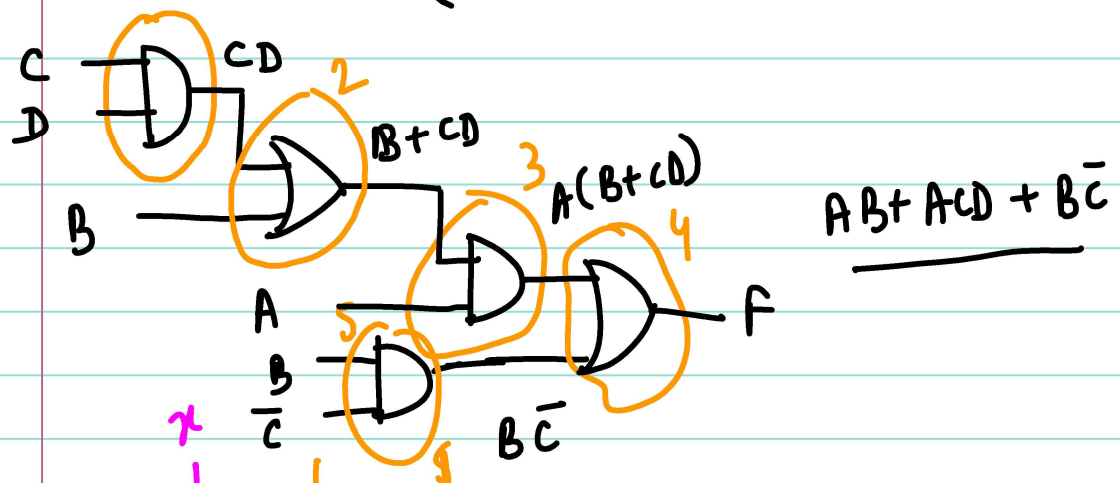

→


NAND Implementation:

$$\rightarrow F(x, y, z) = \sum (0, 6)$$

SOP Form


for
NAND
implementation.
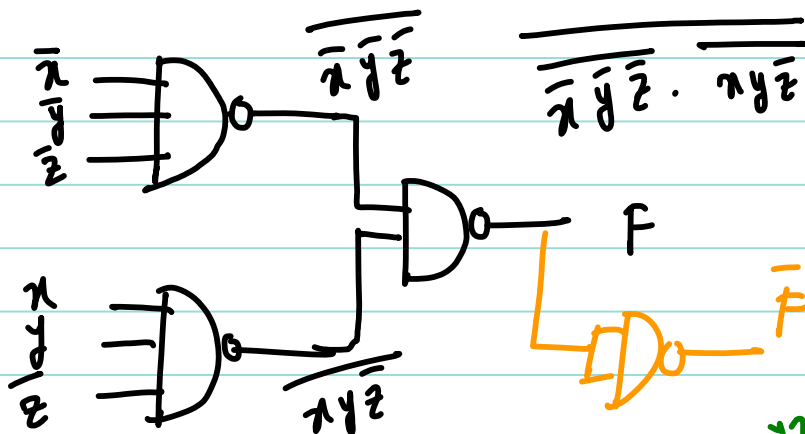
$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + xy\bar{z}$$





$$\overline{\bar{x}\bar{y}\bar{z} \cdot xy\bar{z}} = \bar{x}\bar{y}\bar{z} + xy\bar{z}$$

F(x, y, z)

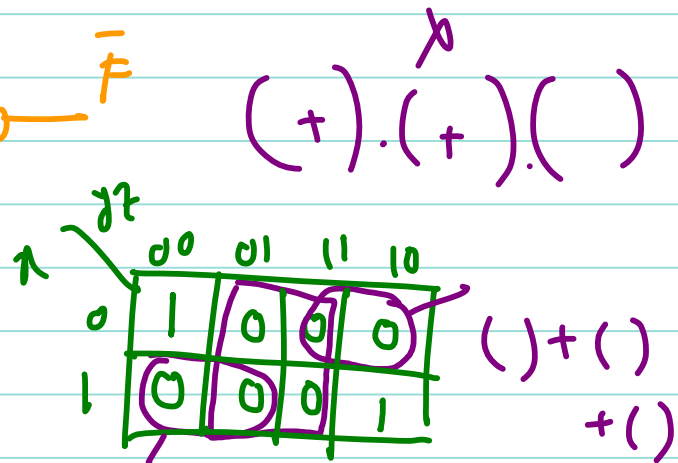
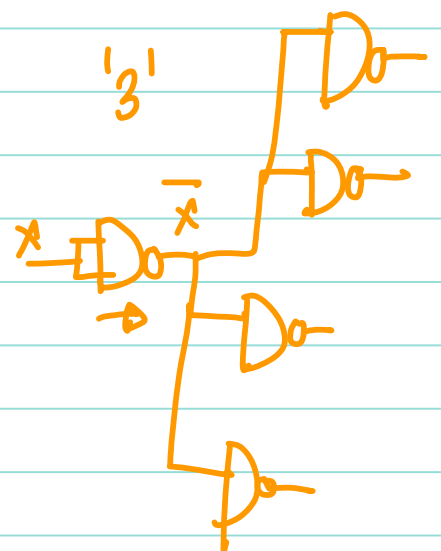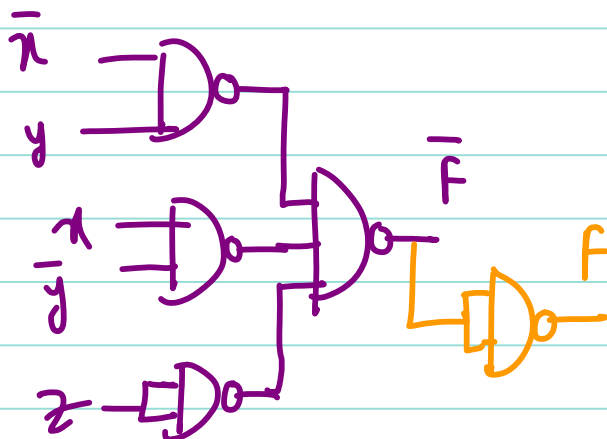
$$\bar{F} = z + \bar{x}y + x\bar{y} \quad \underline{\text{SOP}}$$



NOR implementation.

POS form


$$f = x \quad F(x, y, z) = \sum (0, 6)$$

$$\bar{F} = \bar{x}y + x\bar{y} + z$$

$$\bar{\bar{F}} = F = \overline{\bar{x}y + x\bar{y} + z}$$

$$F = (x + \bar{y}) \cdot (\bar{x} + y) \cdot \bar{z} \quad \checkmark$$

POS form

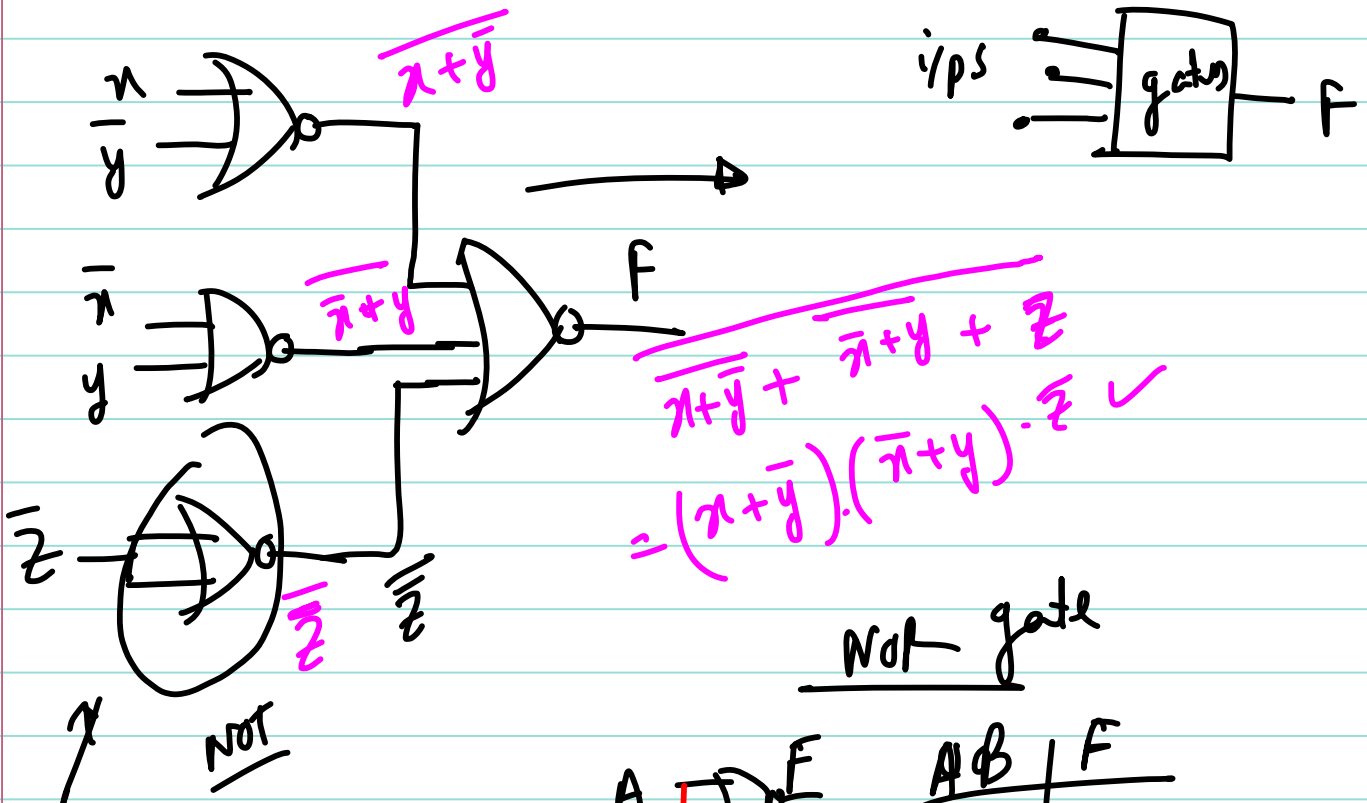


NOR gate


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

Combinational Logic

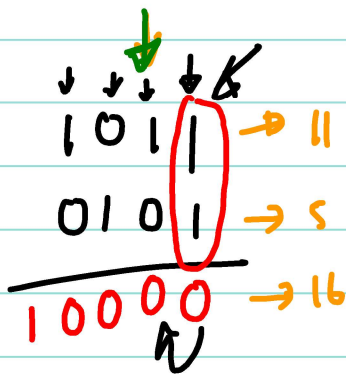Adder (single-bit) → Half-Adder
 → Full-Adder






Half-Adder:

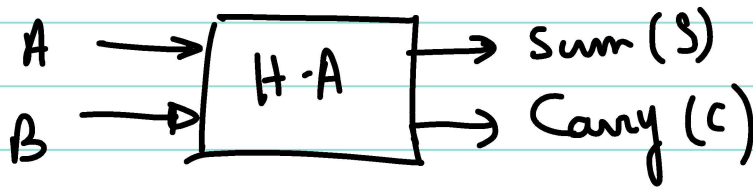

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
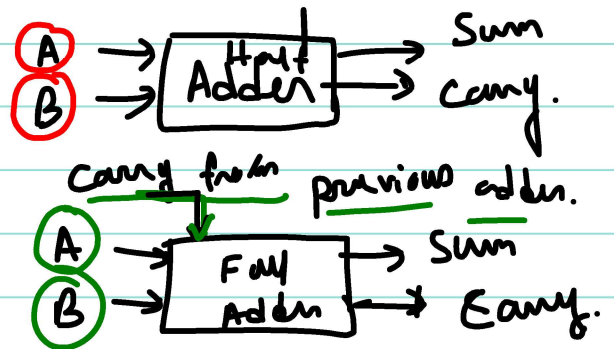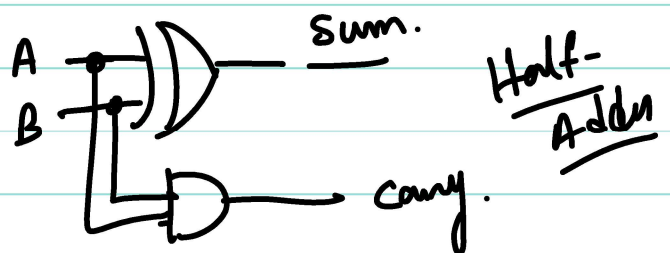
$$\downarrow \\
 S = \bar{A}B + A\bar{B} = A \oplus B \\
 C = AB$$



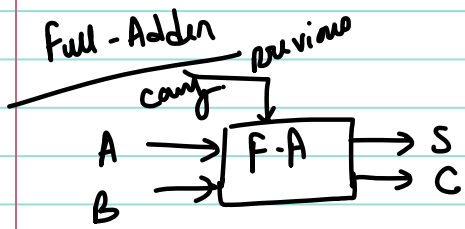


(S)

	BC	00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

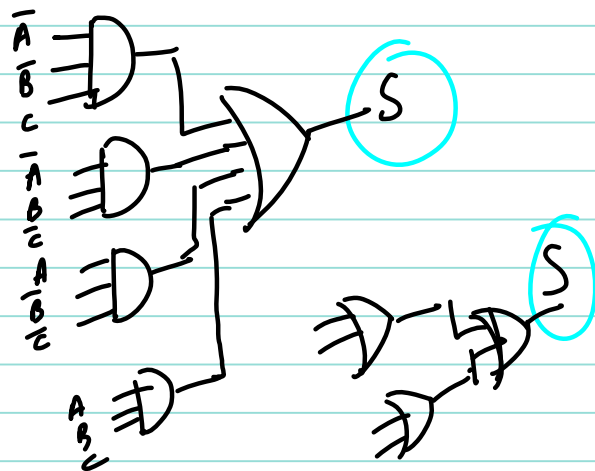
$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$




Carry

	BC	00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

Carry = $AC + AB + BC$

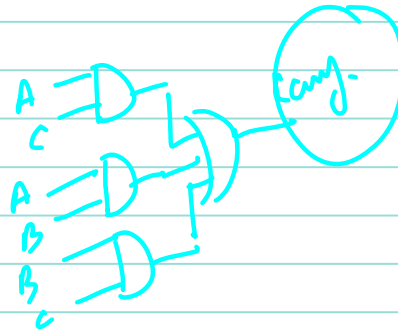

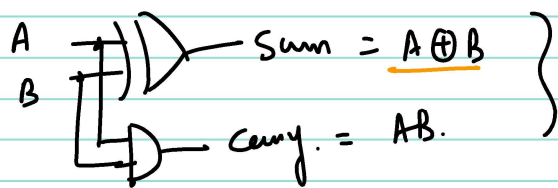Full-Adder using two half-adder circuit and an OR gate



Half-Adder
 $F_1 = A \odot B$
 $A \oplus B = F$

Full-Adder

$$Sum = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$Carry = AC + AB + BC$$

A	B	F	F ₁
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$Sum = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$= C(\bar{A}\bar{B} + AB) + \bar{C}(\bar{A}B + A\bar{B})$$

$$= C(A \oplus B) + \bar{C}(A \oplus B)$$

$$A \oplus B = x$$

$$= Cx + \bar{C}x$$

$$= C \oplus x = C \oplus A \oplus B = \underline{A \oplus B \oplus C}$$

Carry = AC + AB + BC



$$(A \oplus B)C + AB$$

$$= (\bar{A}B + A\bar{B})C + AB(C + \bar{C})$$

$$x + x + x = x$$

$$= \bar{A}BC + A\bar{B}C + ABC + AB\bar{C}$$

$$= \bar{A}BC + A\bar{B}C + ABC + AB\bar{C} + ABC + ABC + AB\bar{C}$$

$$= BC(\bar{A} + A) + AC(\bar{B} + B) + AB(\bar{C} + C)$$

$$= \underline{BC + AC + AB}$$