

1. For the n-channel MOSFET as shown in Fig. 1 has $K_n = 0.2 \text{ mA/V}^2$ and $V_{Th} = 1 \text{ V}$. Given that $V_{DD} = 10 \text{ V}$ and $R_D = 1 \text{ k}\Omega$. Find (a) the region operation, (b) V_{GS} (c) V_{DS} and (d) i_D .

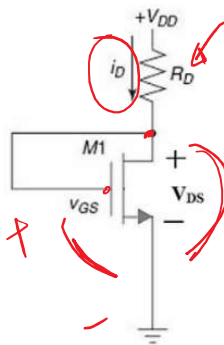


Fig. 1

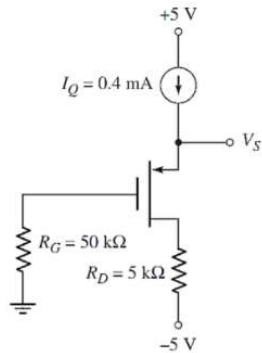


Fig. 2

① Here,

$$V_{DS} \approx V_{GS} > V_{GS} - V_{Th}$$

So, MOSFET is in saturation. — (a)

$$i_D = K_n (V_{GS} - V_{Th})^2 = 0.2 \times 10^{-3} (V_{GS} - 1)^2$$

$$i_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{V_{DD} - V_{GS}}{1 \text{ k}\Omega}$$

equating

$$0.2 \times 10^{-3} (V_{GS} - 1)^2 = \frac{10 - V_{GS}}{1 \text{ k}\Omega}$$

$$V_{GS} = 5.66, -8.66 \text{ V}$$

$V_{GS} < 0$, not possible, so, $V_{GS} = 5.66 \text{ V}$. — (b)

$$V_{DS} = 5.66 \text{ V}$$
 — (c)
$$i_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{10 - 5.66}{1 \text{ k}\Omega} = 4.34 \text{ mA}$$
 — (d)

2. For the circuit in Figure 2, the p-channel transistor has threshold voltage (V_{Th}) = -0.8 V and $K_p = 200 \mu\text{A/V}^2$. Determine V_S and V_{SD} .

②

$$V_G = 0$$

Let us assume, the MOSFET is in saturation

$$I_D = I_S = K_p (V_{GS} + V_{Th})^2$$


$$0.4 = 200 \times 10^{-6} \times (V_S - 0.8)^2$$

$$V_S = 2.214 \text{ V}$$

$$V_{SD} = V_S - V_D$$

$$V_D = -5 + I_D \cdot R_D = -5 + 0.4 \times 5 = -3 \text{ V}$$
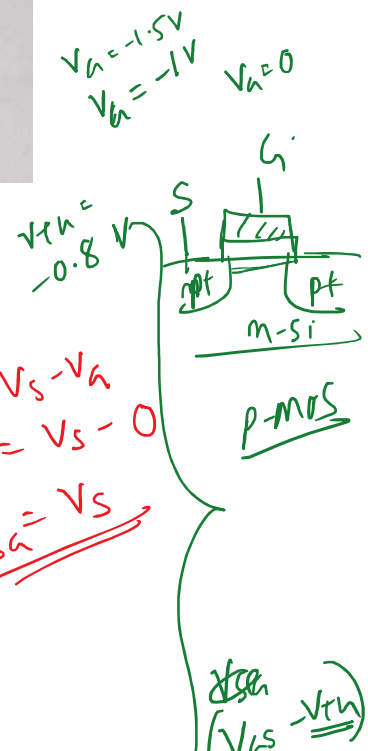
$$V_{SD} = V_S - V_D = 2.214 - (-3) = 5.214 \text{ V}$$



$$\begin{aligned}
 V_D &= -5 + I_D \cdot R_D \\
 &= -5 + 0.4 \times 5 \\
 V_D &= -3 \text{ V.} \\
 \therefore V_{SD} &= V_S - V_D = 2.214 - (-3) \\
 V_{SD} &= 5.214 \text{ V.} \\
 V_{SD}(\text{sat}) &= V_{SA} + V_{TH} \\
 &= 2.214 + 0.8 \\
 &= 3.014 \text{ V.} \\
 \text{as, } V_{SD} > V_{SD}(\text{sat}). \\
 \therefore \text{MOSFET is in saturation as assumed.}
 \end{aligned}$$

Handwritten note: $V_{SA} + V_{TH}$ overdrive

3. A particular n-channel MOSFET has parameters $V_{TH} = 0.6 \text{ V}$, $L = 0.8 \mu\text{m}$, $t_{ox} = 200 \text{ \AA}$, and $\mu_n = 600 \text{ cm}^2/\text{V}\cdot\text{s}$. A drain current of $I_D = 1.2 \text{ mA}$ is required when the device is biased in the saturation region at $V_{GS} = 3 \text{ V}$. Determine the required channel width of the device.

③ n-ch device

$$\begin{aligned}
 V_{TH} &= 0.6 \text{ V} & L &= 0.8 \mu\text{m} \\
 t_{ox} &= 200 \text{ \AA} & \mu_n &= 600 \text{ cm}^2/\text{V}\cdot\text{s} \\
 \text{In saturation, } I_D &= K_m (V_{GS} - V_{TH})^2 \\
 I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\
 \therefore 1.2 &= \frac{1}{2} \times 600 \times \frac{C_{ox}}{t_{ox}} \times \frac{W}{0.8 \times 10^{-4}} (3 - 0.6)^2 \\
 \therefore 1.2 &= 300 \times 1.726 \times 10^{-7} \times \frac{W}{0.8 \times 10^{-4}} \times 5.76 \\
 \therefore 1.2 &= 3.728 \times W \\
 W &= 3.218 \mu\text{m}
 \end{aligned}$$

Handwritten calculations for C_{ox} and E_0 :

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{\epsilon_{SiO_2} \epsilon_0}{t_{ox}}$$

$$E_0 = 8.854 \times 10^{-14}$$

$$\epsilon_r = 3.9$$

$$\epsilon_{SiO_2} = 3.9$$

Handwritten notes:

- $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{\epsilon_{SiO_2} \epsilon_0}{t_{ox}}$
- $E_0 = 8.854 \times 10^{-14}$
- $\epsilon_r = 3.9$
- $\epsilon_{SiO_2} = 3.9$
- Si MOSFET
- SiO₂
- enhancement mode MOSFET
- PMOS, $V_{TH} < 0$
- NMOS, $V_{TH} > 0$

4. For a p-channel enhancement-mode MOSFET, the parameters are $K_P = 2 \text{ mA/V}^2$ and $V_{TP} = -0.5 \text{ V}$. The gate is at ground potential, and the source terminal is at $+5 \text{ V}$. Determine I_D when the drain terminal voltage is: (a) $V_D = 0 \text{ V}$, (b) $V_D = 2 \text{ V}$, (c) $V_D = 4 \text{ V}$, and (d) $V_D = 5 \text{ V}$.

④ P-channel enhancement mode MOSFET.

$$\begin{aligned}
 K_P &= 2 \text{ mA/V}^2 \\
 V_{TP} &= -0.5 \text{ V} \\
 \text{Gate terminal is grounded.} \\
 \text{Source (S) is at } +5 \text{ V.}
 \end{aligned}$$

Handwritten calculations:

$$\begin{aligned}
 V_{GS} &= 0 \text{ V, } V_S = 5 \text{ V. } \therefore V_{SA} = 5 \text{ V.} \\
 V_{SD}(\text{sat}) &= V_{SA} + V_{TP} = 5 - 0.5 = 4.5 \text{ V}
 \end{aligned}$$


(i) When, $V_D = 0$, $V_{SD} = 5 \text{ V} > 4.5 \text{ V}$, biased in saturation

$$\begin{aligned}
 I_D &= K_P (V_{SA} + V_{TP})^2 \\
 &= 2 \times 10^{-3} (5 - 0.5)^2 \\
 I_D &= 40.5 \text{ mA}
 \end{aligned}$$

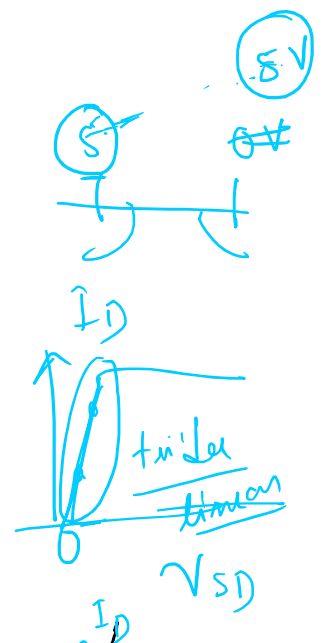(ii) When, $V_D = 2 \text{ V}$, $V_{SD} = V_S - V_D = 5 - 2 = 3 \text{ V}$.

So, MOSFET is in triode region.

$$\begin{aligned}
 I_D &= K_P [2 (V_{SA} + V_{TP}) V_{SD} + V_{SD}^2] \\
 &= 2 \times 10^{-3} [2 (5 - 0.5) 3 + 3^2] \\
 I_D &= 36 \text{ mA}
 \end{aligned}$$



$I_D = 3.6 \text{ mA}$


(iii) When $V_D = 4 \text{ V}$, $V_{SD} = 1 \text{ V}$, so, MOSFET in triode region.

$$I_D = k_p [2(V_{GS} + V_{TP})V_{SD} - V_{SD}^2]$$

$$= 2 \times 10^{-3} [2(5 - 0.5)1 - 1]$$

$$= 1.6 \text{ mA}$$

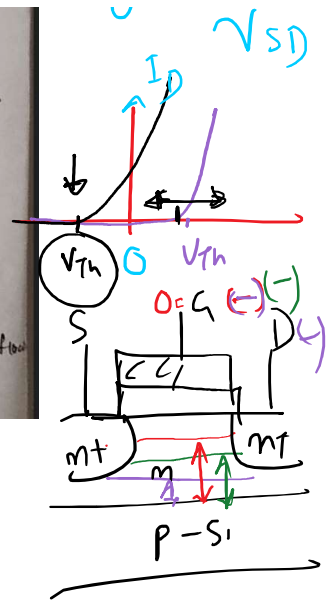(iv) When $V_D = 5 \text{ V}$, $V_{SD} = 0 \text{ V}$, so, no drain current will flow $\therefore I_D = 0$.



5. In the circuit shown in Fig. 3, the transistor parameters are $V_{Th} = 0.8 \text{ V}$ and $K_n = 0.5 \text{ mA/V}^2$. Calculate (i) Drain current I_D , (ii) Gate-source voltage (V_{GS}), and (iii) Drain-source voltage (V_{DS}).

6. The transistors (M_1 & M_2) in the circuit shown in Fig. 4 have parameters $V_{Th} = 0.4 \text{ V}$ and $K'_n = 120 \mu\text{A/V}^2$. (a) If the width-to-length ratios of M_1 and M_2 are $(W/L)_1 = (W/L)_2 = 30$, determine V_{GS1} , V_{GS2} , V_O , and I_D . (b) Repeat part (a) if the width-to-length ratios are changed to $(W/L)_1 = 30$ and $(W/L)_2 = 15$.

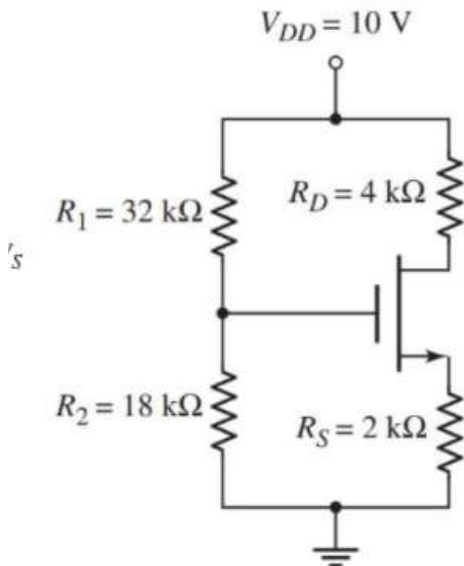


Fig. 3

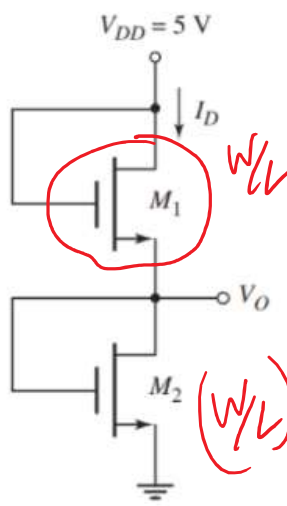


Fig. 4

⑤

$V_{DD} = 10 \text{ V}$

$R_1 = 32 \text{ k}\Omega$, $R_2 = 18 \text{ k}\Omega$, $R_D = 4 \text{ k}\Omega$, $R_S = 2 \text{ k}\Omega$

$V_G = V_{DD} \times \frac{R_2}{R_1 + R_2} = 10 \times \frac{18}{18 + 32} = 3.6 \text{ V}$

Assuming the MOSFET is in saturation,

$$I_D = k_m (V_{GS} - V_{Th})^2$$

$$= 0.5 \times 10^{-3} \times (V_{GS} - 0.8)^2 \quad \text{--- (1)}$$

Again, $I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$

$$I_D = \frac{3.6 - V_{GS}}{2 \times 10^3} \quad \text{--- (2)}$$

\therefore From (1) & (2),

$$0.5 \times 10^{-3} \times (V_{GS} - 0.8)^2 = \frac{3.6 - V_{GS}}{2 \times 10^3}$$

$$V_S = V_G - V_{GS}$$

$$= V_G - (V_G - V_S)$$

$$= V_G - V_G + V_S$$

$$= V_S$$

$V_{GS}^2 - 1.6 V_{GS} + 0.64 = 3.6 - V_{GS}$

$V_{GS}^2 - 0.6 V_{GS} - 2.96 = 0$

(P-3)

$$I_D = \frac{V_S}{R_S}$$

(P-3)

$$V_{GS}^2 - 1.6V_{GS} + 0.64 = 3.6 - V_{GS}$$

$$V_{GS}^2 - 0.6V_{GS} - 2.96 = 0$$

$$V_{GS} = \frac{0.6 \pm \sqrt{(0.6)^2 + 4 \times (2.96)}}{2}$$

$V_{GS} = 2.046 \text{ V}$ — (ii)

$$\frac{V_S}{R_S} = I_D = \frac{V_G - V_{GS}}{R_S} = \frac{3.6 - 2.046}{2} = 0.777 \text{ mA}$$
 — (i)
$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 10 - 0.777 \times (4 + 2)$$

$$V_{DS} = 5.338 \text{ V}$$
 — (iii)

$V_{DS}(\text{sat}) = V_{GS} - V_{TH} = 2.046 - 0.8 = 1.246 \text{ V}$

$V_{DS} > V_{DS}(\text{sat})$, so, MOSFET is in saturation. (our assumption is correct)

$$I_D = \frac{V_S}{R_S}$$

⑥

$V_{DD} = 5 \text{ V}$
 $V_{TH} = 0.4 \text{ V}$
 $K_{M1} = 120 \mu\text{A/V}^2$
 $\therefore K_{M2} = 120 \mu\text{A/V}^2$
 $\left(\frac{W_1}{L_1}\right) = \left(\frac{W_2}{L_2}\right) = 30$

① M_1 and M_2 are in saturation as $V_{DS} > V_{DS}(\text{sat})$
 $[V_{GS} = V_{DS}, V_{DS}(\text{sat}) = V_{GS} - V_{TH}]$

Same current is flowing through both transistors.

$$K_{M1}(V_{GS1} - V_{TH})^2 = K_{M2}(V_{GS2} - V_{TH})^2$$

$$\therefore \frac{1}{2} K_{M1} \left(\frac{W_1}{L_1}\right) (V_{GS1} - V_{TH})^2 = \frac{1}{2} K_{M2} \left(\frac{W_2}{L_2}\right) (V_{GS2} - V_{TH})^2$$

$V_{GS1} = V_{GS2}$ V_{TH} same for M_1 & M_2

$$I_D = \frac{1}{2} K_{M1} \left(\frac{W_1}{L_1}\right) (V_{GS1} - V_{TH})^2$$

$$= \frac{1}{2} \times 120 \times 10^{-6} \times 30 (2.5 - 0.4)^2$$

$$= 7.938 \text{ mA}$$

$V_{GS} = V_{DS}$

$$V_{DS1} + V_{DS2} = 5 \text{ V}$$

$$\therefore V_{GS1} + V_{GS2} = 5 \text{ V}$$

$$2V_{GS1} = 5 \text{ V}$$

$$\therefore V_{GS1} = 2.5 \text{ V} = V_{GS2} = V_0$$

② $\left(\frac{W}{L}\right)_1 = 30$; $\left(\frac{W}{L}\right)_2 = 15$

$$\frac{1}{2} K_{M1} \left(\frac{W_1}{L_1}\right) (V_{GS1} - V_{TH})^2 = \frac{1}{2} K_{M2} \left(\frac{W_2}{L_2}\right) (V_{GS2} - V_{TH})^2$$

$$30 (V_{GS1} - V_{TH})^2 = 15 (V_{GS2} - V_{TH})^2$$


$$1.414 V_{GS1} - 1.414 V_{TH} = V_{GS2} - V_{TH} = V_{DS2} - V_{TH} = 5 - V_{GS1} - V_{TH}$$


$$\therefore 2.414 V_{GS1} = 5 + 0.414 V_{TH} = 5.1656$$

$$\therefore V_{GS1} = 2.139 \text{ V}$$

$$\therefore V_{GS2} = 2.86 \text{ V}$$

Find I_D

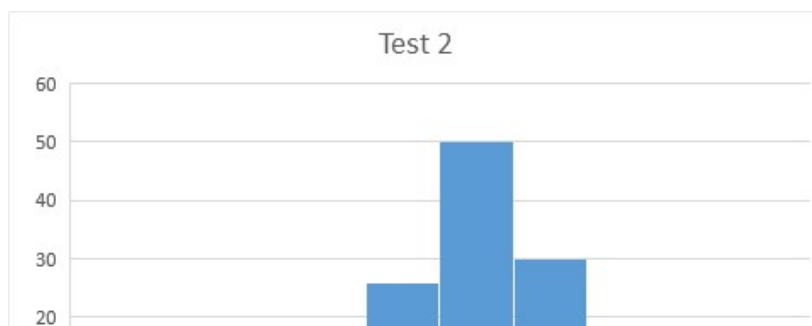

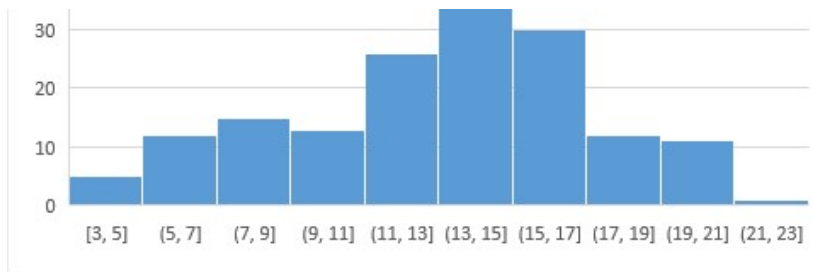

7. In the circuit shown in Fig. 5, find the value of R_S and R_D when $V_D = -3$ V and $I_D = 0.5$ mA. The transistor parameters are given as $K'_p = 30$ $\mu\text{A}/\text{V}^2$, $W/L = 20$ and $V_{Th} = -1.2$ V.

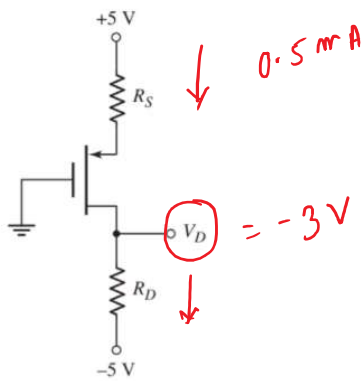


Fig. 5

⑦

$$I_D = \frac{1}{2} K'_p \frac{W}{L} (V_{GS} + V_{Th})^2$$

$$0.5 = \frac{1}{2} \times 30 \times 10^{-6} \times 20 (V_{GS} - 1.2)$$

$$\therefore V_{GS} = 2.49 \text{ V}, \quad V_G = 0, \quad \therefore V_S = 2.49 \text{ V}$$

$$V_S = 5 - I_D R_S$$


$$\therefore R_S = \frac{5 - V_S}{I_D} = \frac{5 - 2.49}{0.5}$$


$$R_S \approx 5 \text{ k}\Omega$$

again, $\frac{V_D - (-5)}{R_D} = I_D$; $V_D = -3$ V given.

$$\therefore R_D = 4 \text{ k}\Omega$$

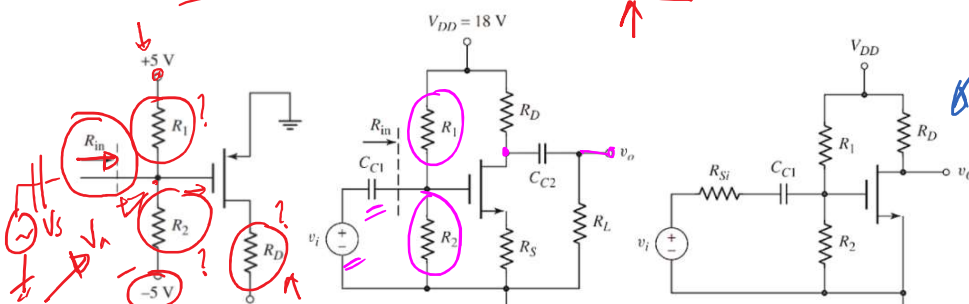8. The circuit shown in Fig. 6 have transistor parameters $V_{Th} = -1.75$ V and $K_p = 3$ mA/V². The drain current (I_D) in the circuit is 5 mA, $V_{SD} = 6$ V and $R_{in} = 80$ k Ω . Find R_1 , R_2 and R_D .



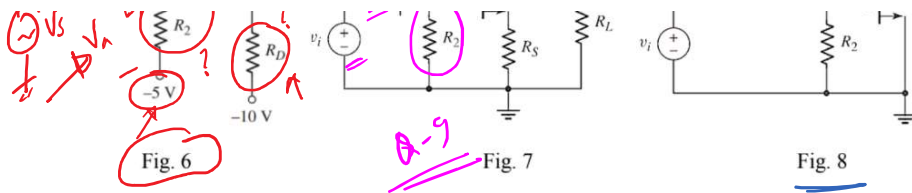

8

$I_D = 5 \text{ mA}$
 $V_{SD} = 6 \text{ V}$
 $V_{TH} = -1.75 \text{ V}, K_P = 3 \text{ mA/V}^2$
 $+V_{SD} + I_D R_D - 10 = 0$
 $R_{in} = 80 \text{ k}\Omega = \frac{R_1 R_2}{R_1 + R_2}$ — (1)

$V_G = -5 + (5 - (-5)) \times \frac{R_2}{R_1 + R_2}$
 $V_G = -5 + 10 \frac{R_2}{R_1 + R_2}$ — (2)

$I_D = K_P (V_{SG} + V_{TH})^2$
 $\therefore 5 = 3 (V_{SG} - 1.75)^2$
 $\therefore V_{SG} = 3.04$
 $V_S - V_G = 3.04; V_S = 0$
 $V_G = -3.04 \text{ V}$

From (2)
 $-3.04 = -5 + 10 \frac{R_2}{R_1 + R_2}$
 $\therefore 1.96 = 10 \left(\frac{R_1 R_2}{R_1 + R_2} \right) \cdot \frac{1}{R_1}$
 $\therefore 1.96 = 10 \times \frac{80}{R_1}$
 $\therefore R_1 = \frac{10 \times 80}{1.96}$
 $R_1 = 408.16 \text{ k}\Omega$ — From (1)

From (1), $R_2 = 99.4 \text{ k}\Omega$

$g_m = 2 \sqrt{K_m I_{DQ}}$
 $2.2 = 2 \sqrt{K_m (6)}$
 $\therefore K_m = 0.202 \text{ mA/V}^2$

$V_{GSQ} = 2.8 \text{ V}$
 $V_{DSQ} = 10 \text{ V}$
 $g_m = 2.2 \text{ mA/V}$
 $\lambda = 20, R_L = 1 \text{ k}\Omega$
 $A_v = -1, R_{in} = 100 \text{ k}\Omega$

$I_{DQ} = K_m (V_{GSQ} - V_{TH})^2$
 $\therefore 6 = 0.202 (2.8 - V_{TH})^2$
 $\therefore V_{TH} = -2.65 \text{ V}$

$V_{DD} = I_{DQ} (R_D + R_S) + V_{DSQ}$
 $\therefore V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S)$
 $V_{DSQ} = 18 - 6 (R_D + R_S) = 10 \text{ V (given)}$
 $R_D + R_S = 1.33 \text{ k}\Omega$ — (1)

given that, $A_v = -1$

Circuit diagram for problem 5 showing a MOSFET with $V_{DD} = 18 \text{ V}$, R_{in} , C_{c1} , R_1 , R_2 , R_D , R_S , C_{c2} , R_L , and V_{GS} . The gate is connected to a voltage divider. The drain is connected to R_D and the source is connected to R_S .

$R_D + R_S = 1.33 \text{ k}\Omega$ — (1)

given that, $A_v = -1$

$V_{i_s} = V_{gs} + g_m V_{gs} R_S$

$V_{gs} = \frac{V_{i_s}}{1 + g_m R_S}$

$V_o = -g_m V_{gs} (R_D || R_L)$


$V_o = -g_m \frac{V_{i_s}}{1 + g_m R_S} (R_D || R_L)$

$V_o = -\frac{g_m (R_D || R_L)}{1 + g_m R_S} V_{i_s}$

$\left(\frac{V_o}{V_{i_s}}\right) = A_v = -\frac{g_m (R_D || R_L)}{1 + g_m R_S} = -1$ — (2)

$g_m (R_D || R_L) = 1 + g_m R_S$; substitute $R_S = 1.33 - R_D$ from (1).

$g_m (R_D || R_L) = 1 + g_m (1.33 - R_D)$

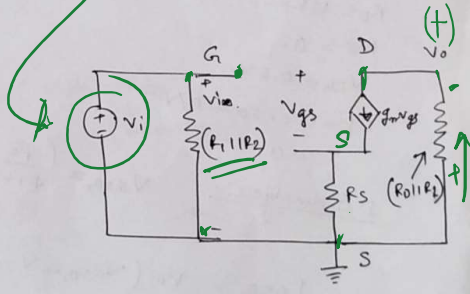

$g_m (R_D || R_L) = 1 + g_m (1.33 - R_D)$ from (1).

g_m, R_L known, Find R_D

$2.2 R_D^2 + 0.47 R_D - 3.93 = 0$

$R_D = 1.23 \text{ k}\Omega$; neglect the (-) value.

$R_S = 1.33 - 1.23 = 0.1 \text{ k}\Omega$

Rin value given, $R_{in} = (R_1 || R_2) = \frac{R_1 \times R_2}{R_1 + R_2} = 100 \text{ k}\Omega$ — (3)

$V_{GS0} = 2.8 \text{ V}$

$V_S = I_{D0} \cdot R_S = 6 \times 0.1 = 0.6 \text{ V}$

$V_{GS} = V_G - V_S$

$V_G = V_{GS} + V_S$

$V_G = 2.8 + 0.6 = 3.4 \text{ V} = V_{DD} \times \frac{R_2}{R_1 + R_2}$


$V_{DD} \times \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_1} = 3.4$

$18 \times 100 \times \frac{1}{R_1} = 3.4$


$R_1 = 529 \text{ k}\Omega$

from (3) Find R_2 ; $R_2 = 123 \text{ k}\Omega$

P-6

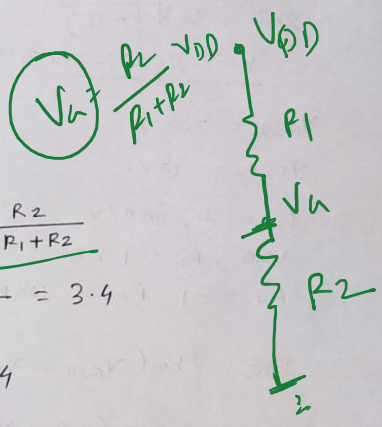

10. The parameters of the circuit shown in Fig. 8 are $V_{DD} = 5 \text{ V}$, $R_1 = 520 \text{ k}\Omega$, $R_2 = 320 \text{ k}\Omega$, $R_D = 10 \text{ k}\Omega$, and $R_{Si} = 0$. Assume transistor parameters of $V_{Th} = 0.8 \text{ V}$, $K_n = 0.20 \text{ mA/V}^2$, and $\lambda = 0$. (a) Determine the small-signal transistor parameters g_m and r_o . (b) Find the small-signal voltage gain. (c) Calculate the input and output resistances. (d) Repeat (a) and (b) considering $R_{Si} = 1 \text{ k}\Omega$.
11. Consider the NMOS amplifier with saturated load in Fig. 9. The transistor parameters are $V_{Th,D} = V_{Th} = 0.6 \text{ V}$, $k_n' = 100 \mu\text{A/V}^2$, $\lambda = 0$, and $(W/L)_L = 1$. Estimate the W/L ratio of M_D for realizing the overall small-signal voltage gain $|A_v| = 5$.

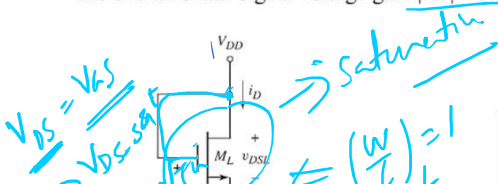

Please Note: For n-channel MOSFET

$K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$ is the conduction parameter

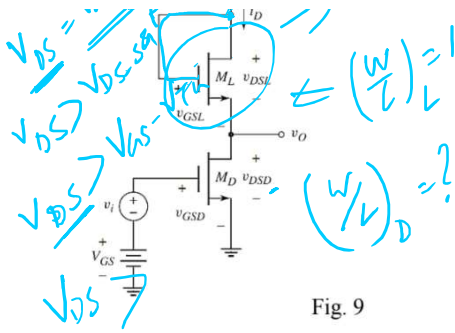


Fig. 9

Please Note: For n-channel MOSFET

$$K_n = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \text{ is the conduction parameter}$$

$$K_n = \frac{1}{2} K'_n \frac{W}{L}$$

$$K'_n = \mu_n C_{ox} \text{ is the process conduction parameter}$$

10

$R_1 = 520 \text{ k}\Omega$
 $R_2 = 320 \text{ k}\Omega$
 $R_D = 10 \text{ k}\Omega$
 $R_{Si} = 0$
 $V_{Th} = 0.8 \text{ V}$
 $K_m = 0.20 \text{ mA/V}^2$
 $\lambda = 0$

D.C analysis:

$$V_{GSB} = \left(\frac{R_2}{R_1 + R_2} \right) \times V_{DD} = \left(\frac{320}{520 + 320} \right) \times 5 \text{ V}$$

$$= 1.9 \text{ V}$$

$$I_{DSB} = K_m (V_{GSB} - V_{Th})^2 = 0.2 (1.9 - 0.8)^2$$

$$= 0.242 \text{ mA}$$

$$\therefore V_{DSB} = V_{DD} - I_{DSB} \cdot R_D$$

$$= 5 - 0.242 \times 10$$

$$= 2.58 \text{ V}$$

$$V_{GSB} - V_{Th} = 1.1$$

As, $V_{DSB} > V_{GSB} - V_{Th}$, the MOSFET is biased in saturation region.

(a) Small-signal parameters.

$$g_m = 2 \sqrt{K_m I_{DSB}}$$

$$= 2 \sqrt{0.2 \times 0.242}$$

$$g_m = 0.44 \text{ mS}$$

$$r_o = \infty \text{ as } \lambda = 0. \quad \left[r_o = \frac{1}{\lambda I_{DSB}} \right]$$

(b)

Small-signal equivalent circuit.

$$V_o = -g_m R_D V_{gs}$$

$$V_o = -g_m R_D \times \frac{R_1 || R_2}{R_{Si} + R_1 || R_2} \times V_i$$

$$R_1 || R_2 = \frac{520 \times 320}{520 + 320} \text{ k}\Omega$$

$$= 198.09 \text{ k}\Omega$$

$V_o = -g_m R_D V_{gs}$
 $V_o = -g_m R_D \times \frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2} \times V_i$
 $\therefore \left(\frac{V_o}{V_i} \right) = -g_m R_D \times \frac{R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2}$ (general expression).
 $A_v = -0.44 \times 10 \times \frac{198.09}{0 + 198.09}$; $R_{si} = 0$ for this case. (b).
 $A_v = -4.4$

(c) Input impedance = $R_i = R_1 \parallel R_2 = 198 \text{ k}\Omega$.
 Output " = $R_o = R_D = 10 \text{ k}\Omega$.

(d) When, $R_{si} = 1 \text{ k}\Omega$.
 g_m remains unchanged (0.44 mS).
 $r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{0} = \infty$ (unchanged).
 \therefore gain $A_v = -4.4 \times \frac{198.09}{1 + 198.09} \approx -4.37$.

