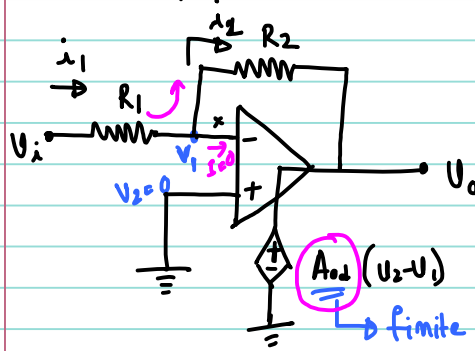


Lec-26

# Inverting Amplifier having finite $A_{od}$



Assuming, input resistance is infinite

$$\begin{aligned} i_1 &= \frac{V_i - V_1}{R_1} \\ i_2 &= \frac{V_1 - V_o}{R_2} \end{aligned}$$

$$i_1 = i_2$$

$$\frac{V_i - V_1}{R_1} = \frac{V_1 - V_o}{R_2}$$

$$\therefore \frac{V_i + V_o/A_{od}}{R_1} = \frac{-\frac{V_o}{A_{od}} - V_o}{R_2}$$

$$\checkmark \rightarrow \frac{V_o}{V_i} = \frac{-R_2}{R_1 \left[ 1 + \left( 1 + \frac{R_2}{R_1} \right) \frac{1}{A_{od}} \right]} = A_v$$

fixed for this case

$$\rightarrow R_2 = 10 R_1$$

$$A_{od} = 100, \quad \frac{V_o}{V_i} = -9.001$$

$$A_{od} = 1000, \quad \frac{V_o}{V_i} = -9.89$$

$$A_{od} = 10000, \quad \frac{V_o}{V_i} = -9.99$$

Ideal op-amp

$$A_{od} \rightarrow \infty$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$R_2 = 10 R_1$$

$$\frac{V_o}{V_i} = -10$$

$$\text{Gain} = -\frac{R_2}{R_1}$$

gain = 100


$$\downarrow \rightarrow R_1 = 50 \text{ k}\Omega$$

$$R_2 = 5000 \text{ k}\Omega$$

$$R_2 = 5 \text{ M}\Omega$$
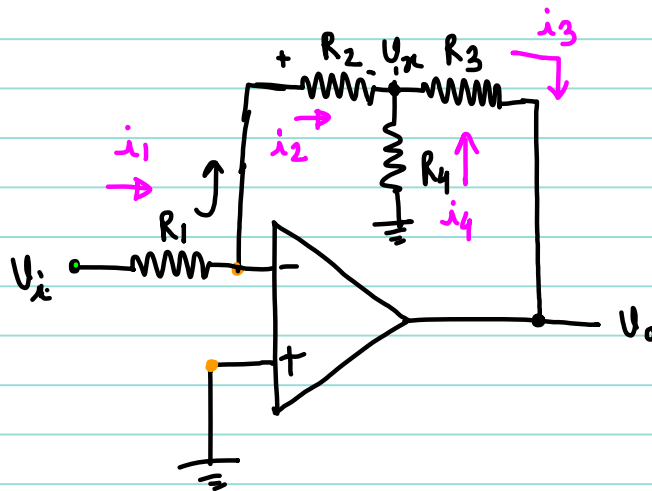
# Inverting Amplifier with T-Network

op-Amp is Ideal  
input resistance  $\rightarrow \infty$   
 $A_{od} \rightarrow \infty$



$$\frac{V_x - V_o}{R_3} = i_3 \\ = i_2 + i_4$$

$$i_1 = \frac{V_i - 0}{R_1} = \frac{V_i}{R_1} = i_2 \quad ; \quad V_x = 0 - i_2 R_2 \\ = - \frac{V_i}{R_1} \cdot R_2 = - V_i \times \frac{R_2}{R_1}$$

$$i_4 = \frac{0 - V_x}{R_4} = - \frac{V_x}{R_4}$$

$$i_2 + i_4 = i_3$$

$$- \frac{V_x}{R_2} - \frac{V_x}{R_4} = \frac{V_x - V_o}{R_3}$$

$$- \frac{V_x}{R_2} - \frac{V_x}{R_4} - \frac{V_x}{R_3} = - \frac{V_o}{R_3}$$

gain  $\rightarrow$


$$V_o = R_3 \times \left( - \frac{R_2}{R_1} V_i \right) \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) \\ \frac{V_o}{V_i} = - \frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right)$$

-100

$$\left. \begin{aligned} R_1 &= 50 \text{ k}\Omega \\ R_2 &= R_3 = 390 \text{ k}\Omega \\ R_4 &= 33 \text{ k}\Omega \end{aligned} \right\}$$

$$\frac{V_o}{V_i} = -107.78$$

## Summing Amplifier:

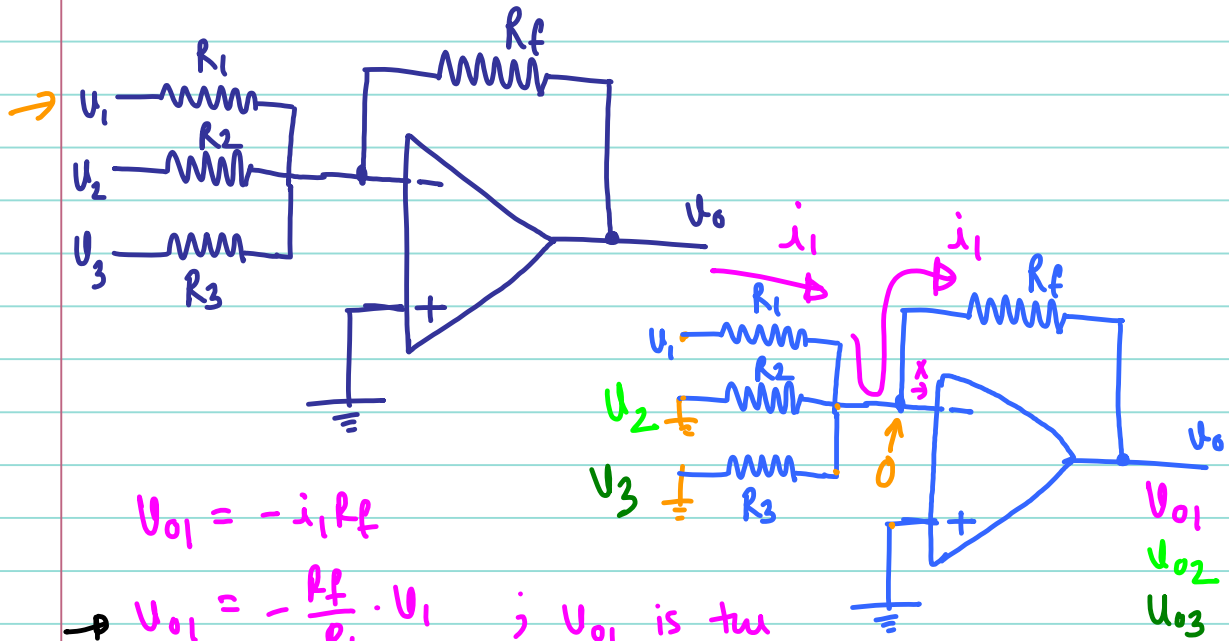

$$V_{01} = -i_1 R_f$$

$$\rightarrow V_{01} = -\frac{R_f}{R_1} \cdot U_1 \quad ; \quad V_{01} \text{ is the o/p for i/p } U_1$$


$$V_{03} \rightarrow U_3 \quad V_{02} \rightarrow U_2$$

$$\rightarrow V_{02} = -\frac{R_f}{R_2} U_2 \quad \rightarrow V_{03} = -\frac{R_f}{R_3} \cdot U_3$$

$$\text{Total o/p} = V_{01} + V_{02} + V_{03} = - \left( \frac{R_f}{R_1} U_1 + \frac{R_f}{R_2} U_2 + \frac{R_f}{R_3} U_3 \right)$$

$$\underline{R_1 = R_2 = R_3}, \quad \text{Total o/p} = - \frac{R_f}{R_1} (U_1 + U_2 + U_3)$$

## Non-Inverting Amplifier:

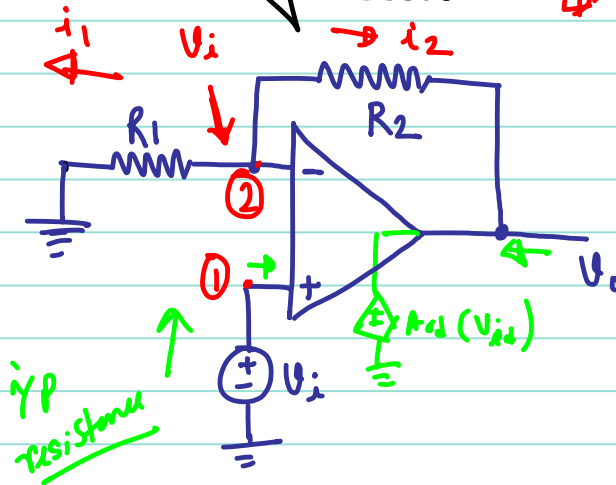

Node ① and ② are virtually shorted.

$$i_1 = \frac{V_i}{R_1} \quad ; \quad i_2 = \frac{V_i - V_o}{R_2}$$

$$i_1 = -i_2, \quad \frac{V_i}{R_1} = \frac{V_o - V_i}{R_2} ;$$


$$V_i R_2 = V_o R_1 - V_i R_1$$

$$\text{gain} = \frac{V_o}{V_i} = \frac{R_2 + R_1}{R_1} = \left(1 + \frac{R_2}{R_1}\right) \quad \begin{matrix} \text{Always} \\ \geq 1 \end{matrix}$$



↑  
positive

$\left\{ \begin{array}{l} \text{i/p resistance} \rightarrow \infty \\ \text{o/p} \quad \quad \quad \rightarrow 0. \end{array} \right.$

## Voltage Follower/Buffer:

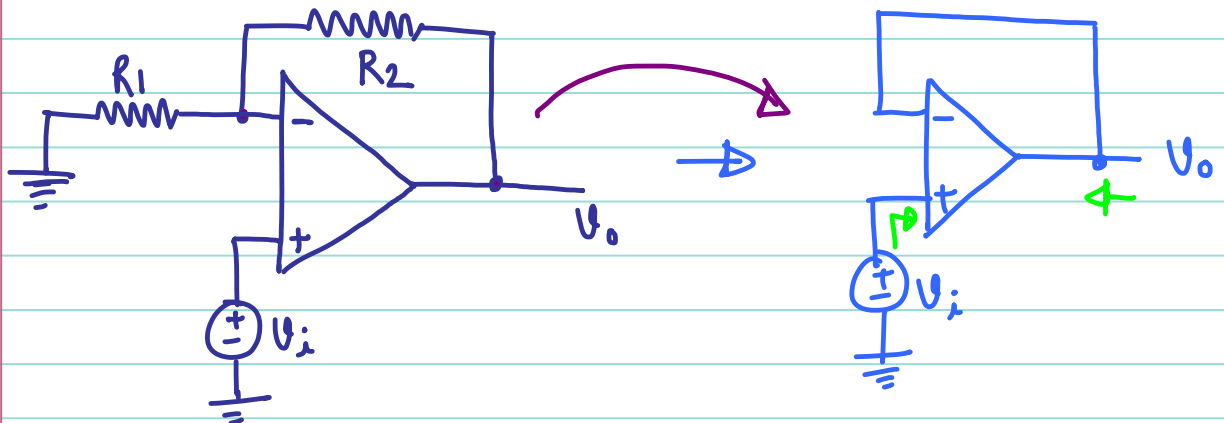

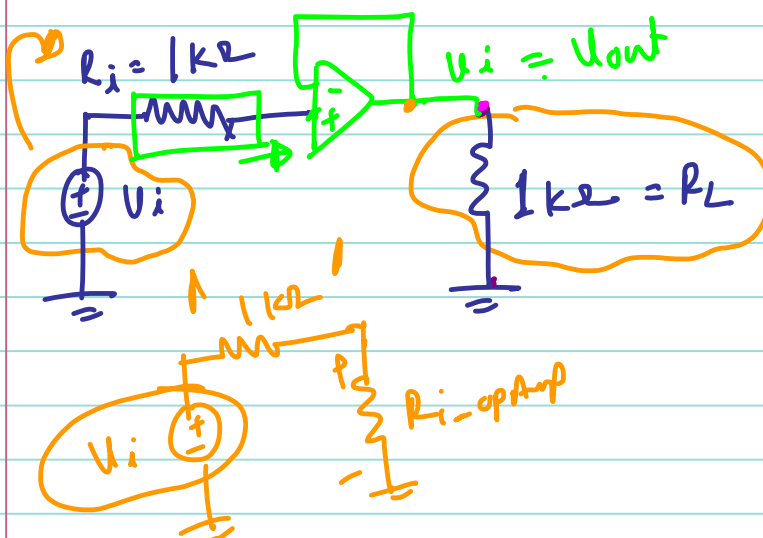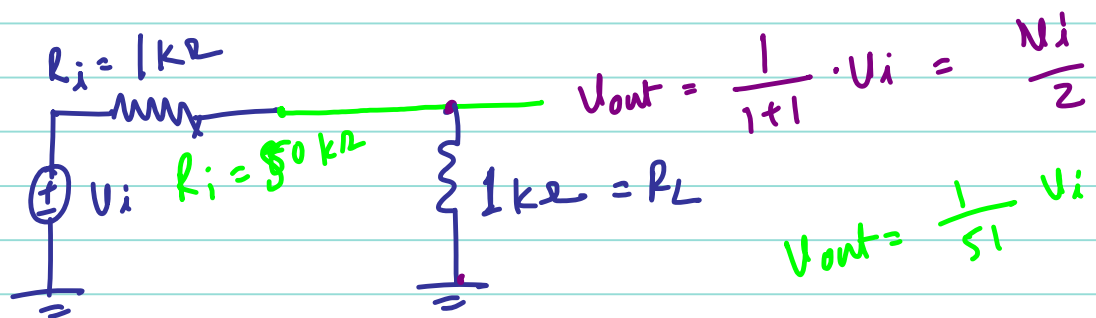$\text{gain} = 1 + \frac{R_2}{R_1}$  ; if,  $R_2 = 0$ ,  $R_1 \rightarrow \text{any value}$   
 $\left. \begin{array}{l} \text{i/p resistance} \rightarrow \infty \\ \text{o/p} \quad \quad \quad = 0 \end{array} \right\}$  Say,  $R_1 \rightarrow \infty$ , if,  $R_2$  is finite  
 $\hookrightarrow \text{gain} = 1 \rightarrow R_2 = 0$




Loading effect

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$$I = C \frac{dV}{dt}$$

Integrator:

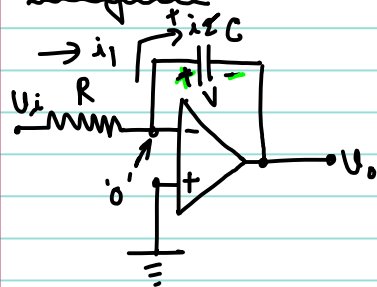

$$i_1 = \frac{U_i}{R}$$

$$V_o = -V$$

$$i_2 = C \frac{dV}{dt} = -C \frac{dV_o}{dt}$$

$$i_2 = i_1$$

$$\frac{U_i}{R} = -C \frac{dV_o}{dt}$$

'C' was discharged initially

$$V_o = -\frac{1}{RC} \int U_i dt$$


if, capacitor was charged initially by a voltage  $V_C$

then,

$$V_o = -V_C - \frac{1}{RC} \int U_i dt$$

sign depends on the polarity

Differentiator:

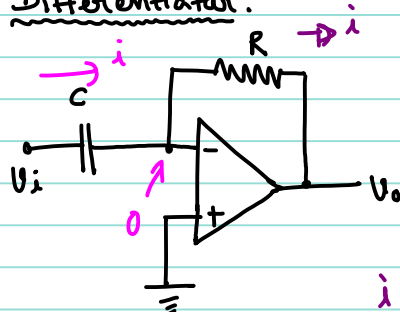


$$i = C \frac{dU_i}{dt}$$

$$V_o = 0 - iR = -RC \frac{dU_i}{dt}$$

$$\rightarrow V_o = -RC \frac{dU_i}{dt}$$

### Log Amplifier:

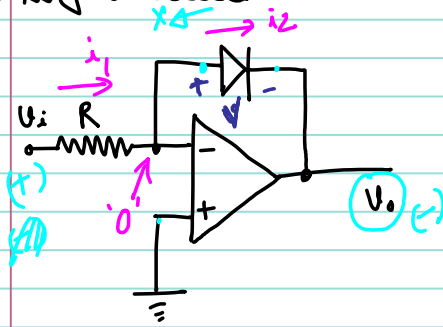

$$i_1 = \frac{U_i}{R}$$

$$i_2 = I_s \left[ \exp\left(\frac{V}{V_T}\right) - 1 \right]$$

$$[V_o = -V]$$

$$i_2 = I_s \left[ \exp\left(-\frac{V_o}{V_T}\right) - 1 \right]$$

$$i_1 = i_2$$

$$\frac{U_i}{R} = I_s \left[ \exp\left(-\frac{V_o}{V_T}\right) - 1 \right]$$


$|V_o| > 3V_T$   
neglect '-1' term

$$\frac{U_i}{R} = I_s \exp\left(-\frac{V_o}{V_T}\right)$$

$$\ln\left(\frac{U_i}{I_s R}\right)$$

$$V_o = -V_T \ln\left(\frac{U_i}{I_s R}\right)$$

### Anti-log Amplifier:

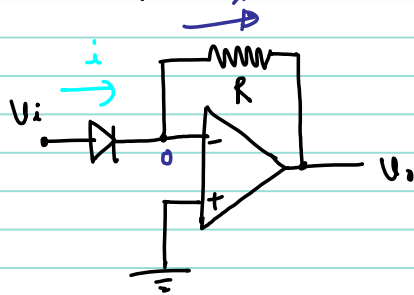


$$i = I_s \exp\left(\frac{U_i}{V_T}\right)$$

$$V_o = -iR$$


$$V_o = -I_s R \exp\left(\frac{U_i}{V_T}\right)$$

$$V_o \propto \exp\left(\frac{U_i}{V_T}\right)$$


### Analog Multipliers:

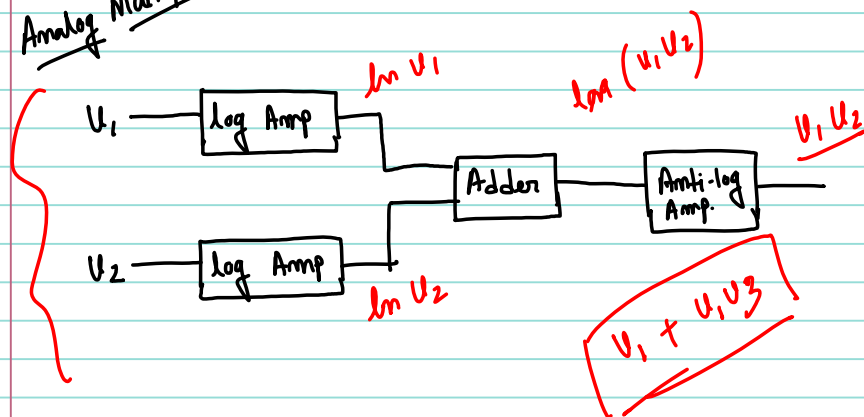

# Difference Amplifier:

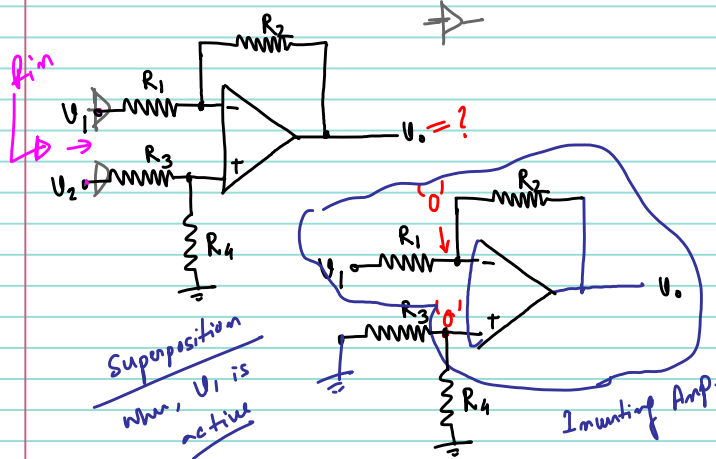

$$U_{o1} = -\frac{R_2}{R_1} U_1$$

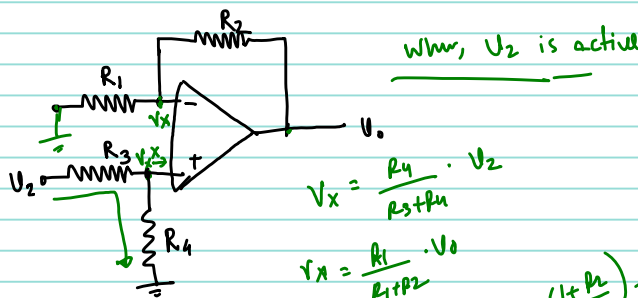

$$V_x = \frac{R_4}{R_3 + R_4} \cdot U_2$$

$$V_x = \frac{R_1}{R_1 + R_2} \cdot U_{o1}$$

$$U_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_x = \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} U_2$$

$$U_{o2} = U_2 \left( \frac{R_4}{R_3 + R_4} \right) \cdot \left( \frac{R_2 + R_1}{R_1} \right) - \frac{R_2}{R_1} U_1$$

Total o/p  $U_o = U_{o1} + U_{o2}$

$$U_o = U_2 \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) - \frac{R_2}{R_1} U_1$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} ; U_o = \frac{R_2}{R_1} (U_2 - U_1)$$

$$1 + \frac{R_2}{R_1} = \frac{R_2}{R_1} + 1 \quad \frac{R_3 + R_4}{R_3} = \left( \frac{R_2 + R_1}{R_1} \right)$$

$$V = I R_1 + I R_2$$

$$\frac{V}{I} = R_1 + R_2$$

input resistance

$$= (R_1 + R_2)$$

