
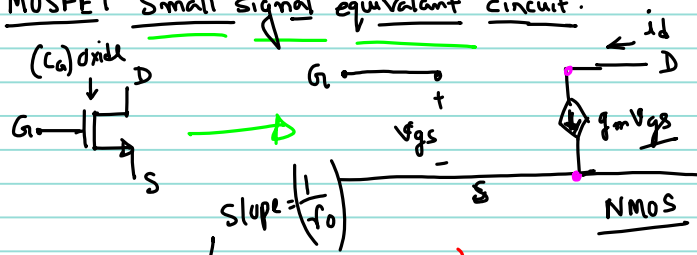


$\tau_R = \frac{1}{\omega_c}$ range of freq. for which gate is open circuit.

MOSFET Small signal equivalent circuit:

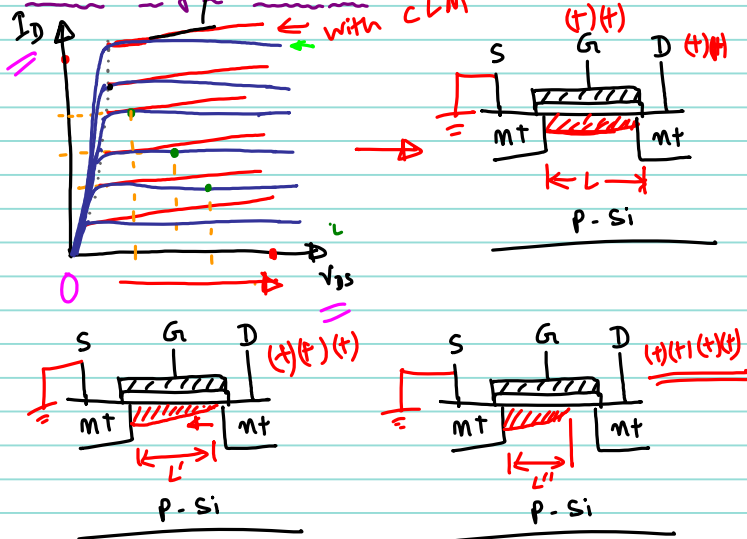

Channel length modulation: (CLM)




$\uparrow I_D \propto \left(\frac{W}{L}\right) \downarrow L$ is decreasing.

$$I_D = k_n (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \quad ; \quad \lambda = \text{channel length modulation parameter.}$$


$$r_o = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \left[k_n (V_{GS} - V_{th})^2 \lambda \right]^{-1}$$
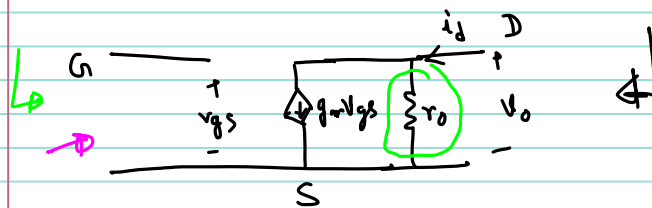
$$r_o = [I_{DQ} \lambda]^{-1} = \frac{1}{\lambda I_{DQ}}$$




lec-24

For PMOS:

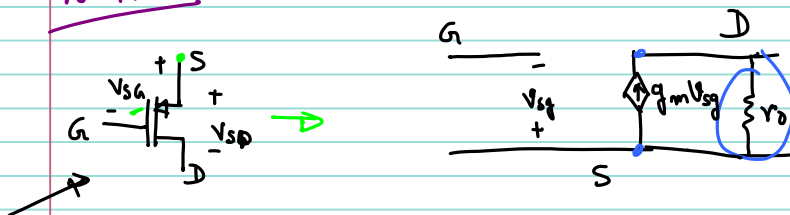

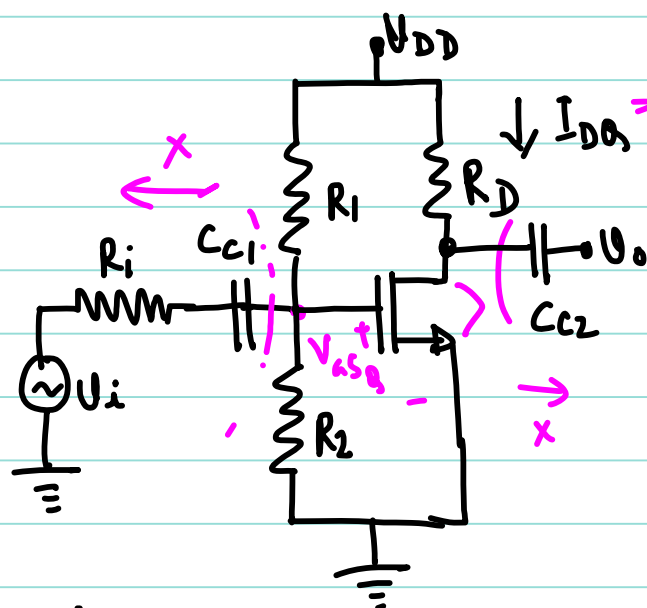Basic Common-Source Amplifier (CS Amplifier)



$$V_{DD} = 10V$$

$$R_1 = 70.9 k\Omega, R_2 = 29.1 k\Omega$$

$$R_D = 5 k\Omega$$

$$\rightarrow V_{TH} = 1.5V$$

$$k_n = 0.5 \text{ mA/V}^2$$

$$\lambda = 0.01 \text{ V}^{-1}$$

$$R_i = 4 k\Omega$$

Find the small-signal gain.

DC Analysis

$$V_{GSQ} = V_{DD} \times \frac{R_2}{R_1 + R_2} = 2.91V$$

Assume, MOSFET is in saturation, $I_{DQ} = k_n (V_{GSQ} - V_{TH})^2 = 1 \text{ mA}$

$$V_{DSQ} = V_{DD} - I_D R_D = 5V$$



$$; V_{DS\text{-}sat} = V_{GSQ} - V_{TH}$$

$$V_{DSQ} > V_{DS\text{-}sat}, \text{ Saturation}$$

$$= 2.91 - 1.5$$

$$= 1.41V.$$

AC Analysis.

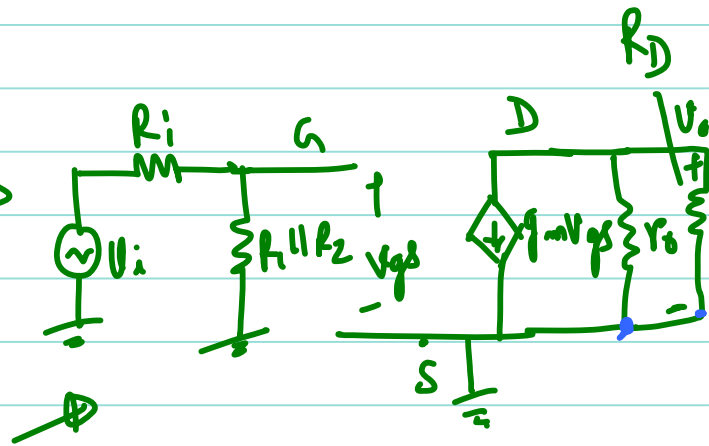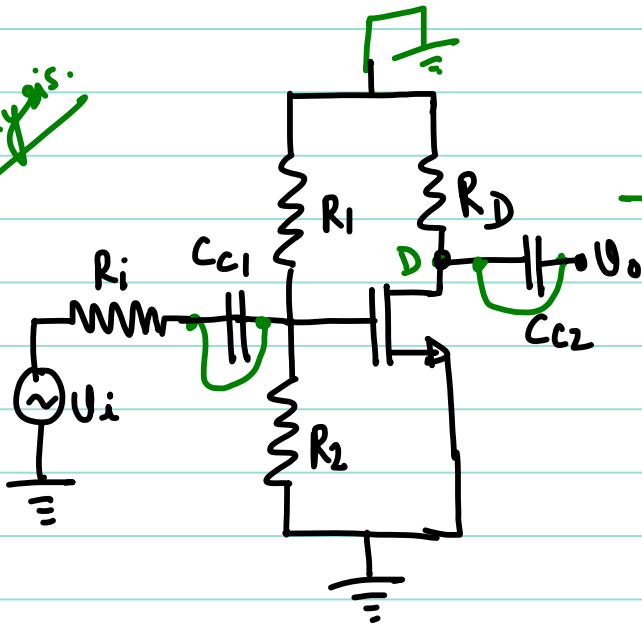

$$Gain = \frac{U_o}{U_i}$$

$$g_m = 2k_n(V_{GS} - V_{TN})$$

$$= 1.41 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}}$$

$$= 100 \text{ k}\Omega$$

if, r_o is infinite



$$Gain = \frac{U_o}{U_i} = -g_m (r_o || R_D) \times \frac{R_1 || R_2}{R_i + R_1 || R_2}$$

$$Gain = -5.62$$



$$Gain = -g_m R_D \cdot \frac{R_1 || R_2}{R_i + R_1 || R_2}$$

CS Amplifier with Source Resistor:

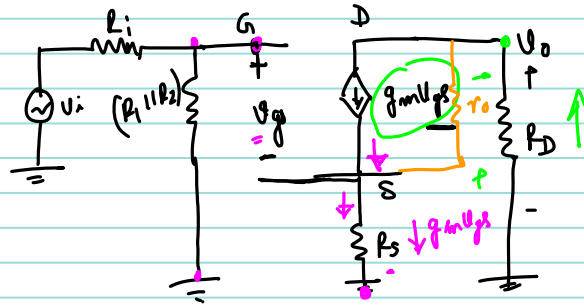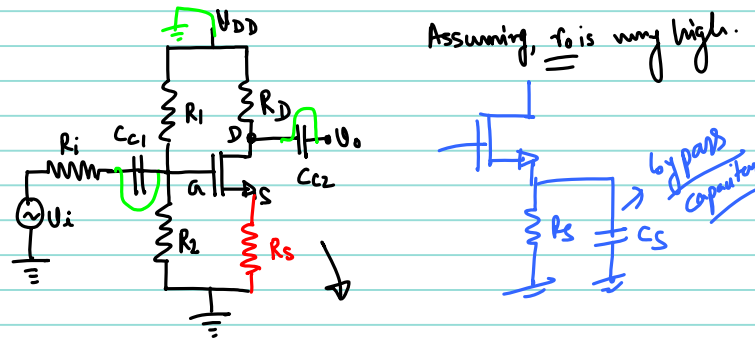

$V_{gs} + g_m V_{gs} R_s = \text{Voltage drop across } (R_1 || R_2)$

$$V_{gs} + g_m V_{gs} R_s = V_i \times \left(\frac{R_1 || R_2}{R_1 || R_2 + R_i} \right)$$

$$V_{gs} (1 + g_m R_s) = V_i \times \left(\frac{R_1 || R_2}{R_1 || R_2 + R_i} \right)$$

$$V_{gs} = \frac{V_i}{1 + g_m R_s} \cdot \frac{R_1 || R_2}{R_1 || R_2 + R_i}$$

$$V_o = -g_m V_{gs} \times R_D$$

$$V_o = -g_m \cdot \frac{V_i}{1 + g_m R_s} \cdot \frac{R_1 || R_2}{R_1 || R_2 + R_i} \times R_D$$

$$\text{Gain} = \frac{V_o}{V_i} = - \frac{(g_m R_D)}{1 + g_m R_s} \cdot \left(\frac{R_1 || R_2}{R_1 || R_2 + R_i} \right) \quad \text{--- (1) --- with } R_s$$

$$\text{Gain} = - (g_m R_D) \cdot \left(\frac{R_1 || R_2}{R_1 || R_2 + R_i} \right) \quad \text{--- without } R_s$$


Gain reduces by $\frac{1}{1 + g_m R_s}$ factor.

if, $(R_1 || R_2) \gg R_i$ and, $1 + g_m R_s \gg 1$


with R_s

$$\text{Gain} = \frac{V_o}{V_i} \approx - \frac{g_m R_D}{g_m R_s} \approx \left(- \frac{R_D}{R_s} \right)$$


Enhancement Load:

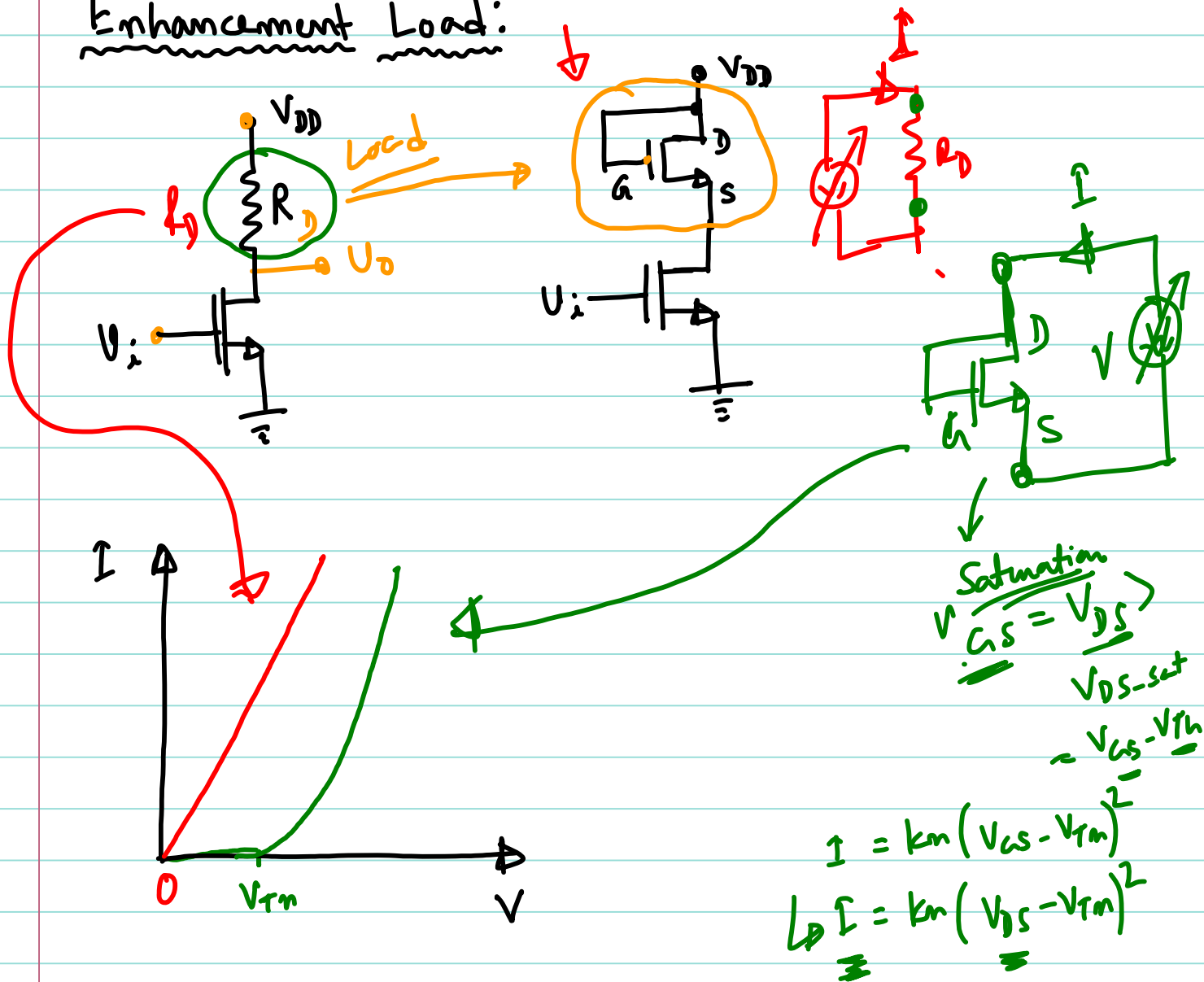

Small signal model:

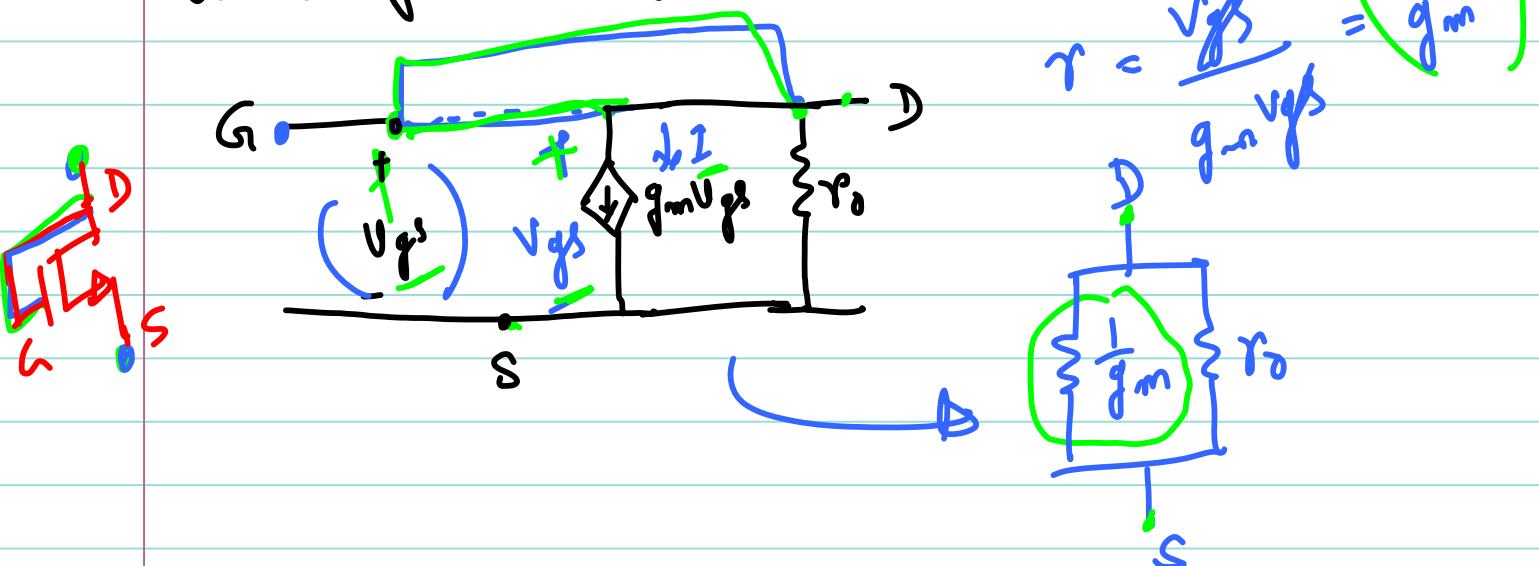

NMOS Amplifier with Enhancement Load:

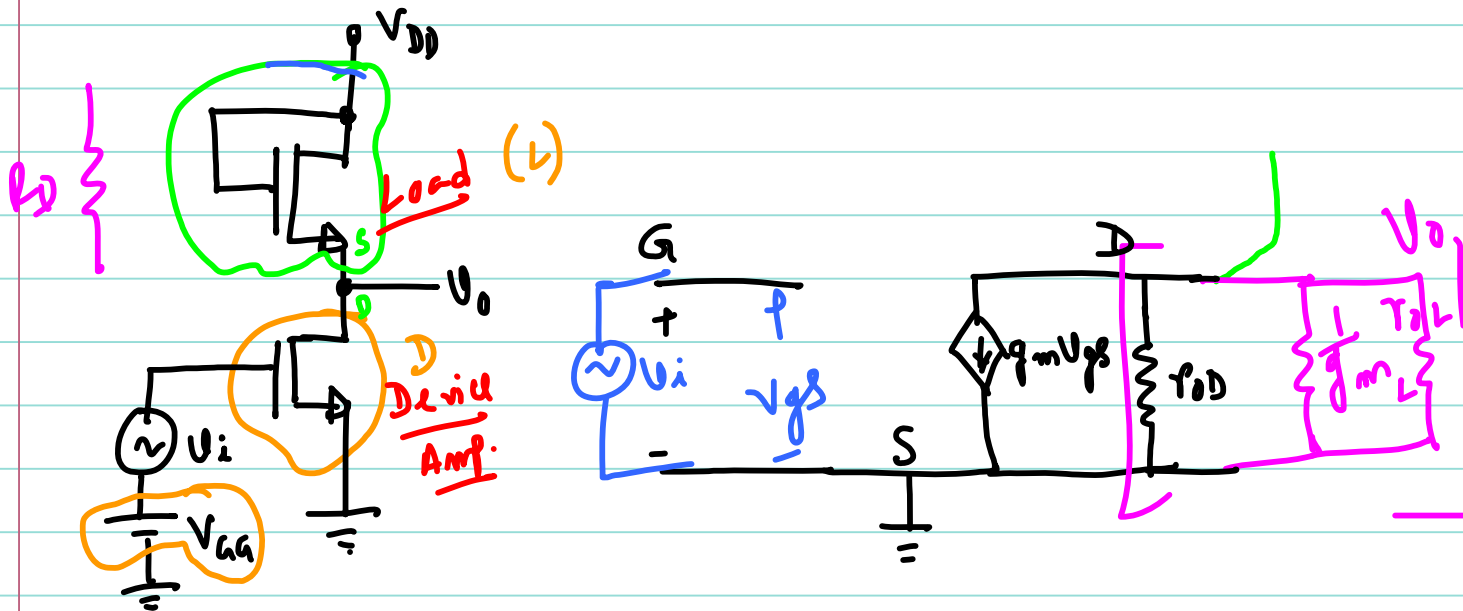

$$V_{gs} = V_i$$

$$V_o = -g_m V_{gs} \left(r_{OD} \parallel \frac{1}{g_{mL}} \parallel r_{OL} \right)$$

$$V_o = -g_m V_i \left(r_{OD} \parallel \frac{1}{g_{mL}} \parallel r_{OL} \right)$$

$$\therefore A_{v_{mid}} = \frac{V_o}{V_i} = -g_m \left(r_{OD} \parallel \frac{1}{g_{mL}} \parallel r_{OL} \right)$$