

Topic: Op-Amp

1. Determine the expressions/values of v_o (V_o) in the following circuits:

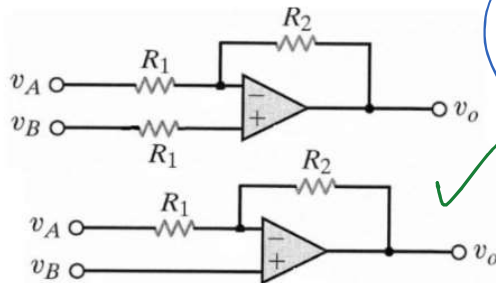


Fig. 1a (i & ii)

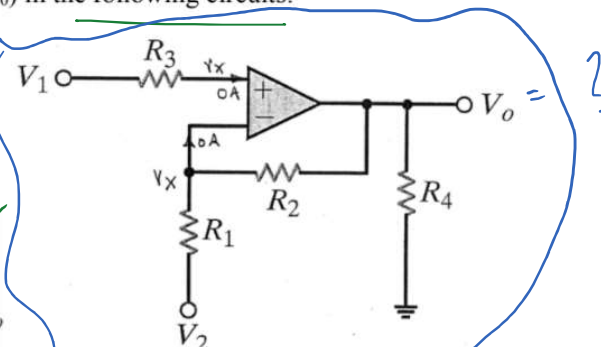


Fig. 1b

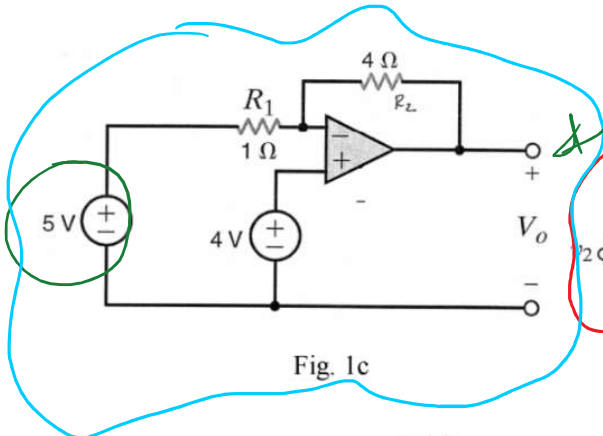


Fig. 1c

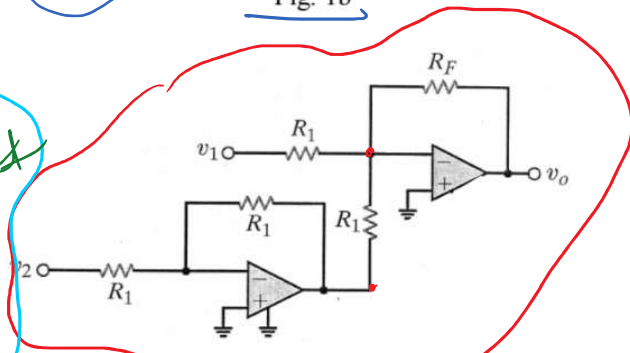


Fig. 1d

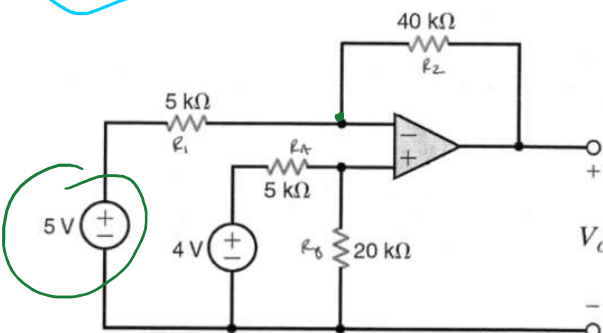


Fig. 1e



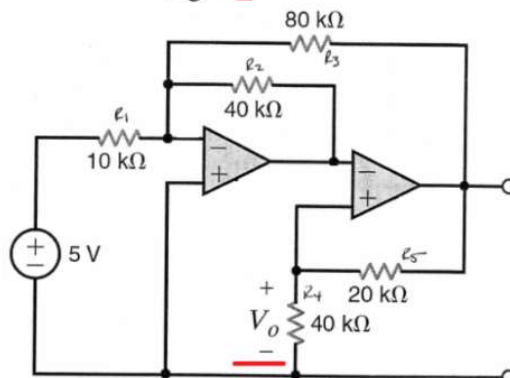


Fig. 1f

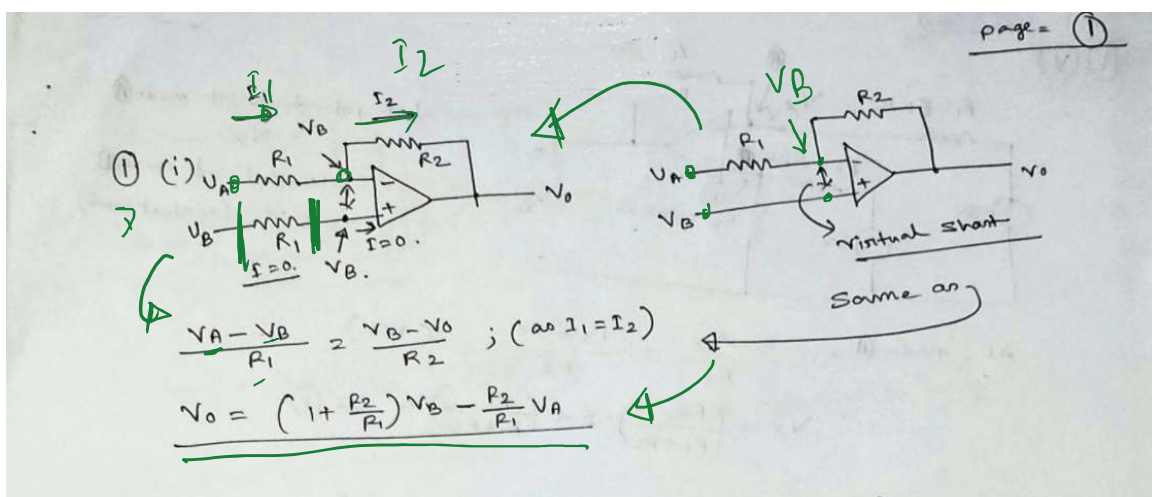
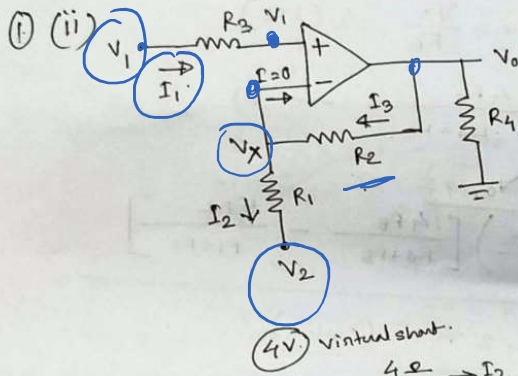
$$V_0 = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$



$$\infty, I_1 = I_2 = 0.$$

$$V_x = V_1 \text{ (virtual short).}$$


$$I_2 = I_3$$

$$\therefore \frac{V_x - V_2}{R_1} = \frac{V_0 - V_x}{R_2}$$

$$V_0 = \frac{V_x R_2 - V_2 R_2 + V_x R_1}{R_1}$$

$$\therefore V_0 = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$


① (iii)

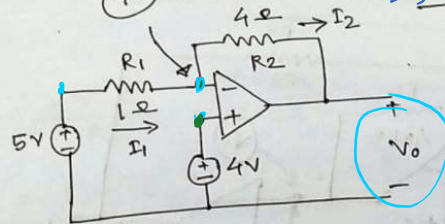

$$\infty, I_1 = I_2$$

$$\therefore \frac{5 - 4}{1} = \frac{4 - V_0}{4}$$

$$\therefore V_0 = 0$$

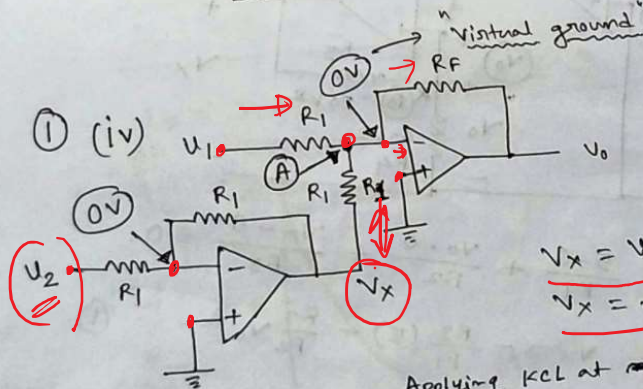

$$V_x = V_2 \times \left(-\frac{R_1}{R_1}\right)$$


$$V_x = -V_2$$

Applying KCL at node (A),

$$\frac{V_1 - 0}{R_1} + \frac{V_x - 0}{R_1} = \frac{0 - V_0}{R_F}$$

$$\therefore V_0 = -\frac{R_F}{R_1} (V_1 - V_2)$$

① (V)

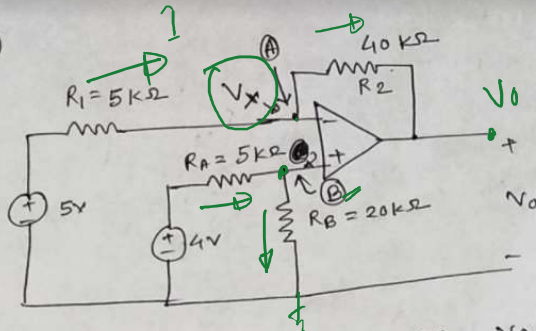

Let potential at node A
 $= V_x$
 So, potential at node B
 $= V_x$ (virtual short).

At, node (A), $\frac{5 - V_x}{R_1} = \frac{V_x - V_0}{R_2}$ (KCL)

$\therefore V_x = \left(\frac{R_2}{R_1 + R_2} \right) \cdot 5 + \left(\frac{R_1}{R_1 + R_2} \right) V_0$ — (1)


At, node (B), $\frac{4 - V_x}{R_A} = \frac{V_x}{R_B}$; (KCL)

$\therefore V_x = \frac{4 R_B}{R_A + R_B}$ — (2)

From, (1) & (2), Find V_0 .

$$V_0 = \left(\frac{R_1 + R_2}{R_1} \right) \left[\frac{4 R_B}{R_A + R_B} - \frac{5 R_2}{R_1 + R_2} \right]$$

$V_0 = -11.2 \text{ V.}$ (value).

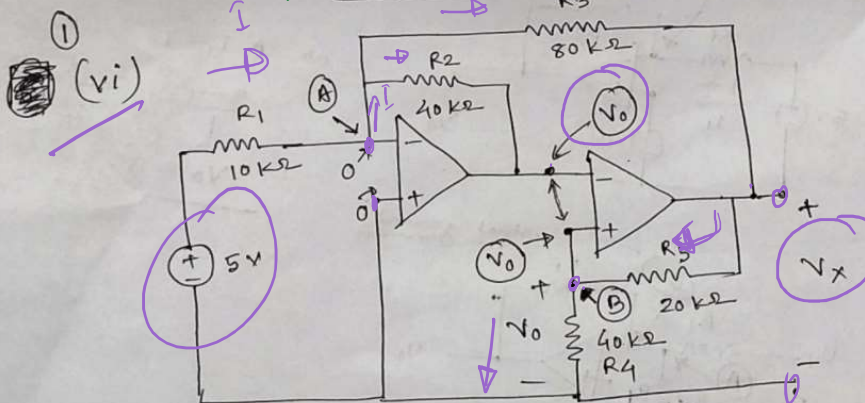

At node (A), $\frac{5 - 0}{R_1} + \frac{V_0 - 0}{R_2} + \frac{V_x - 0}{R_3} = 0$.

$\therefore V_x = -\frac{R_3}{R_1} (5) - \frac{R_3}{R_2} V_0$ — (1)

At node (B), $\frac{V_0}{R_4} + \frac{V_0 - V_x}{R_5} = 0$.

$V_x = V_0 \left(1 + \frac{R_5}{R_4} \right)$ — (2)


From (1) and (2), find V_0 .

$V_0 = -11.43 \text{ V.}$

2. You have given a bunch of 10 kΩ resistors and an Op-Amp. Design a circuit that will produce the following output (V_0).

$V_0 = -2V_1 - 4V_2$

$V_0 = - (2V_1 + 4V_2)$

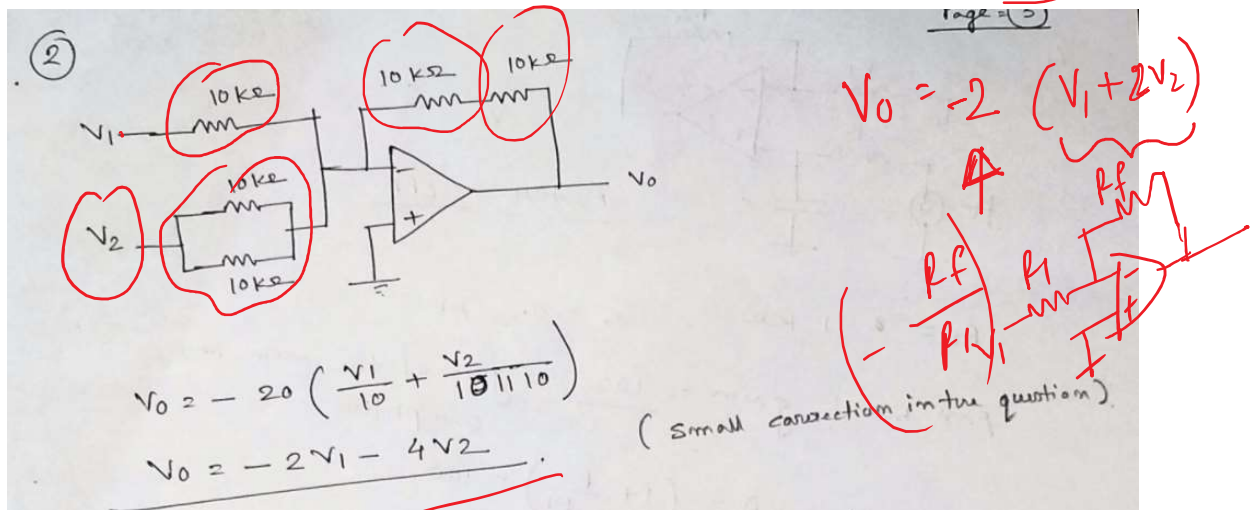

3. In the Op-Amp circuit shown in Fig. 2, find I_0 and I_S if $V_S = 1\text{ V}$ and $R_L = 1\text{ k}\Omega$. Also, plot the variation of I_0 with R_L .



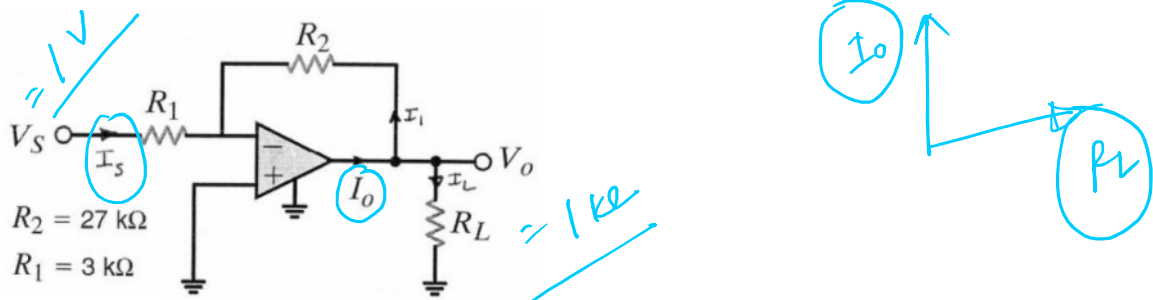


Fig. 2

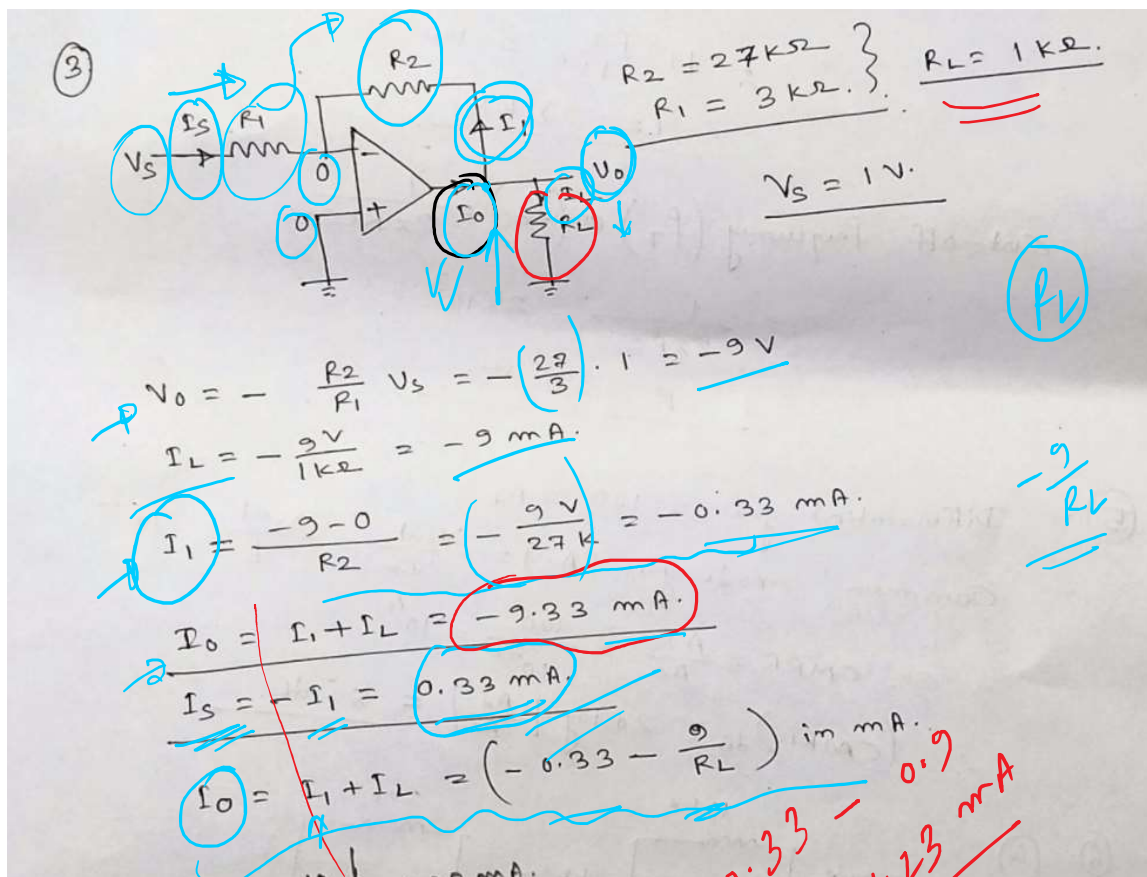

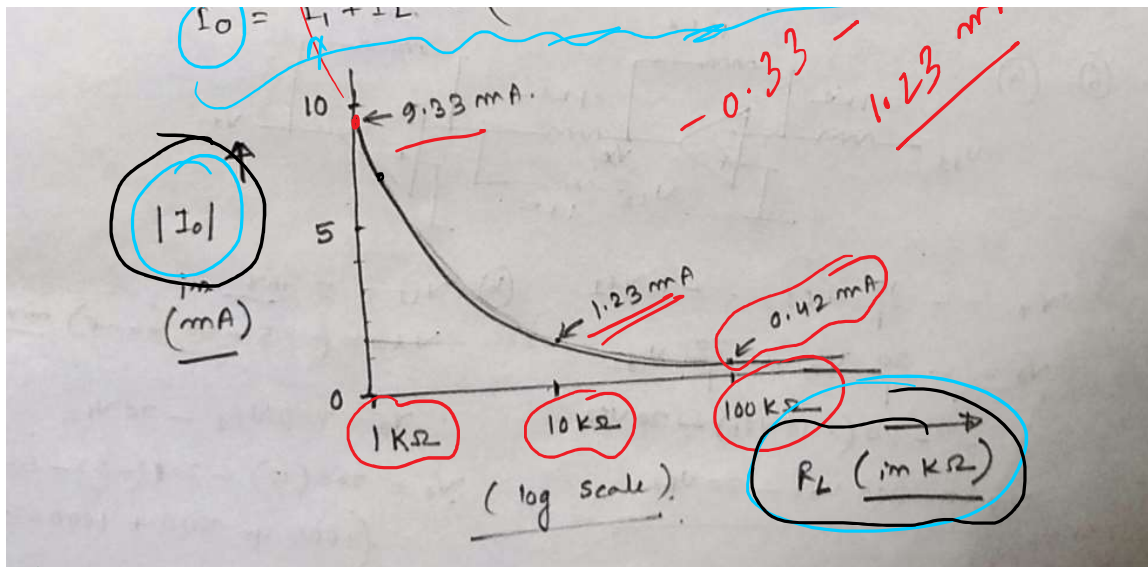

4. Fig. 3 shows a low-pass filter. Estimate the value of feedback resistor R_2 such that the 'pass-band' gain of the total circuit is 100. Given that $C = 0.2 \mu\text{F}$ and $R_1 = 1 \text{ k}\Omega$. Also calculate the value of resistor R for realizing a cut-off frequency of 2 kHz.

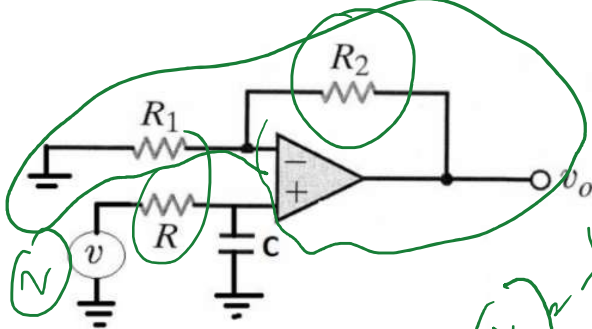


Fig. 3

④

Active 'LPF'

$R_1 = 1 \text{ k}\Omega$, $C = 0.2 \mu\text{F}$

pass-band gain = 100 = gain of the non-inverting amplifier.

$$A = \left(1 + \frac{R_2}{R_1}\right) = 100$$

$$\therefore 1 + \frac{R_2}{1 \text{ k}\Omega} = 100$$

$$\therefore R_2 = 99 \text{ k}\Omega$$

Cut-off frequency (f_T) or (f_c) = $\frac{1}{2\pi RC}$


$$\therefore \frac{1}{2\pi RC} = 2 \times 10^3$$

$$\frac{1}{2\pi RC} = 2 \times 10^3$$


$$\therefore R = 398 \Omega$$

5. For an Op-Amp, the differential gain (A_d) is 100. When 1 V is applied (common) to both the inputs, the output voltage measured is 0.01 V. Calculate the CMRR of the Op-Amp in dB.

⑤ Differential gain = 100 $\therefore A_d$
Common mode gain (A_c) = $\frac{V_{out}}{V_{in}} = \frac{0.01}{1} = 10^{-2}$
 \therefore So, CMRR = $\frac{A_d}{A_c} = \frac{100}{10^{-2}} = 10^4$
 $\therefore (CMRR)_{dB} = 20 \log \left| \frac{A_d}{A_c} \right| = 80 \text{ dB}$

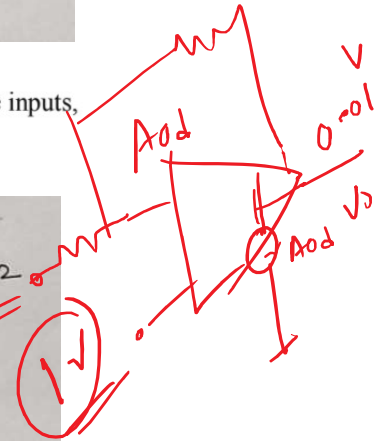

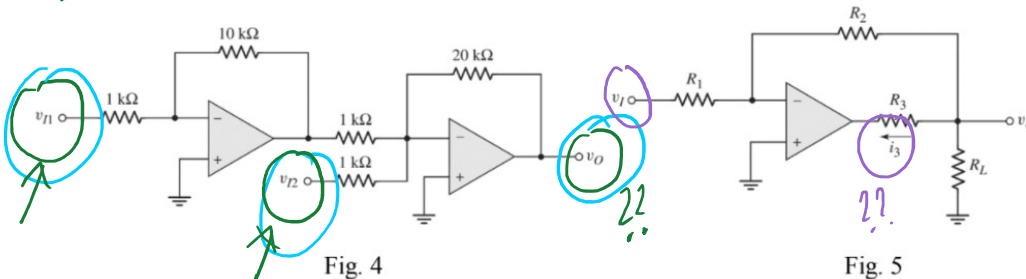6. Consider the circuit in Fig. 4, (a) Derive the expression for the output voltage v_o in terms of v_{i1} and v_{i2} . (b) Determine v_o for $v_{i1} = +5 \text{ mV}$ and $v_{i2} = (-25 - 50 \sin \omega t) \text{ mV}$.



$$V_o = -\frac{20}{R_1} V_{i1} - \frac{20}{R_2} V_{i2}$$

7. In the circuit shown in Fig. 5, derive the expression for i_3 in terms of v_i .


⑥ (a) $V_x = -\frac{10}{1} V_{i1} = -10 V_{i1}$
 $V_o = -\frac{20}{1} V_x - \frac{20}{1} V_{i2}$
 $= -20(-10 V_{i1}) - 20 V_{i2}$
 $\therefore V_o = 200 V_{i1} - 20 V_{i2}$
(b) $V_{i1} = 5 \text{ mV}$
 $V_{i2} = (-25 - 50 \sin \omega t) \text{ mV}$
 $\therefore V_o = 200 V_{i1} - 20 V_{i2}$
 $V_o = 200(5) - 20(-25 - 50 \sin \omega t)$
 $= (1000 + 500 + 1000 \sin \omega t) \text{ mV}$
 $V_o = (1.5 + \sin \omega t) \text{ V}$

$$V_o = \frac{20}{1} (V_{i1} + V_{i2})$$

$$V_o = -20(-10 V_{i1}) - 20 V_{i2}$$

$$V_o = 200 V_{i1} - 20 V_{i2}$$

$$V_o = -200 V_{i1} - 20 V_{i2}$$

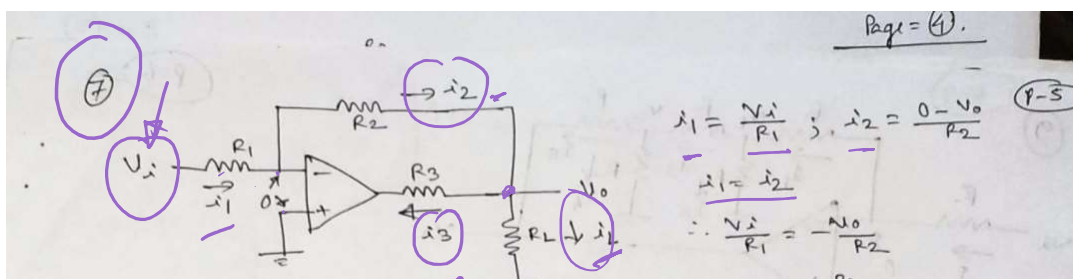

Handwritten notes and equations:

$$\frac{V_i}{R_1} = -\frac{V_o}{R_2}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_i$$

21

$$i_L = \frac{V_o}{R_L}$$

again,

$$i_2 = i_3 + i_L$$




$$\therefore \frac{V_i}{R_1} = i_3 + \frac{V_o}{R_L}$$

$$\therefore \frac{V_i}{R_1} = i_3 - \frac{R_2}{R_1 R_L} V_i$$

$$\therefore i_3 = \frac{V_i}{R_1} \left(1 + \frac{R_2}{R_L} \right)$$

20mA

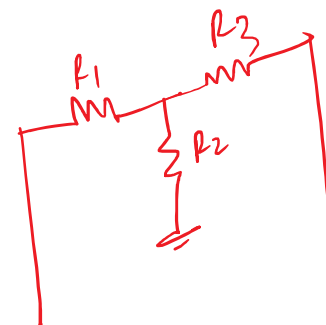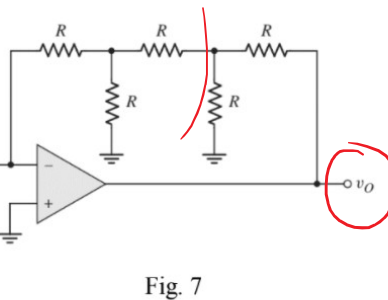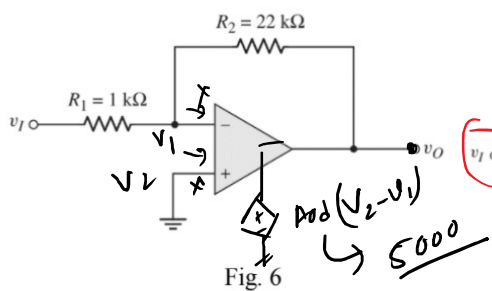8. Consider the circuit shown in Fig. 6. (a) Determine the ideal voltage gain. (b) Find the actual gain if the open-loop gain (A_{od}) of the op-amp is $A_{od} = 5 \times 10^3$. (c) Determine the required value of A_{od} in order that the actual voltage gain be within 0.2 percent of the ideal value.



9. For the inverting op-amp amplifier shown in Fig. 7, determine the gain $A_v = v_o/v_i$.

8

(a) Considering the op-amp as ideal, the gain is $= -\frac{R_2}{R_1} = -\frac{22}{1} = -22$

(b) Actual gain $= -\frac{R_2}{R_1} \times \frac{1}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1} \right)}$; [we have derive this in the class]

Where, A_{od} = open-loop gain.

$$= -22 \times \frac{1}{1 + \frac{1}{5 \times 10^3} (1 + 22)}$$

$$= -21.9$$

(c) Gain $= -22 \pm 0.2\% = -22 \pm 0.044 = -21.956$ ✓

$$\therefore -21.956 = -22 \times \frac{1}{1 + \frac{1}{A_{od}} \times 23}$$

$$\therefore \frac{23}{A_{od}} = 1.002 - 1$$

$$\therefore A_{od} = 11.4 \times 10^3$$

P-6

9

$$I = \frac{V_1 - 0}{R} = \frac{V_1}{R} = I_1 \quad \therefore V_1 = 0 - I_1 R$$

$$V_1 = -\frac{V_1}{R} \times R = -V_1$$

$$\therefore I_2 = \frac{V_1}{R} = -\frac{V_1}{R} \quad ; \quad \text{again, } I_1 = I_2 + I_3$$

$$\therefore I_3 = I_1 - I_2 = \frac{V_1}{R} - \left(-\frac{V_1}{R}\right)$$

$$I_3 = \frac{2V_1}{R}$$

$$\therefore V_2 = V_1 - I_3 R = -V_1 - \frac{2V_1}{R} \times R$$

$$\therefore V_2 = -3V_1$$

$$\text{So, } I_4 = \frac{V_2}{R} = -\frac{3V_1}{R}$$

$$I_5 = I_3 - I_4 = \frac{2V_1}{R} - \left(-\frac{3V_1}{R}\right) = \frac{5V_1}{R}$$

$$V_0 = V_2 - I_5 R = -3V_1 - \frac{5V_1}{R} \cdot R = -8V_1$$

$$\therefore \frac{V_0}{V_1} = -8 = A_v$$

10. The circuit shown in Fig. 8 is a first-order high-pass active filter. Determine how the gain of this circuit [$A_v = v_o/v_i$] is dependent on frequency i.e. find the voltage transfer function.

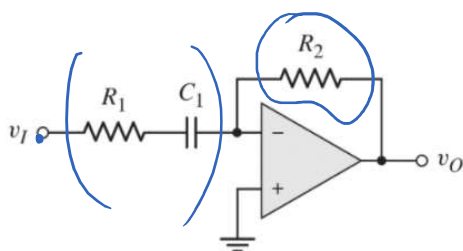


Fig. 8


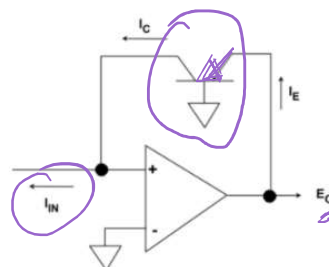



Fig. 9

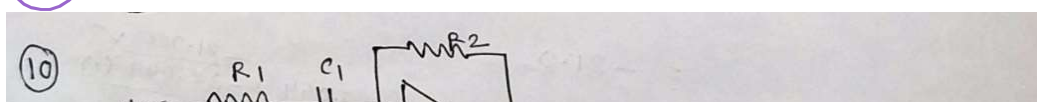11. In Fig. 9, show that $E_0 = \frac{kT}{q} \ln\left(\frac{I_{IN}}{I_{ES}}\right)$, where, I_{ES} is the reverse saturation current.

$$I_E = I_{ES} \exp\left(\frac{V_{BE}}{V_T}\right)$$



10

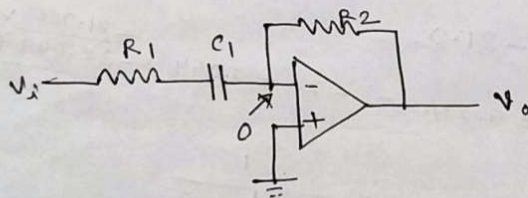


Non-inverting amplifier, gain $= \frac{V_o}{V_i} = - \frac{Z_2}{Z_1}$

$$= - \frac{R_2}{R_1 + \frac{1}{j\omega C_1}}$$

$$\Rightarrow \text{Gain} = - \frac{R_2 (j\omega C_1)}{R_1 j\omega C_1 + 1}$$

$\frac{\text{Gain}}{2}$

11

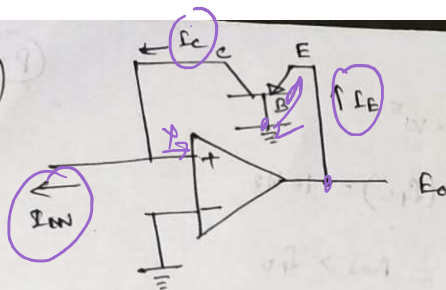

$$V_{EB} = E_0$$

$$I_E \approx I_{ES} \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$I_E \approx I_C \quad (\beta \text{ very high})$$

$$\therefore I_C = I_{IN}$$

$$\therefore I_{IN} = I_{ES} \exp\left(\frac{V_{EB}}{V_T}\right)$$

$$\left(\frac{I_{IN}}{I_{ES}}\right) = \exp\left(\frac{E_0}{V_T}\right)$$

$$\therefore E_0 = \frac{K_T}{q} \ln\left(\frac{I_{IN}}{I_{ES}}\right); \left[V_T = \frac{K_T}{q}\right]$$

12. If an op-amp has a slew-rate of $5 \text{ V}/\mu\text{s}$, find the full-power bandwidth for a peak output voltage of (a) 5 V , (b) 1.5 V , and (c) 0.4 V

12

$$\text{Full power bandwidth (FPBW)} = \frac{SR}{2\pi V_{o,max}}$$

SR = Slew rate

$V_{o,max}$ = peak output voltage

$$(a) \text{ FPBW} = \frac{5 \text{ V}/\mu\text{s}}{2\pi (5)} = \frac{5 \times 10^6 \text{ V/s}}{2\pi \times 5} = 159.2 \text{ kHz}$$

$$(b) \text{ FPBW} = 530.78 \text{ kHz}$$

$$(c) \text{ FPBW} = 1.99 \text{ MHz}$$

13. An amplifier system is to be designed to provide an undistorted 10 V peak sinusoidal signal at a frequency of $f = 12 \text{ kHz}$. Determine the minimum slew rate required for the amplifier.

13. An amplifier system is to be designed to provide an undistorted 10 V peak sinusoidal signal at a frequency of $f = 12 \text{ kHz}$. Determine the minimum slew rate required for the amplifier.

⑬ output peak = 10 V, max. frequency = 12 kHz.
 $\therefore \text{FPBW} = 12 \text{ kHz}$
 If the max. operating freq. is limited by the slew rate, then

$$\text{FPBW} = \frac{\text{SR}}{2\pi V_{\text{omax}}}$$

$$\therefore \text{SR} = \text{FPBW} \times 2\pi V_{\text{omax}}$$

$$= 12 \times 10^3 \times 2\pi \times 10$$

 $\text{SR} = 0.75 \text{ V}/\mu\text{s}$

14. An audio amplifier system is to use an op-amp with an open-loop gain of $A_{\text{od}} = 2 \times 10^5$ and a dominant-pole frequency of 10 Hz. The maximum closed-loop gain for the audio amplifier is 100. Determine the closed loop bandwidth of the amplifier.

⑭ open-loop gain (A_{od}) = 2×10^5
 Dominant pole frequency (f_{PD}) = 10 Hz.
 $\therefore \text{unity-gain bandwidth} = A_{\text{od}} \times f_{\text{PD}}$

$$= 2 \times 10^6$$

 Closed loop gain (A_{cd}) = 100
 $\therefore \text{so, closed loop frequency} = \frac{2 \times 10^6}{100} = 2 \times 10^4$

$$= 20 \text{ kHz}$$

15. For Fig. 10, neatly sketch the output voltage V_0 when V_{in} is a sine wave of amplitude 2 V (zero to peak). Consider the op-amp as ideal and zero voltage drop across the diode in forward bias.

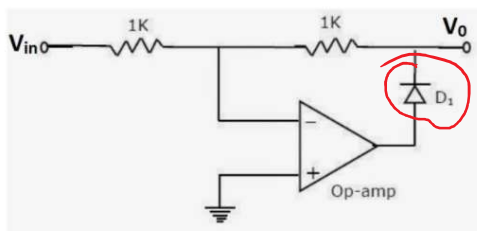


Fig. 10

