

## STUDIES ON SMALL SIGNAL CE AMPLIFIER:

**OBJECTIVE:**

To study small signal CE Amplifiers.

**APPARATUS REQUIRED:**

- Printed circuit board.
- DC Power supply 12V.
- AC Signal generator
- Connecting wires
- Cathode Ray oscilloscope.
- Multimeter.

**MEASUREMENT OF DC CONDITIONS:**

The following experimental values of resistors are measured using multimeter:

$$R_X \rightarrow 1.05\text{ k}\Omega$$

$$R_2 \rightarrow 4.67\text{ k}\Omega$$

$$R_{A1} \rightarrow 47.1\text{ k}\Omega$$

$$R_{E2} \rightarrow 357\Omega$$

$$R_{E1} \rightarrow 359\Omega$$

$$R_c \rightarrow 6.85\text{ k}\Omega$$

$$R_L \rightarrow 1.024\text{ k}\Omega$$



Teacher's Signature : \_\_\_\_\_

+12V  $V_{cc}$  is applied to amplifier circuit from dc power supply and the values of  $V_B$ ,  $V_c$  and  $V_E$  are measured:

$$\left. \begin{array}{l} V_B : 1.019V \\ V_c : 7.57V \\ V_E : 0.441V \end{array} \right\} \text{with respect to ground.}$$

$$\text{Thus } V_{BE} = V_B - V_E = 0.578V$$

$$V_{CE} = V_C - V_E = 7.129V.$$

$$I_C = \frac{V_{IN} - V_c}{R_C} = \frac{12 - 7.57}{6.8 \times 10^3} = 0.65 \text{ mA.}$$

writing Kirchoff's loop law;

$$V_B - V_{BE} - I_E (R_{E1} + R_{E2}) = 0.$$

$$\Rightarrow I_E = \left( \frac{V_B - V_{BE}}{R_{E1} + R_{E2}} \right) = 0.668 \text{ mA.}$$

Readings of this experiment lead us to following conclusions:


$\rightarrow$  Region collector junction is reverse biased and emitter is forward biased.

$\rightarrow I_B > 0$  and  $V_{CE} > 0.5V$  and thus, it is in active region.  
and Q-point is suitably located.



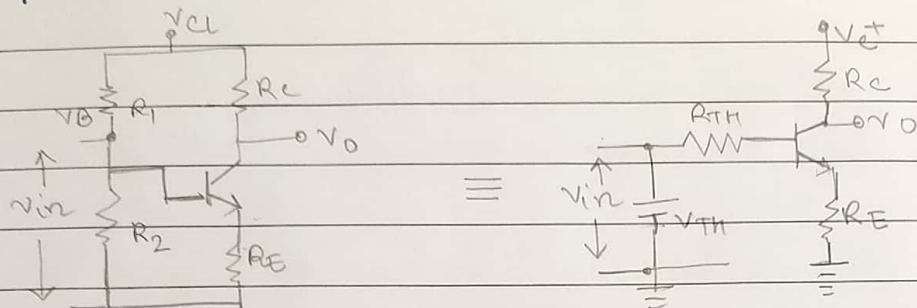**THEORY:**

We also emphasize the use of transistor biasing in this experiment with resistance divider or  $V$ -divider bias.



This circuit stabilizes the Q-point of DC equivalent circuit by stabilizing  $\beta$  for significant changes in  $V_{in}$ .

The capacitors act as open circuit for DC equivalent circuit and hence has no effect on  $I_{DQ}$ . However for AC circuit and significant values of  $\omega$  (it acts as high pass filter), it can be treated as short the circuit ( $X_C \ll R_E, R_C, R_B$ ) and trace amounts for stability of AC circuit.

Next we have seen Miller effect. Miller equation can be used to provide equivalent circuit formed due to application of  $C_{cb}$ :

In our experiment,  $Z$  is  $v_i$   $v_o$ .

$\times C_{cb}$ . Using miller equation, we shall have:  $v_i^o$   $v_o$   $(1+A)c$   $(1+\frac{1}{A})c$

Lastly we have found out  $R_i$  and  $R_o$  for the transistor circuit:  $r_i = \frac{\beta V_T}{I_{CQ}}$

$$r_o = \frac{V_A}{I_{CQ}} \quad (\text{A} \rightarrow \text{Early voltage})$$

Teacher's Signature : \_\_\_\_\_

**THEORY :**

In this experiment, we are working with BJT with ~~in~~ amplifier configuration.

BJT stands for Bipolar Junction transistor. There can be three types of BJTs - common Base (CB), Common Emitter (CE) and common collector.

In common emitter,  $V_i$  is applied across Base and emitter. Thus,

$$I_B = \frac{V_i - V_{BE(on)}}{R_B}$$



also, it is constant for a given  $V_{BE}$ .

The current in  $I_B$  is due to movement of electrons. They cross the B-E depletion layer and reach the Base. The electrons then move across the p-n junction in BC by diffusion while some of them recombine giving rise to  $I_B$ .

The relations are:

$$I_C = \alpha I_E \quad (\alpha \text{ is common base gain } \approx 1)$$




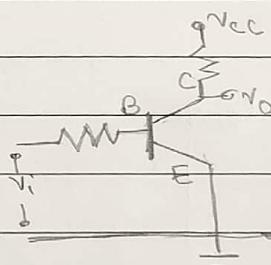
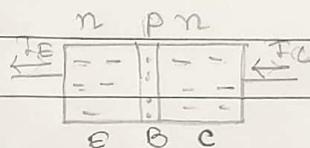
$$I_C = \beta I_B \quad (\beta \text{ is common emitter gain } \gg 1)$$



The circuit has two equivalent circuits - DC equivalent and AC equivalent. Addition of  $R_E$  decreases  $I_B$  and thus gain, however it stabilizes the circuit to prevent thermal run-off.

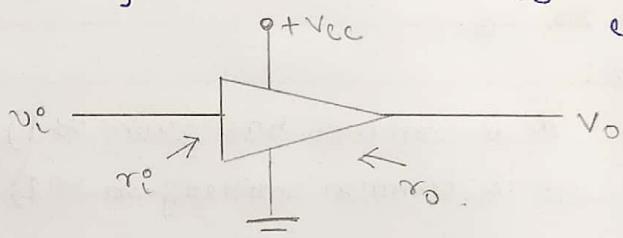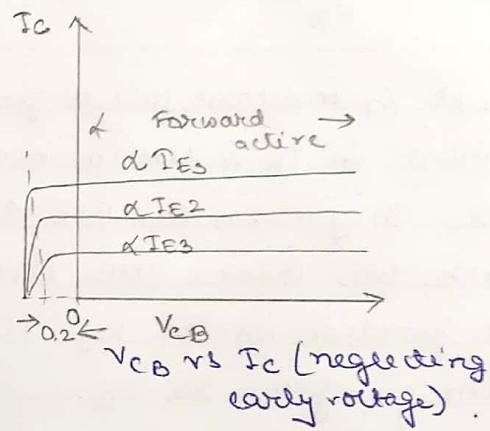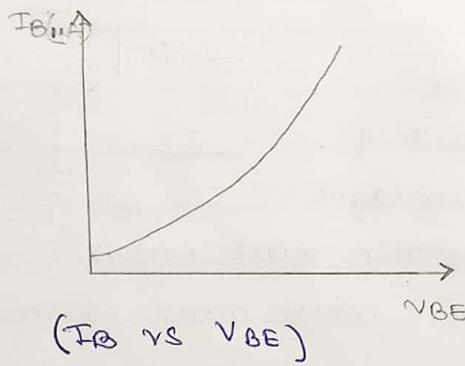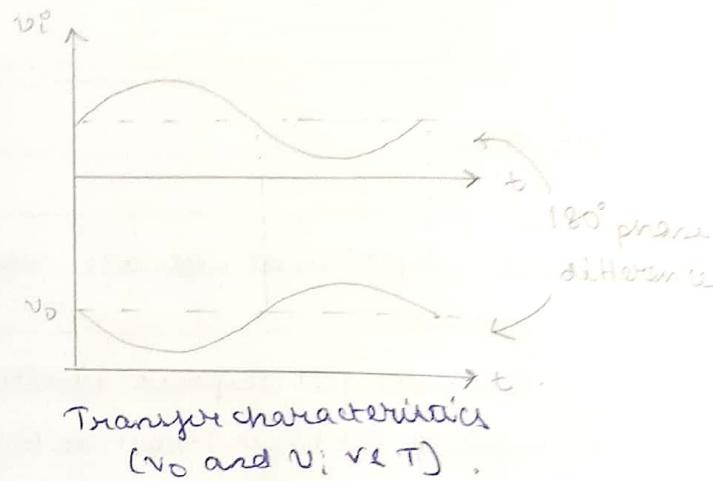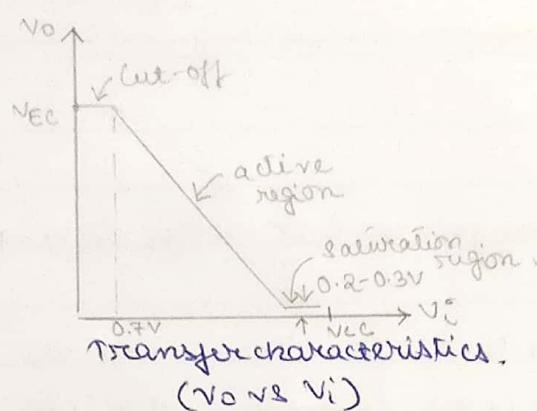Capacitors are used in various experiments in this circuit to prevent dc offset voltages in the source currents, without changing the Q-points.





(input and output resistance)



### MEASUREMENT OF SIGNAL HANDLING CAPACITY:

$R_x$  is shorted by connecting 1-1' and capacitor is connected across  $R_{F2}$  by joining 2-2'.

case 1:

$r_2 = \infty$  (no load).

Frequency: 3.962 kHz.


SL. NO.	$V_{in}$ (mV)	$V_{out}$ (V)	$(\text{Gain } V_o/V_i)$
1.	100	1.8	18
2.	120	2.2	18.33
3.	140	2.6	18.57
4.	250	3.8	17.75
5.	350	6.3	18.00
6.	500	8.6	17.2
7.	590	9.6	16.27
8.	670	10.4	15.5
9.	1000	10.4	10.4.

$V_{sm}$  is the point where clipping starts. The  $V_{sm}$  is thus concluded to be at 580mV of  $V_{in}$ . The output voltage is undistorted till this point.


Thus,  $V_{sm} = 580\text{mV}$ .



Teacher's Signature : \_\_\_\_\_

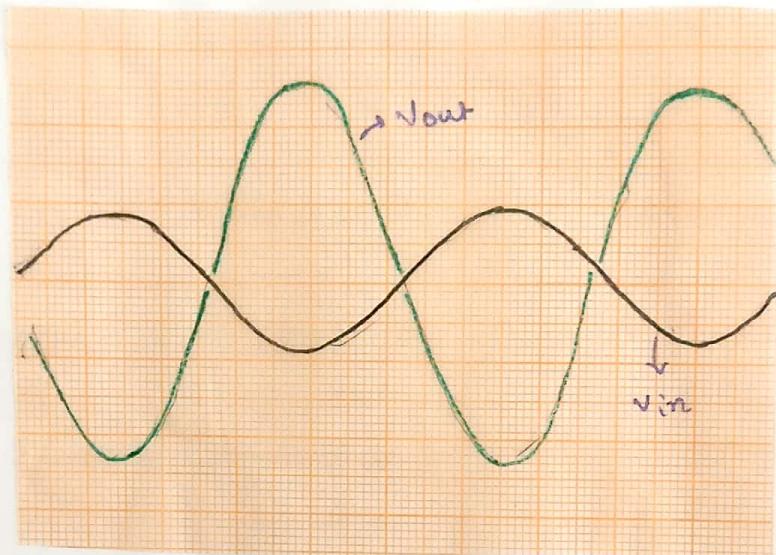

$v_i$  below  $v_{sm}$

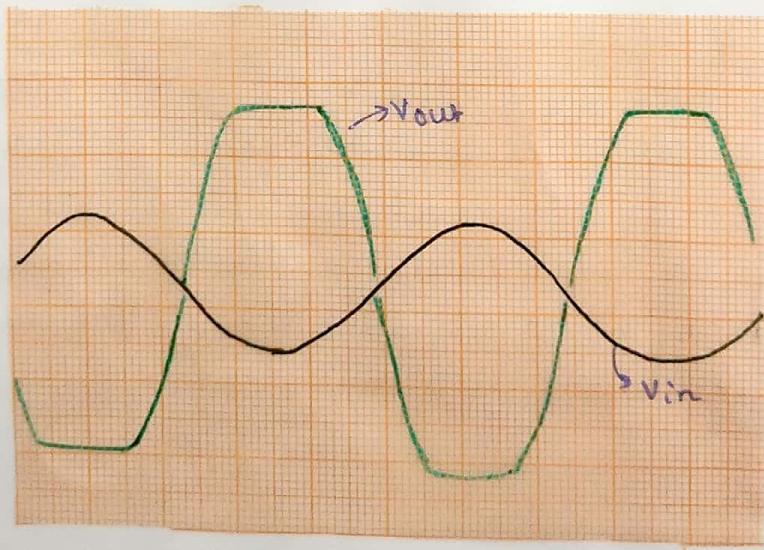

$v_i$  Above  $v_{sm}$  (saturated)



(iii)  $R_L$  connected case:

$$R_L = 1\text{ k}\Omega$$

$$f \rightarrow 4\text{ kHz}$$

SL. NO.	$V_{in}(\text{mV})$	$V_{out}(\text{V})$	Gain ( $V_o/V_i$ )
1	100	.24	2.4
2	160	.38	2.375
3	250	.60	2.4
4	350	.84	2.4
5	500	1.14	2.28
6	540	1.2	2.22
7	880	1.5	1.87
8	1000	1.7	1.7

Similar to previous case, we note the value of  $V_m$ : 540mV.  
 We also notice that  $V_m$  is approximately same for both the cases.

Gain decreased due to connection of  $R_L$ .



Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

**FREQUENCY RESPONSE :** $V_{in} = 0.5V$  (maintained constant).  $R_L = 1k\Omega$ 

SL.NO.	Frequency(Hz)	$V_{out}(V)$	$20 \log(V_o/V_i)$
1	117.2 10.38	0.804	4.02
2	20.03	1.04	6.36
3	35.31	1.10	6.85
4	49.3	1.12	7.00
5	100 117.2	1.12	7.00
6	117.2 400	1.12	7.00
7	150K	1.10	6.85
8	201K	1.08	6.69
9	268.7K	1.06	6.53
10	349.4K	1.04	6.36
11	383.3K	1.00	6.02
12	526 K	0.96	5.66
13	590 K	0.92	5.29
14	651 K	0.88	4.91
15	736 K	0.84	4.50
16	804 K	0.80	4.08
17	911 K	0.76	3.64
18	980 K	0.72	3.17
19	1084 K	0.68	2.67



Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

(iii)  $V_{in} = 0.5 \text{ V}$ .  $R_L = \infty$  (no load)

Sl. No.	Frequency (Hz)	$V_{out}$ (V)	$20 \log(V_{out}/V_{in})$ dB
1	10.33	6.8	2.67 22.67
2	20	8	4.08 24.08
3	35	8.4	24.5
4	42.6	8.6	24.7
5	319	8.6	24.7
6	26.27K	8.4	24.08 24.5
7	54.5K	8.0	24.08
8	82.5K	7.6	23.63
9	104.2K	7.2	23.17
10	128.8K	6.8	22.6
11	148K	6.4	22.14
12	173.5K	6	21.58
13	221.3K	5.2	20.34
14	279.4K	4.4	18.89
15	324.4K	4	18.06
16	386K	3.4	16.55
17	440K	3	15.56
18	567K	2.4	13.62
19	681K	2	12.04
20	846K	1.6	10.1
21	1000K	1.3	8.29

✓

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

(iii) Effect of CE :

$$a) R_L = 1 \text{ k}\Omega$$

$$V_{in} = 0.5V$$

SL. NO.	Frequencies	$V_{out}$ (V)	$20 \log(V_o/V_i)$ db
1	.5	0.42	2.114, -1.514
2	10	0.48	-0.354
3	20	0.55	0.828
4	100	0.58	1.289
5	20K	0.57	1.138
6	300K	0.56	0.984
7	500K	0.55	0.828
8	800K	0.52	0.341
9	1M	0.50	0
10	2M	0.37	-2.615
11	3M	0.28	-5.036

✓

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

by  $R_{E1}$  and  $R_{E2}$  fully bypassed:

Sl. No.	Frequency	Vout (V)	$20 \log(V_o/V_i) \text{ dB}$
1	10.3	1.9	11.59
2	19.2	2	12.04
3	35.15	3.8	17.61
4	54	4.2	18.48
5	76	4.4	18.89
6	100	4.5	19.08
7	167	4.6	19.27
8	292.4	4.7	19.46
9	932	4.8	19.64
10	14.09K	4.6	19.27
11	31.45K	4.4	18.88
12	46K	4.3	18.48
13	64.3K	4	18.06
14	94.1K	3.8	17.61
15	178.3K	3.4	16.65
16	282.3K	3	15.56
17	383K	2.7	14.64
18	500K	2.2	12.86
19	730K	2	12.04
20	950K	1.8	11.12
21	1009K	1.8	11.12

✓

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

iii) Miller effect due to  $C_{ab}$ :

Disconnect 1-1' and 4-4' are connected:

$$V_{in} = 0.5V$$

SL.NO.	Frequency(Hz)	$V_{out}(V)$	$20 \log(V_o/V_i) \text{ db}$
1	9.47	0.72	3.167
2	14.91	0.86	4.71
3	21.58	0.88	4.91
4	35.41	0.82	5.29
5	51.1	0.94	5.48
6	61.8K	0.92	5.29
7	138.9K	0.88	4.91
8	198.6K	0.84	4.506
9	257.8K	0.8	4.08
10	351.4K	0.72	3.167
11	466K	0.64	2.14
12	503K	0.6	1.58
13	574K	0.56	0.98
14	707K	0.48	-0.35
15	920K	0.40	-1.93
16	1000K	0.36	-2.8



Teacher's Signature : \_\_\_\_\_

b) Terminals 4-4' are disconnected:

Sl. No.	Frequency	$V_{out}(V)$	$20 \log(V_o/V_i) \text{ dB}$
1	10.63	0.76	3.636
2	21.05	0.84	4.506
3	51.8	0.86	4.71
4	76.6	0.92	5.29
5	79.2	0.94	5.48
6	116.9	0.94	5.48
7	37.93K	0.92	5.29
8	240.2K	0.88	4.91
9	348.3K	0.84	4.506
10	412K	0.80	4.08
11	542K	0.78	3.636
12	632K	0.72	3.167
13	678K	0.68	2.67
14	761K	0.64	2.14
15	864K	0.6	1.58
16	931K	0.56	0.98
17	1002K	0.54	0.668

✓

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_

Page No. \_\_\_\_\_

**DISCUSSION:****MEASUREMENT OF INPUT RESISTANCE IN MID-FREQUENCY RANGE:**

$$V_{in} = 500 \text{ mV}$$

$$R_x = 1 \text{ k}\Omega$$

$$\text{Frequency} = 4 \text{ kHz}$$

$R_s (\Omega)$	$V_{out1o} (V)$	$V_{out1Rx} (V)$	$R_{in}$ $\frac{R_x \cdot V_{out1Rx}}{V_{out1o} - V_{out1Rx}} - R_s$
50 $\Omega$	3.2V	2.7V	5350 $\Omega$
600 $\Omega$	2.6V	2.24V	5560 $\Omega$

**MEASUREMENT OF OUTPUT RESISTANCE IN MID-FREQUENCY RANGE:**

$$V_{in} = 150 \text{ mV}$$

$$R_L = 1 \text{ k}\Omega$$

$$\text{frequency} = 4 \text{ kHz}$$

$R_s (\Omega)$	$V_{out1RL} (V)$	$V_{out1o}$	$R_{out}$ $\frac{R_L \cdot V_{out1o} - V_{out1RL}}{V_{out1RL}}$
50 $\Omega$	0.41V	3.2V	6805 $\Omega$
600 $\Omega$	0.39V	3.0V	6894 $\Omega$

✓

Teacher's Signature : \_\_\_\_\_

**DISCUSSION :**

Swastika Dutt  
(16CS10060)

In active region, BE is forward biased while BC is reverse biased. Thus suitable  $V_B$  is applied such that saturation level is not reached (less than  $V_{EM}$ ). Hence we achieve an amplified output voltage without deformation in signal waveform.

The capacitors used at input and output act as coupling capacitors and DC blocking capacitors. The offset DC voltage effect and sine voltage effects can be superposed on the circuit to find the net effect. Capacitor acts as open circuit for DC current and allows current to pass at high cut frequencies (high pass circuit filter). Suitable values of capacitors are used to reduce attenuation of input voltage. Again, this setting does not bring about change of DC quiescent point (i.e., maintains it at active region).

In signal handling experiment, we show the working of voltage divider. Thus,  $V_O$  reduced and gain ( $A$ ) =  $V_O/V_I$  reduced subsequently. However, bias stability of the circuit increased on account of voltage divider biasing.

In measurement of frequency response, voltage gain improved from 1.00 to 24.64db, alongside reduction in cutoff frequency as depicted in the results.

On the next part of the frequency response experiment, we use  $C_F$  as a bypass circuit for resistors  $R_E$  and  $R_{E2}$ .

Teacher's Signature : \_\_\_\_\_

Date \_\_\_\_\_

Expt. No. \_\_\_\_\_


Page No. \_\_\_\_\_

Reduction of resistance in path of input, increases  $\beta I_B$ , and subsequent increase in  $I_C (= \beta I_B)$ . Thus, saturation point is reached at a lesser  $V_i$ , transistor was becoming saturated. Also the voltage gain improved from max at 1.289 to max at 19.64 when  $R_{E1}$  &  $R_{E2}$  were bypassed.

(Base-emitter loop)

On the next part of the experiment, we consider Miller effect. This effect is observed due to presence or absence of  $C_{EB}$  in the circuit. This is also called feedback effect. The capacitive feedback from collector to base effectively multiplies  $\beta_{EB}$  with  $\beta$ . The amount of negative gain-reducing feedback is related to both current gain and amount of collector-base capacitance.

Then in the last part of the experiment we took mid-frequency range and calculated the  $\#$  input and output resistances in respective cases.

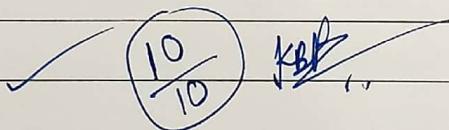 10/10 ✓ KBF

Teacher's Signature : \_\_\_\_\_

## Discussion:-

By Neha Ratreja

(16 CS 10013)

1. For BJT to work as an amplifier, it should operate in its active region where the configuration between base-emitter junction is in FB but base-collector junction is in Reverse Bias. We should have kept voltage quite below  $V_{cm}$ , i.e. the <sup>maximum input</sup> voltage for which the gain remains almost constant. This is called signal handling capacity.
  2. Observation of  $V_{cm}$  was obtained by voltage that initiates the distortion of LDO displayed output voltage curve. Voltage above  $V_{cm}$  leads the transistor to switch to saturation region where both junctions are in forward bias.
  3.  $R_1$  and  $R_2$  are providing voltage divider biasing which provides stability such that  $I_B \ll I_{R_2}$  which implies  $V_B$  almost constant.
  4.  $C_{C_2}$  capacitor was used to avoid change in O-point by the load because direct coupling without  $C$  leads to voltage divider b/w  $R_C$  and  $R_L$  whereas which leads to change in O-point.
- Direct coupled:  $V_E = V_{CC} \frac{R_L}{R_C + R_L}$  Capacitor-coupled:  $V_C = V_{CC} - I_C R_C$
5.  $C_{C_1}$  capacitor was similarly used to avoid formation of voltage divider by  $R_1$  and  $R_2 || R_S$  to limited involvement of only two resistors  $R_1$  and  $R_2$  to form voltage divider such that  $V_B = V_{CC} \frac{R_2}{R_1 + R_2}$  stays valid.

Teacher's Signature : \_\_\_\_\_

6. In measurement of frequency response, voltage gain improved from  $\pm 2\text{db}$  to  $24.64\text{ db}$  alongside reduction in cut-off frequency.
7.  $R_E$  and  $R_{E2}$  as emitter resistances are used to provide stability biasing stability, i-e, change in  $I_C$  is reduced by a factor of  $R_E$  but ~~red~~ increment in stability cost for the output voltage supplied.  $R_E$  are acting as feedback resistors (negative).
- 8 If  $V_{in}$  increases leading increment in  $I_C$  which leads to decrease in  $V_{CE}$  which lead to decrement in  $I_B$ <sup>due to  $R_E$</sup>  which leads to decrease in  $I_C$ . Thus, providing good-bias stability with reduced gain and less distortion in input waveform.
- 9  $C_B$  also act as feedback capacitor across base collector which is used to restrict the range of operation to lower frequencies. Stray capacitance between capacitor and base increase by Miller effects due to its high gain lowering the high frequency response of the device.
- 10 Increment in  $V_{in}$  resulting in increment in  $V_{RE}$  as  $I_B$  increases leading to reduced increase in  $V_B$  leading to avoid thermal runaway because increase in  $I_B$  to a large extent to heat up the transistor which will require more bias current to provide some bias voltage and

Teacher's Signature : \_\_\_\_\_

also as  $R_1 | R_2$  voltage divider is designed to provide the correct quiescent current through base to operate it in desired operation needs to get changed ~~as~~ leading to errors in output to a large extent.

✓  
  
10  
10  
kbf

Teacher's Signature : \_\_\_\_\_