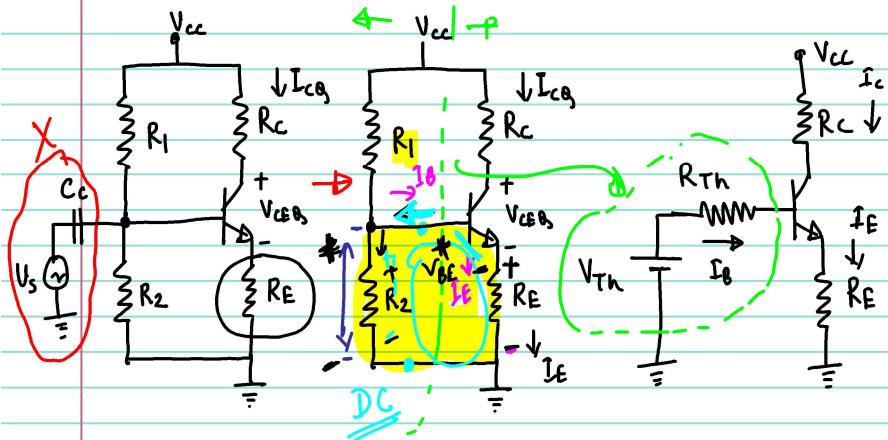


(i) Voltage divider biasing with emitter resistor:



$$V_{Th} = V_{cc} \cdot \frac{R_2}{R_1 + R_2} ; \quad R_{Th} = R_1 \parallel R_2$$

$$V_{Th} = I_B \cdot R_{Th} + V_{BE\text{ON}} + I_E R_E ; \quad I_E = (1+\beta) I_B$$

$$V_{Th} = \frac{I_B \cdot R_{Th} + V_{BE\text{ON}} + (1+\beta) I_B R_E}{=}$$

$$I_B = \frac{V_{Th} - V_{BE\text{ON}}}{R_{Th} + (1+\beta) R_E} ; \quad I_C = \beta I_B$$

$$I_C = \beta \times \frac{V_{Th} - V_{BE\text{ON}}}{R_{Th} + (1+\beta) R_E}$$

$$R_{Th} = R_1 \parallel R_2$$

$$R_{Th} \ll (1+\beta) R_E \quad 4)$$

$$I_C \approx \frac{\beta (V_{Th} - V_{BE\text{ON}})}{(1+\beta) R_E} ; \quad \underline{\underline{\beta \gg 1}} \quad \underline{\underline{1+\beta \approx \beta}}$$



$$I_C \approx \frac{V_{Th} - V_{BE\text{ON}}}{R_E} ; \quad \underline{\underline{I_C \text{ is independent of } \beta}}$$

$$R_{Th} \approx 10 \cdot \underline{\underline{R_E (1+\beta)}}$$

Lec-16

Basic BJT Amplifier:


Recd.

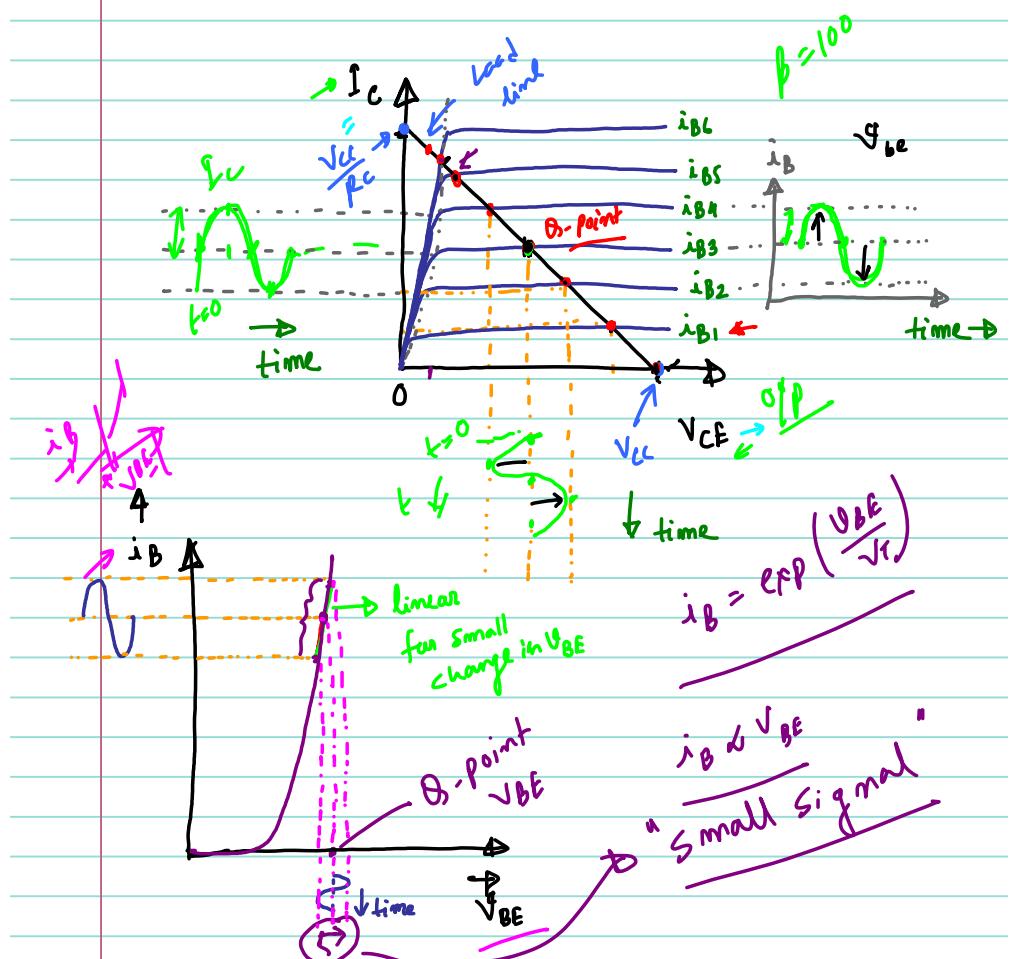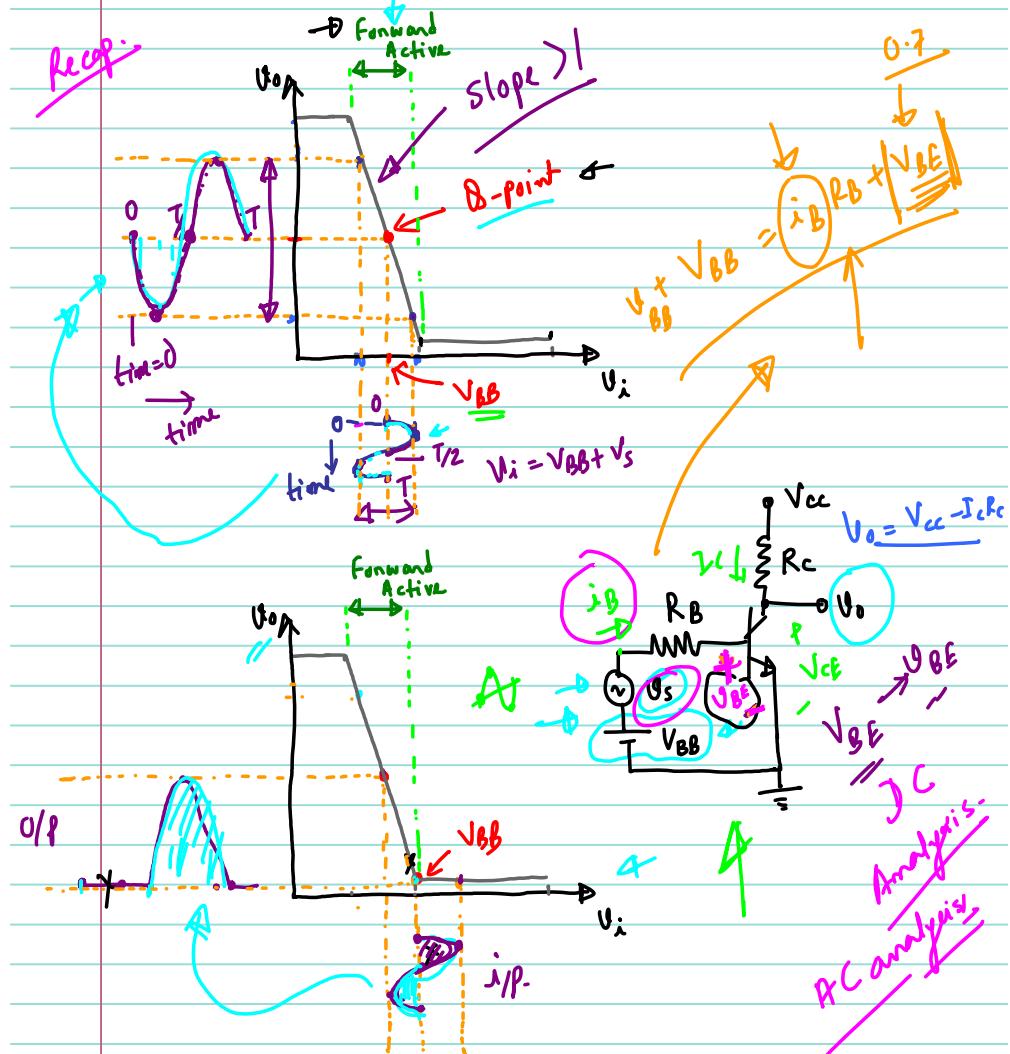

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$I_B = \frac{I_S}{\beta} \cdot \frac{I_C}{P}$$

Small Signal ??

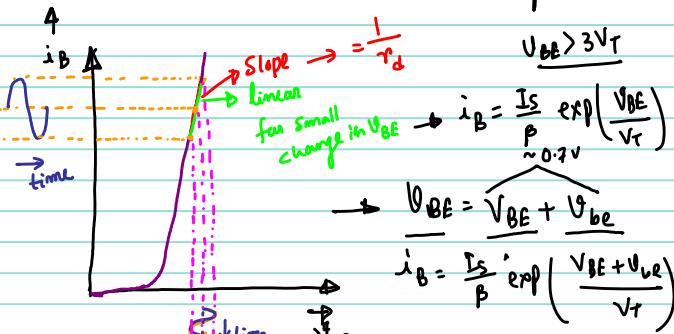

$$i_B = I_{B0} \cdot \exp\left(\frac{V_{be}}{V_T}\right)$$

$e^x = 1 + x + \frac{x^2}{2} + \frac{x^3}{6} + \dots$ if $x < 1$ then $i_B = I_{B0} \cdot \exp\left(\frac{V_{be}}{V_T}\right)$

$$i_B = I_{B0} \left[1 + \frac{V_{be}}{V_T} \right]; I_{B0} + i_B = I_{B0} + I_{B0} \cdot \frac{V_{be}}{V_T}$$

$V_{be} \ll V_T$ $\rightarrow V_{be} < V_T$ (condition)
 $i_B = I_{B0} \cdot \frac{V_{be}}{V_T}; i_B \propto V_{be}$

$$V_T = 26 \text{ mV at } 300K \rightarrow V_{be} < 10 \text{ mV}$$

$$i_B \propto V_{be}, V_{be} \propto V_s, i_B \propto V_s$$

$$i_C = \beta i_B, V_o = V_{cc} - i_C R_C$$

$$e^x = 1 + x + \frac{x^2}{2} + \frac{x^3}{6} + \dots$$

$$x = \frac{V_{be}}{V_T} = \frac{V_m \sin \omega t}{V_T}$$

$$\sin \omega t = \frac{1}{2} [1 - \cos 2\omega t]$$

$$= \frac{1}{2} [1 - \sin(2\omega t + 90^\circ)]$$

$$e^x = 1 + \frac{V_m \sin \omega t}{V_T} + \frac{V_m^2 \sin^2 \omega t}{2V_T^2} + \left(\frac{V_m}{V_T}\right)^3 \frac{\sin^3 \omega t}{6} + \dots$$

$$+ \left(\frac{V_m}{V_T}\right)^3 \times \frac{1}{6} \times \frac{1}{4} [3 \sin \omega t - \sin 3\omega t]$$


$$= \left[1 + \frac{1}{4} \left(\frac{V_m}{V_T} \right)^2 \right] + \left(\frac{V_m}{V_T} \left[1 + \frac{1}{8} \left(\frac{V_m}{V_T} \right)^2 \right] \right) \sin \omega t$$

$$- \frac{1}{4} \left(\frac{V_m}{V_T} \right)^2 \cdot \sin(2\omega t + 90^\circ) - \frac{1}{24} \left(\frac{V_m}{V_T} \right)^3 \sin 3\omega t + \dots$$

Harmonics \rightarrow Harmonic distortion

Total Harmonic Distortion (THD) %
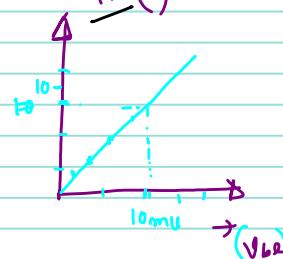
$$= \frac{\sqrt{\sum_{n=2}^m V_n^2}}{V_1} \times 100\%$$



Notations used in BJT Amplifier Section:



Total instantaneous value $\rightarrow i_B, i_C, V_{BE}, V_{CE}$

DC values $\rightarrow I_B, I_C, V_{BE}, V_{CE}$

Instantaneous AC value $\rightarrow i_B, i_C, V_{BE}, V_{CE}$

$$\left\{ \begin{array}{l} i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \\ i_C = \beta i_B \end{array} \right.$$

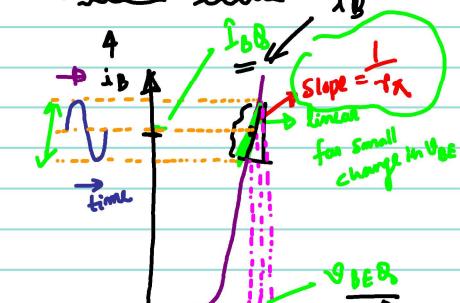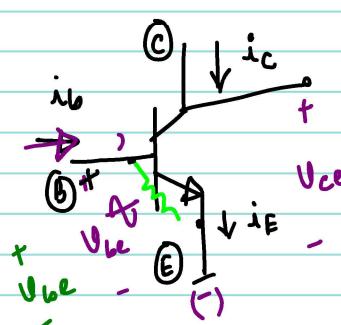Small Signal hybrid- π equivalent circuit:



$$\frac{i_v}{V_{be}} = \frac{1}{r_\pi} \quad ; \quad V_{be} = i_v r_\pi$$

r_π = diffusion resistance on

$$\rightarrow i_B = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$at B.P.t = \frac{I_{BS}}{\sqrt{T}} = \frac{I_{CS}}{\beta \sqrt{T}}$$

F.W.B. base-emitter resistance

$$\frac{1}{r_\pi} = \frac{\partial i_B}{\partial V_{BE}} = \frac{I_S}{\beta \sqrt{T}}$$

$$\left\{ \begin{array}{l} -1 = \frac{I_{BS}}{\sqrt{T}} = \frac{I_D}{\sqrt{T}} \\ r_\pi = \frac{V_L}{I_D} \end{array} \right.$$

$$\rightarrow \Delta i_C = \left. \frac{\partial i_C}{\partial V_{BE}} \right|_{B.P.t} \cdot \Delta V_{BE}$$


$$i_C = \left(\left. \frac{\partial i_C}{\partial V_{BE}} \right|_{B.P.t} \right) (V_{be})$$

$$\left. \frac{\partial i_C}{\partial V_{BE}} \right|_{B.P.t} = \frac{\partial}{\partial V_{BE}} I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$\left. \frac{\partial i_C}{\partial V_{BE}} \right|_{B.P.t} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_{CS}}{\sqrt{T}}$$


transconductance (g_m)
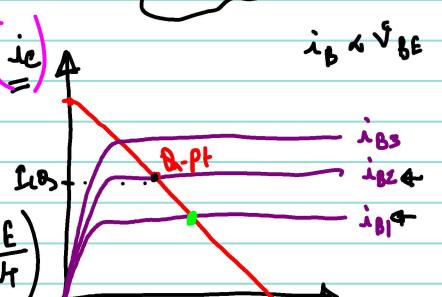
$$g_m = \left(\frac{I_{CS}}{V_T} \right)$$




$$\left[\begin{array}{l} \Delta i_C \rightarrow i_C \\ g_m V_{be} \quad (\text{small}) \end{array} \right]$$

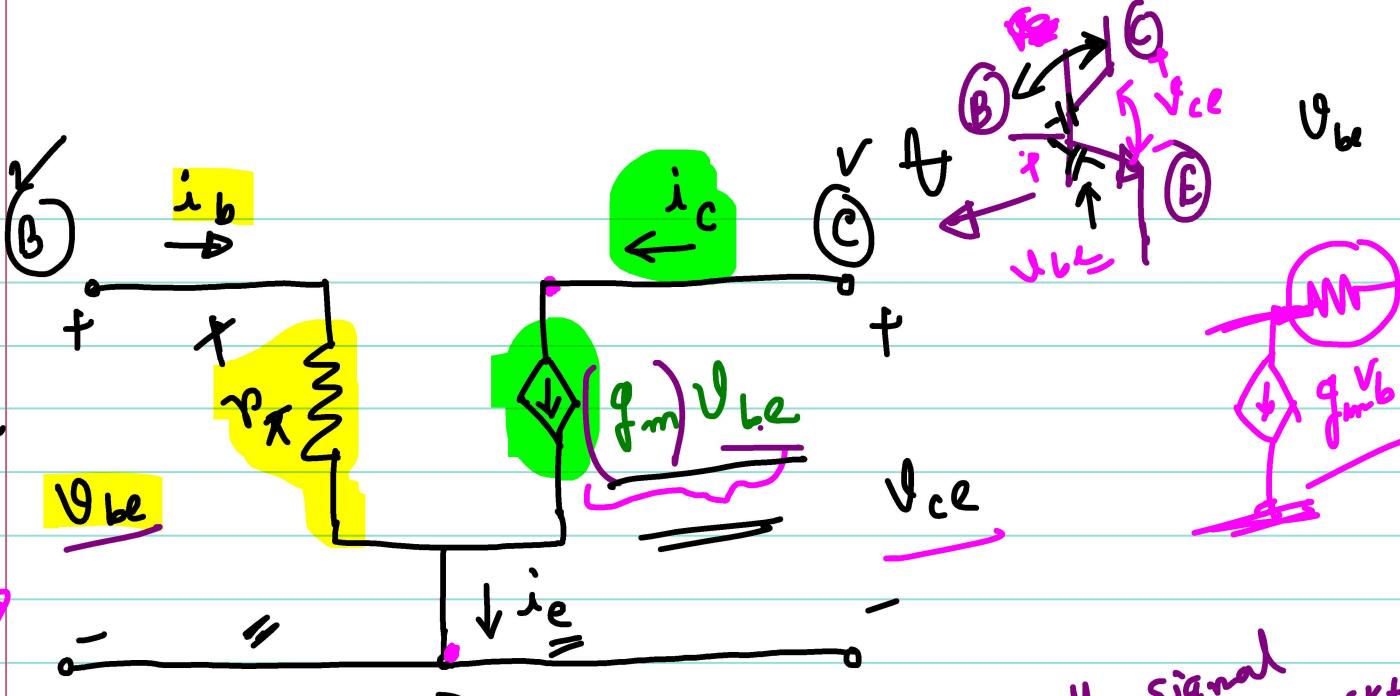Small signal parameters (g_m, r_π) are dependent on operating point (B.P.t).



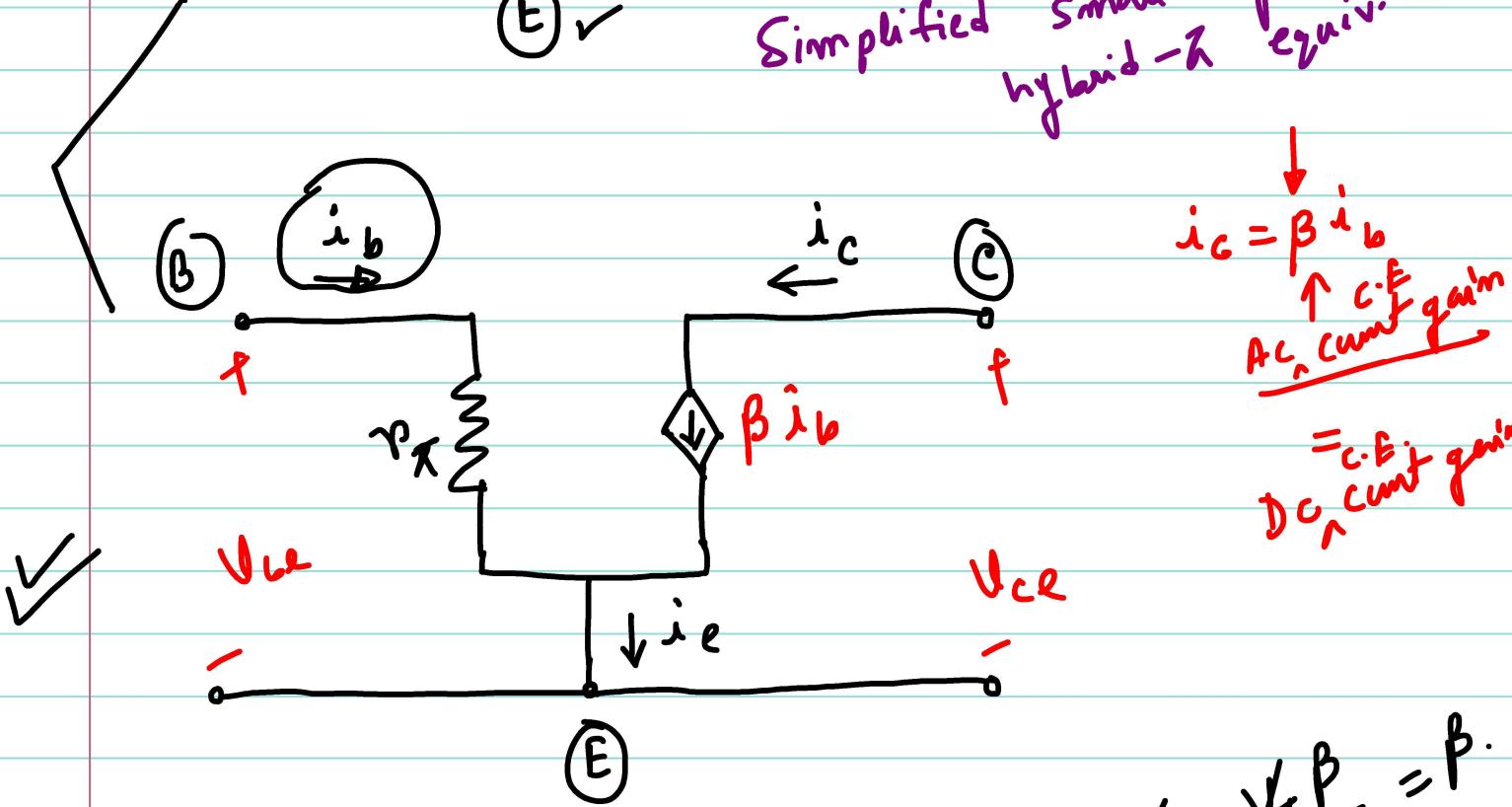
Simplified small-signal
hybrid- π equiv. ckt.




$$g_m \times r_\pi = \frac{I_{CS}}{\sqrt{V_T}} \times \frac{\sqrt{V_T} \beta}{I_{CS}} = \beta$$

$$g_m \times r_\pi = \beta$$

Example

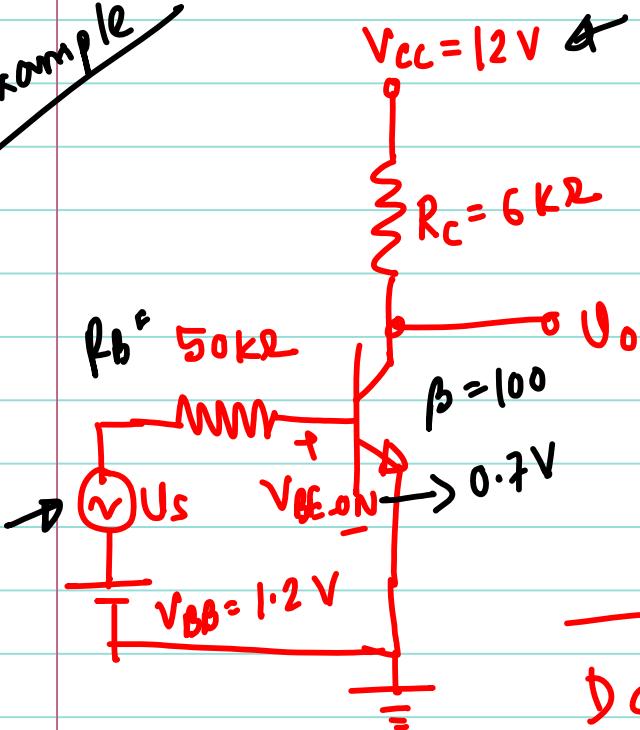

Find the Small Signal gain.

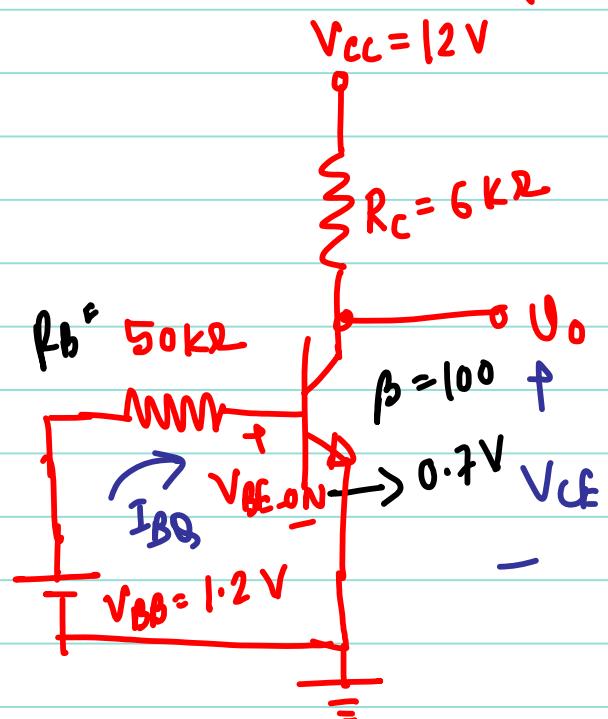

Component DC AC

$$I_{BQ} = \frac{1.2 - 0.7}{R_B}$$


R	R	R
C	open	short
$\rightarrow L$	short	open
Diode	$v_T + r_f$	$r_d = \frac{v_T}{I_D}$
Independent V_s	$+ v_s -$	short
Independent I_s	$\rightarrow I_s$	open

$$\begin{aligned} I_{BB.} &= \frac{10 \mu A}{\beta} \\ I_{CQ} &= \beta I_{BQ} = 100 \times 10 \mu A \\ &= 1 mA \end{aligned}$$

$$I_{EOL} = I_{BQ} + I_{CQ.} = 1.01 mA$$

$$V_{CEQ} = V_{CC} - I_C \cdot R_C = 6V$$

$$V_A = V_B$$

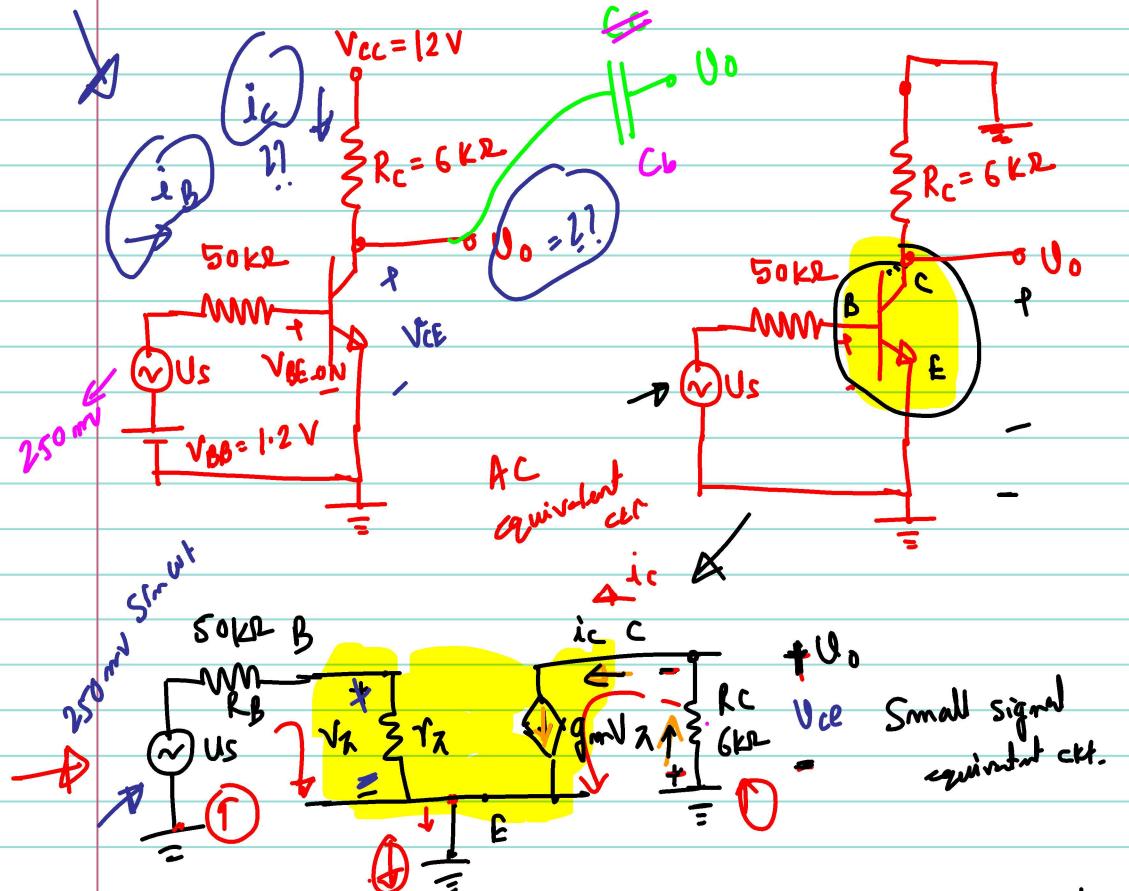





$$\gamma_x = \frac{\beta V_T}{I_{C8}} = \frac{100 \times 0.026}{1 \times 10^{-3}} = 2.6 \text{ k}\Omega \quad g_m = \frac{I_{C8}}{V_T} = 38.5 \text{ mA/V}$$

$$\begin{aligned} \text{gain} &= \frac{V_o}{V_s} = \frac{-i_c R_C}{V_s} = \frac{-g_m V_x R_C}{V_s} \\ \left[V_x = V_s \times \frac{r_x}{R_B + r_x} \right] &\quad \downarrow \\ \rightarrow \text{gain} &= -\frac{g_m R_C r_x}{R_B + r_x} \end{aligned}$$

$$V_s = 0.25 \sin \omega t \text{ V.}$$



$$\text{gain} = -11.4$$

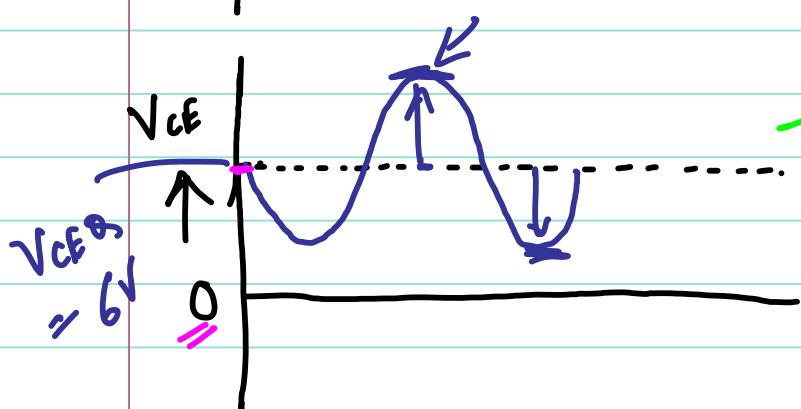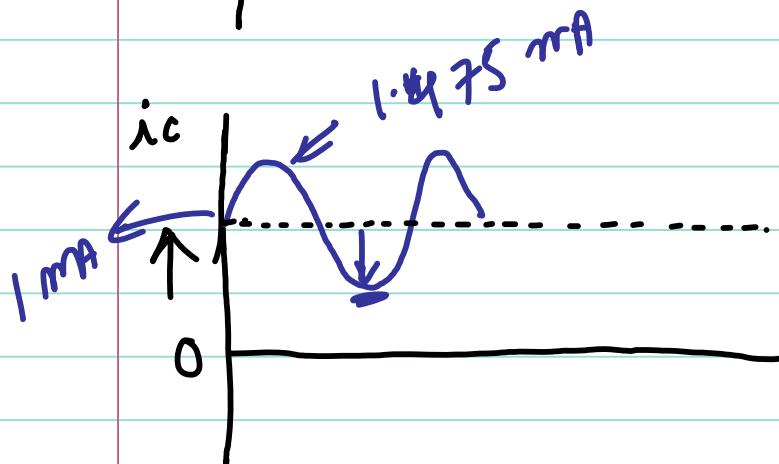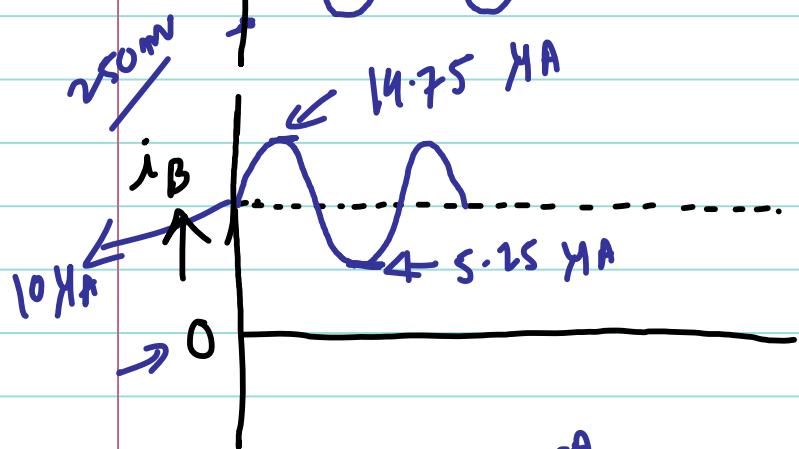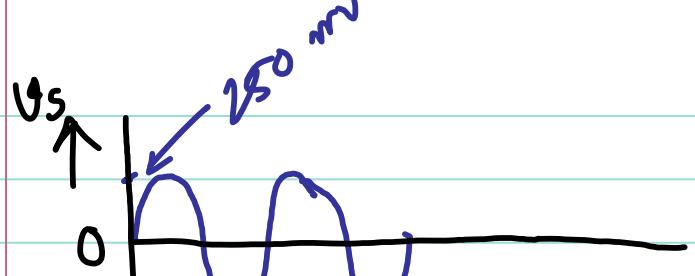

$$i_B = \frac{V_B}{r_A + R_B} \sin \omega t$$

$$= \frac{250 \text{ mV}}{12.96 \text{ mV} + 50} \sin \omega t$$

$$= 4.75 \sin \omega t$$

$$i_C = \beta \cdot i_B$$

$$= 0.475 \text{ mA}$$

capacitor


0V

$$V_{CE} = g_{ATM} \times V_S$$


$$= -11.4 \times 250 \text{ mV}$$

$$V_{BE} \rightarrow 10 \text{ mV}$$

$$V_{BE} = 12.96 \text{ mV}$$

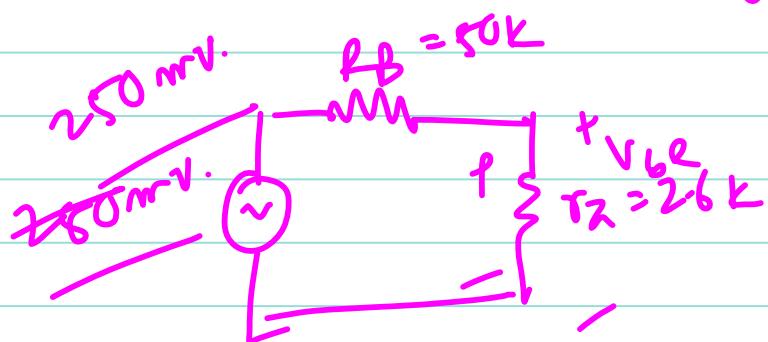

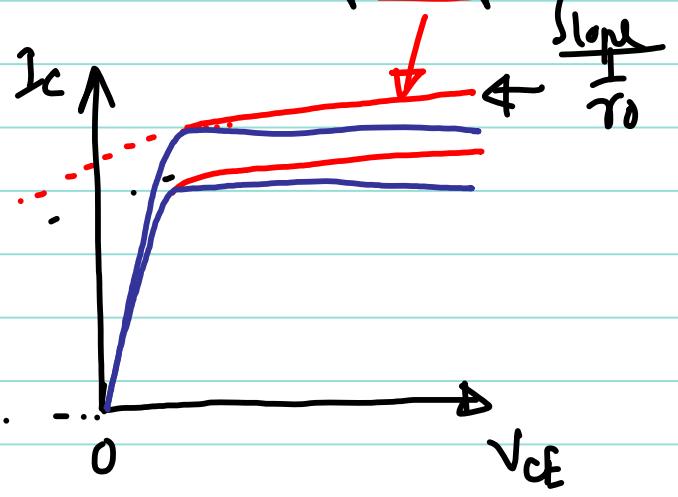Hybrid- π equivalent circuit considering early effect




(VA)


$$i_c = I_s \left[\exp \left(\frac{V_{BE}}{V_t} \right) \right] \left[1 + \frac{V_{CE}}{V_A} \right]$$

$$\frac{1}{r_0} = \frac{\partial i_c}{\partial V_{CE}} = \frac{I_{C0}}{V_A} ; \quad r_0 = \frac{V_A}{I_{C0}}$$

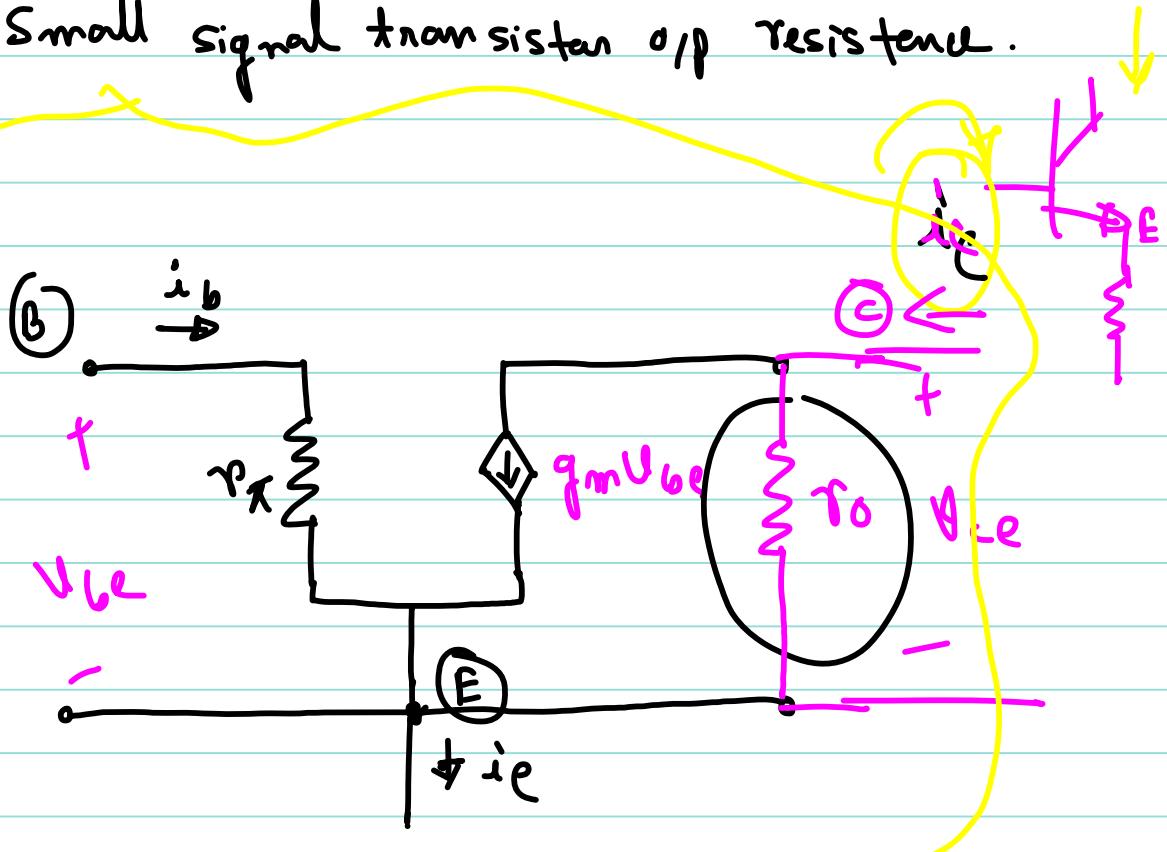r_0 = Small signal transistor o/p resistance.



Example

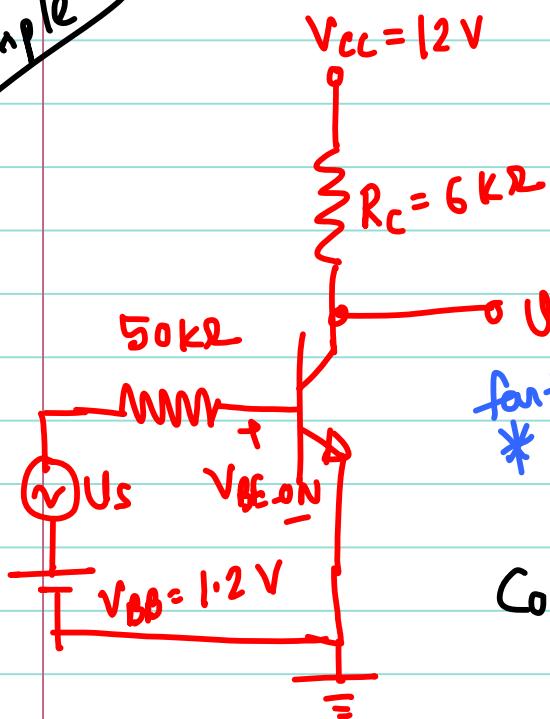


current gain = -11.4 ; without Early effect

Find the Small Signal gain.

Repeat this Considering Early Effect *

fartnis problem
* You can neglect Early effect during DC Analysis

Consider $V_A = 50\text{V}$.

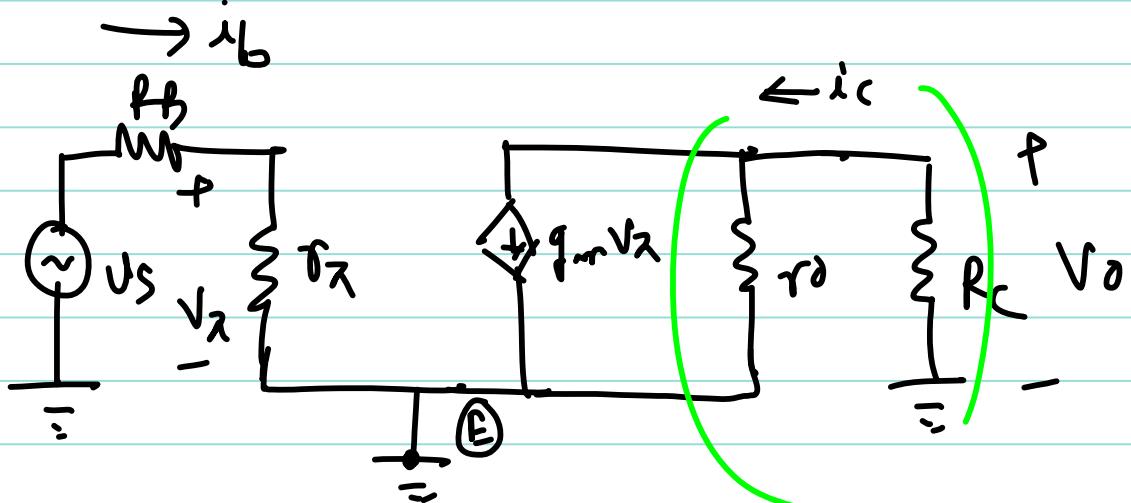

$$V_d = -g_m V_A (R_C \parallel r_o) ; V_A = \frac{V_{in} \times r_A}{r_A + r_B}$$

$$\text{gain} = \frac{V_o}{V_{in}} = -g_m \left(\frac{r_A}{r_A + r_B} \right) (R_C \parallel r_o)$$

$$\text{gain.} = -10.18$$

Equivalent circuit for p-n-p BJT

