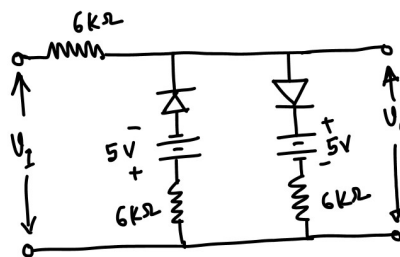



## Basic Electronics (Test – 1, Part - A)

- **Instructions:** Please mention these on the first page of your answer script (your name, roll no., subject name, your signature and date); Insert page no. in every page; The final answer(s) (numerical values with unit) should be enclosed within a box ; Show the necessary steps in your answers with high clarity and supported explanation; All waveform sketches / diagrams must be neatly drawn and clearly labelled; At the end of this test, you have to upload a single PDF file of your hand-written answer script (Max file size 10 MB); Please note that, this question paper has two parts: **Part A** and **Part B**; For any doubt, please feel free to ask the instructor.

1. For the circuit shown in the following figure, consider the diodes are ideal ( $V_f = 0$  V). If the input voltage ( $V_i$ ) is swept from  $-8$  V to  $+8$  V, find the output voltage ( $V_o$ ). Neatly plot the variation of  $V_o$  with  $V_i$  for this range of input. [3+2]



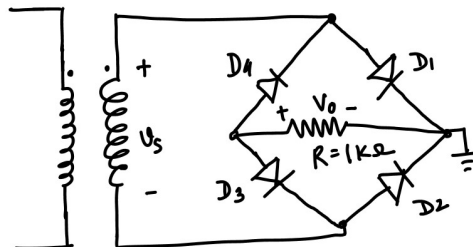2. For the following circuit, the secondary voltage ( $V_s$ ) is  $5 \sin(314t)$  V. For one time-period ( $T$ ), estimate the time duration during which the diodes are conducting. Neatly draw the waveforms of  $V_o$  and  $V_s$  on the same X and Y-axis. Calculate the PIV of diode  $D_3$ . Given that,  $V_f = 0.6$  V. [3+1+1]



3. An n-type Si material has a resistivity of  $\rho = 0.65 \Omega\text{-cm}$ . (i) If the electron mobility is  $\mu_n = 1250 \text{ cm}^2/\text{V-s}$ , what is the concentration of donor atoms? (ii) Determine the required electric field to establish a drift current density of  $J = 160 \text{ A/cm}^2$ . [2+2]

4. Assuming the diodes are ideal ( $V_f = 0$ ), estimate the current  $I$  as indicated in the following circuit. [3]

