

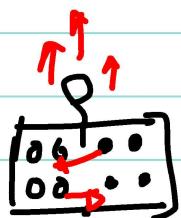


Lec-5

p-n junction in forward Bias

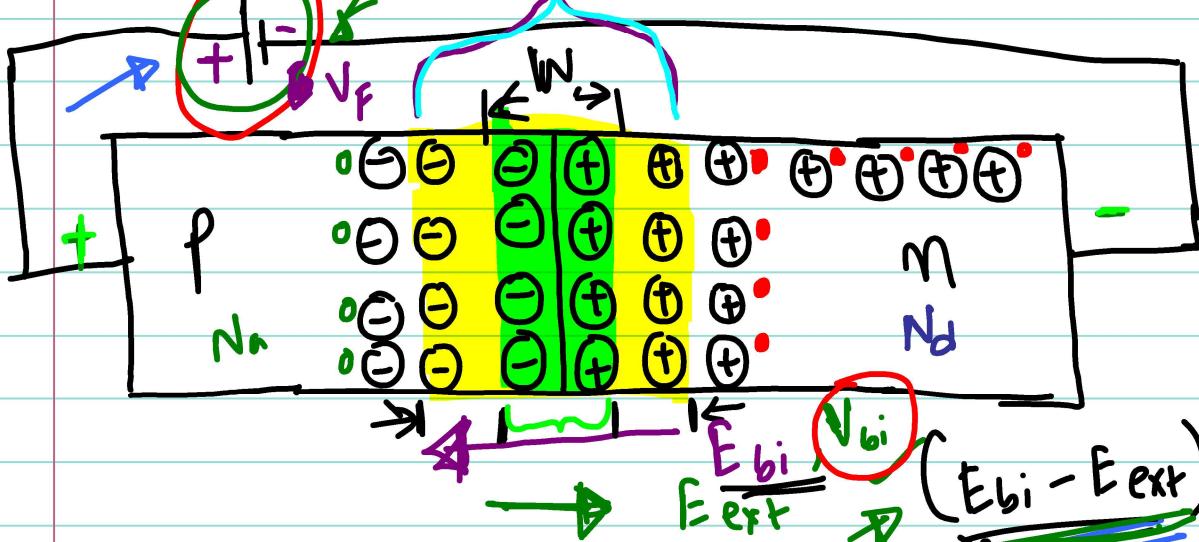


$$V_{bi} > V_{ext}$$

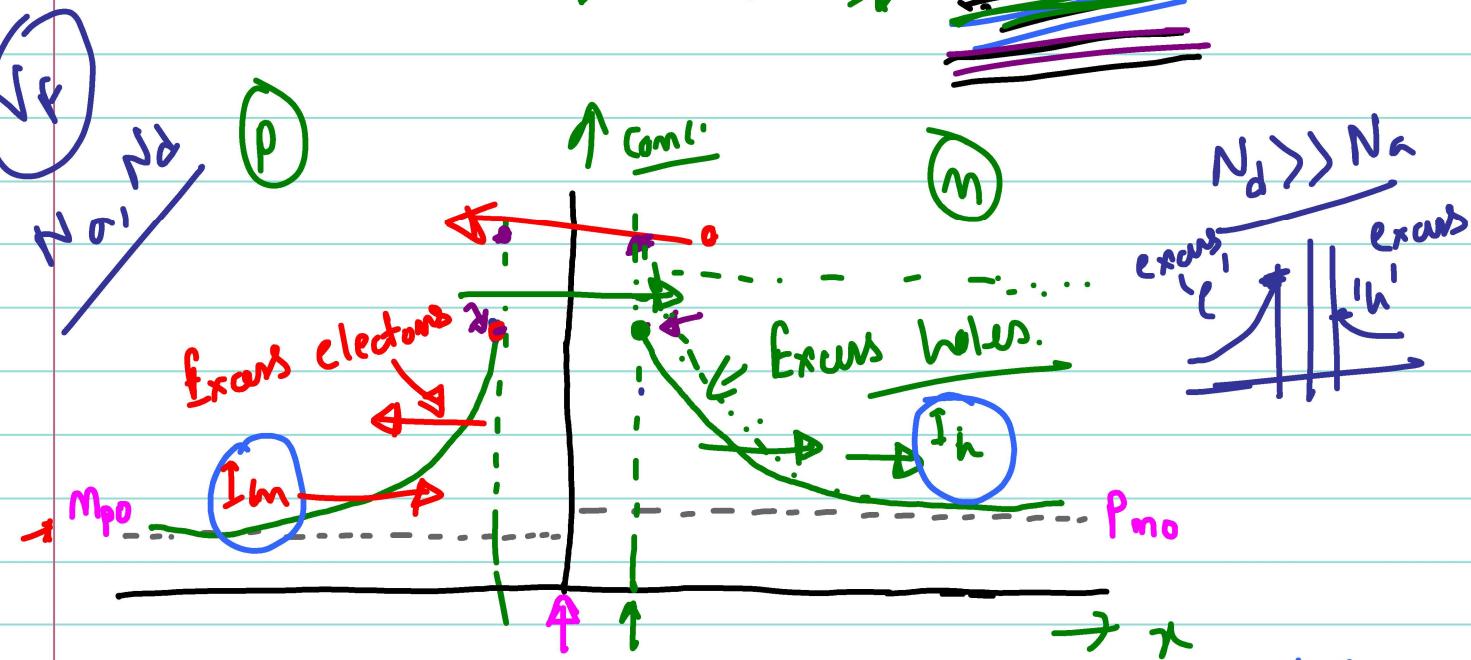

$$I_D = I_s \left[e^{-\frac{V_D}{nV_T}} - 1 \right]$$

$$V_T = \frac{kT}{q}$$


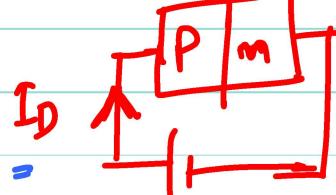
η = ideality factor or
emission coefficient } $\eta = 1$





I_s = Reverse-bias saturation current $\rightarrow \eta = 1$

$$= 10^{-13} \text{ A to } 10^{-9} \text{ A}$$

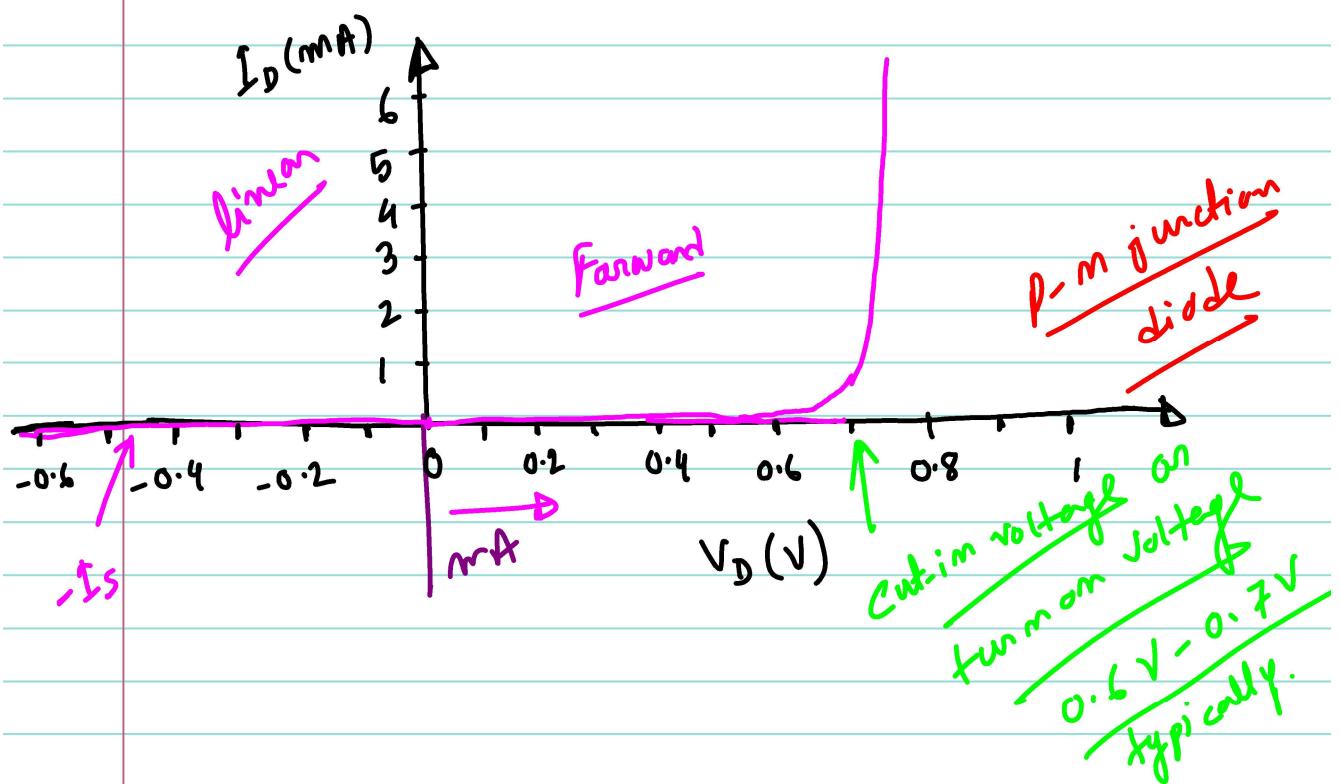
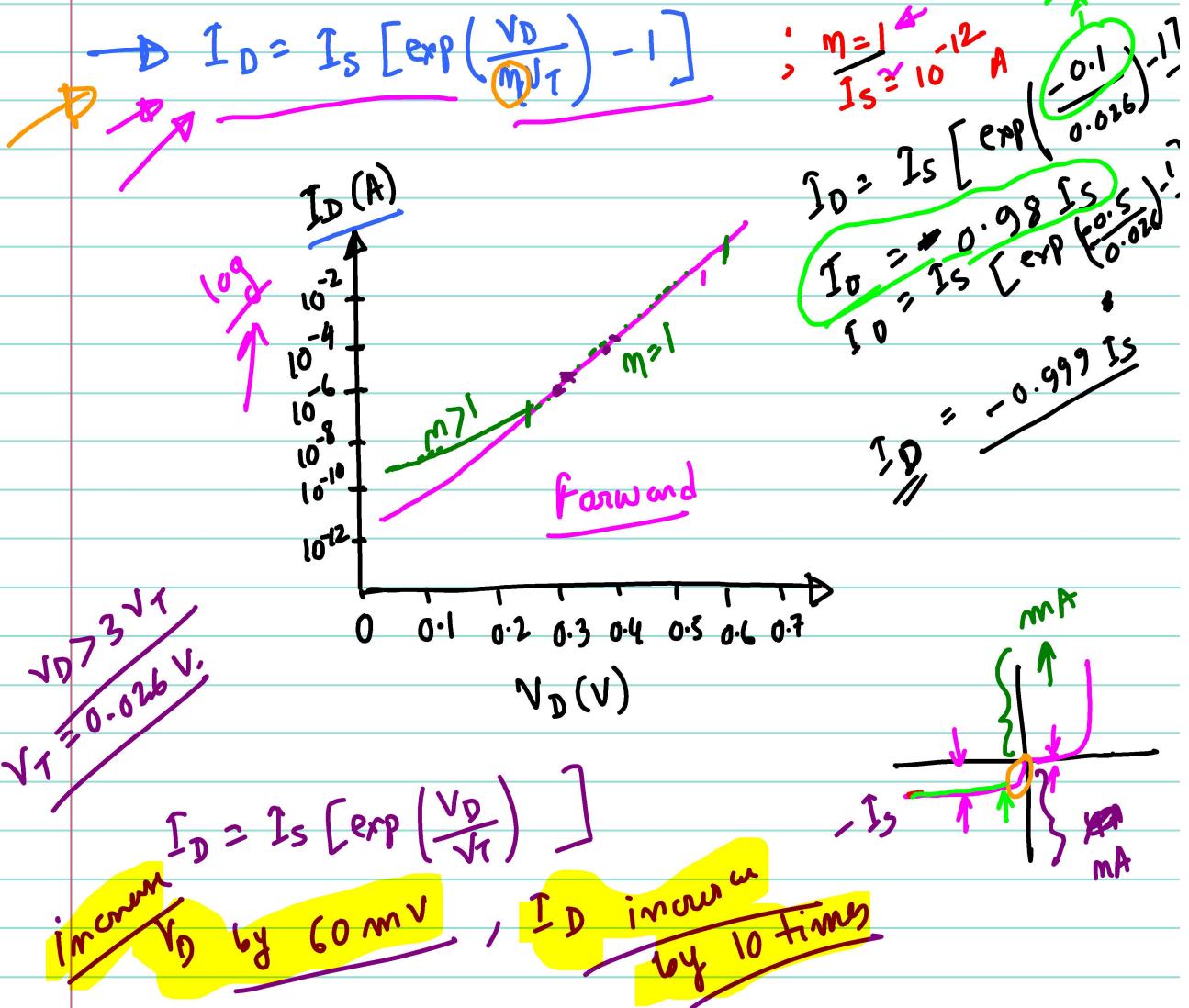
Current - Voltage characteristics of pn junction:





Breakdown im pn junction diode:

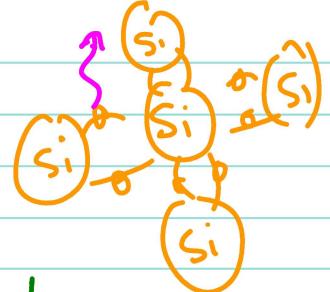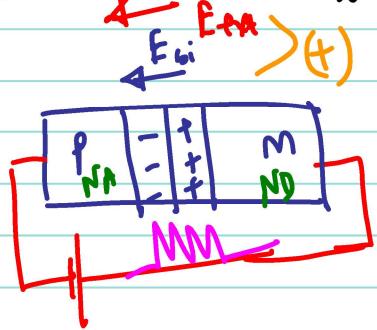


$I_D(A)$ linear

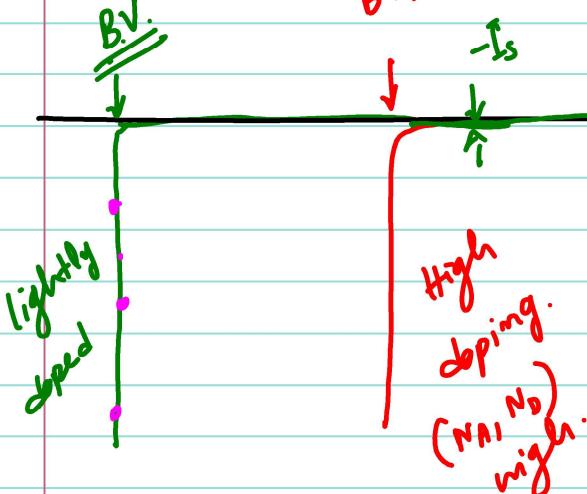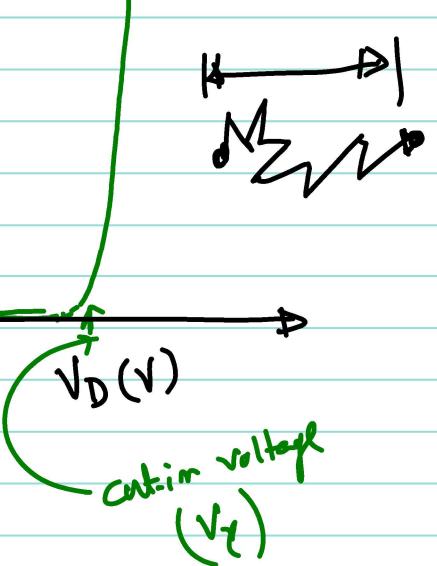


Avalanche Breakdown:

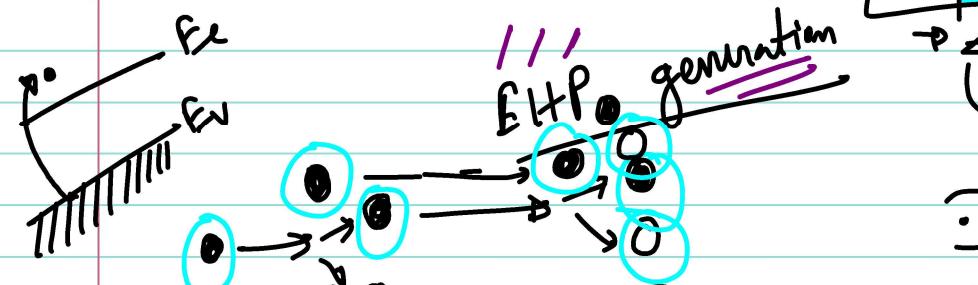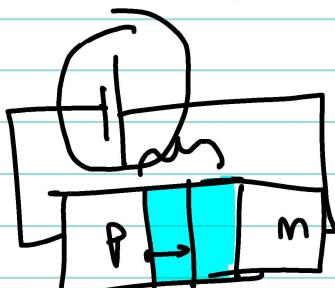

Zener Breakdown:


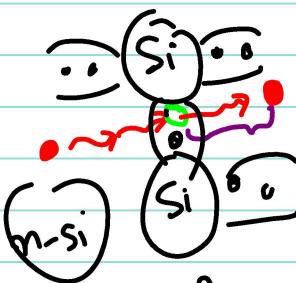



Tunneling, Doping conc. high.

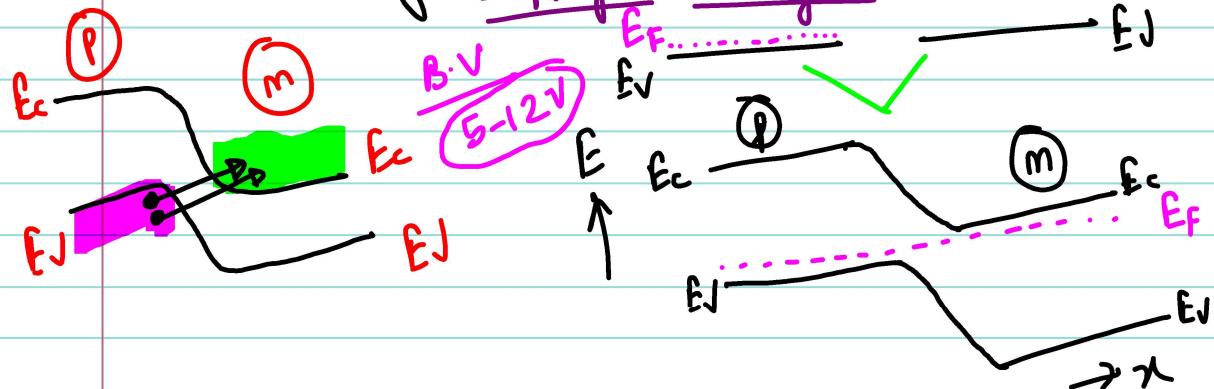


$$I_S \approx A_2 \left(\frac{Dm}{Lm} \right) \Delta A + \frac{D_p}{L_p} \frac{n_A^2}{N_D} m_i = B T^{3/2} \exp\left(-\frac{E_g}{2kT}\right)$$

Effect of temperature:

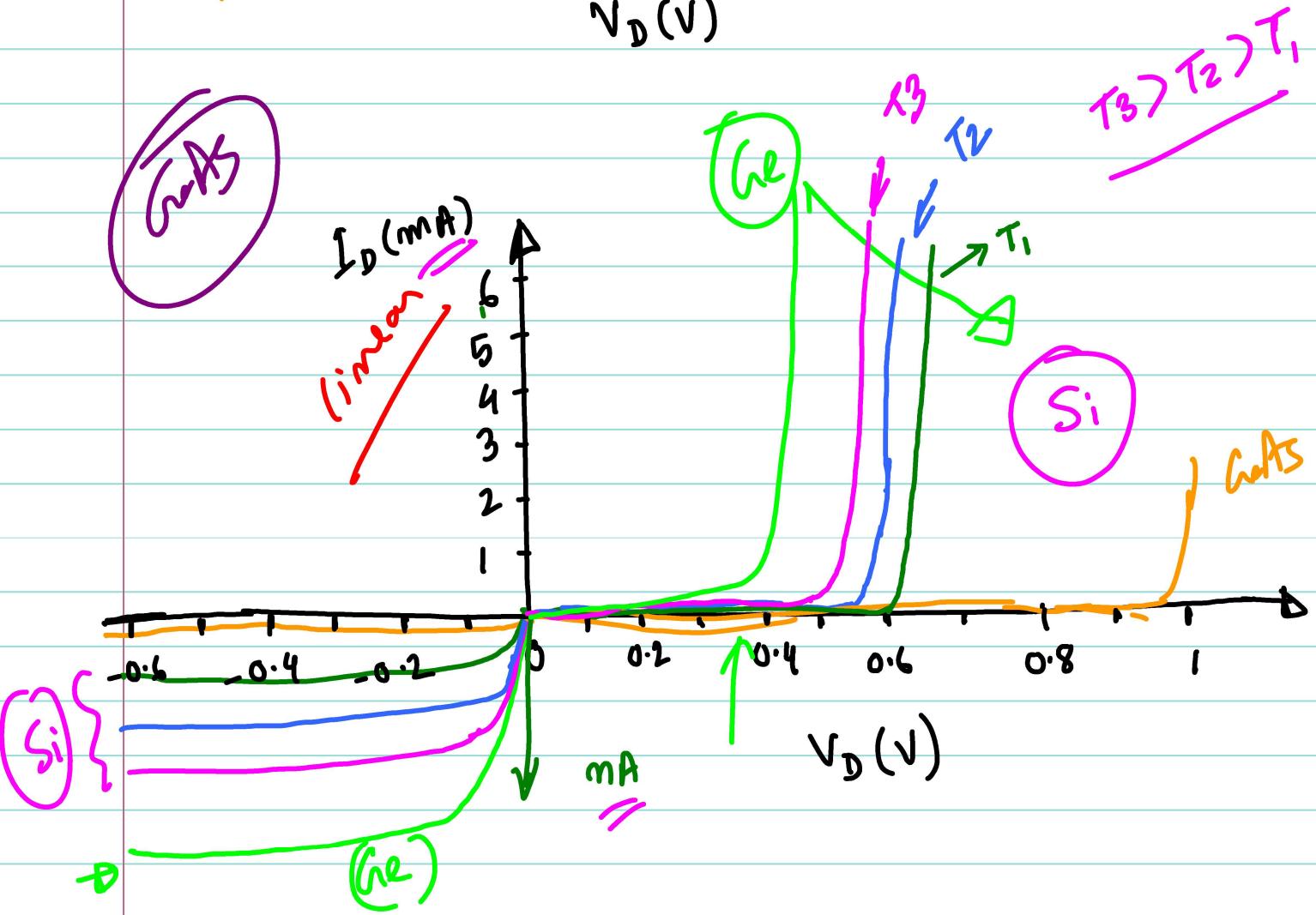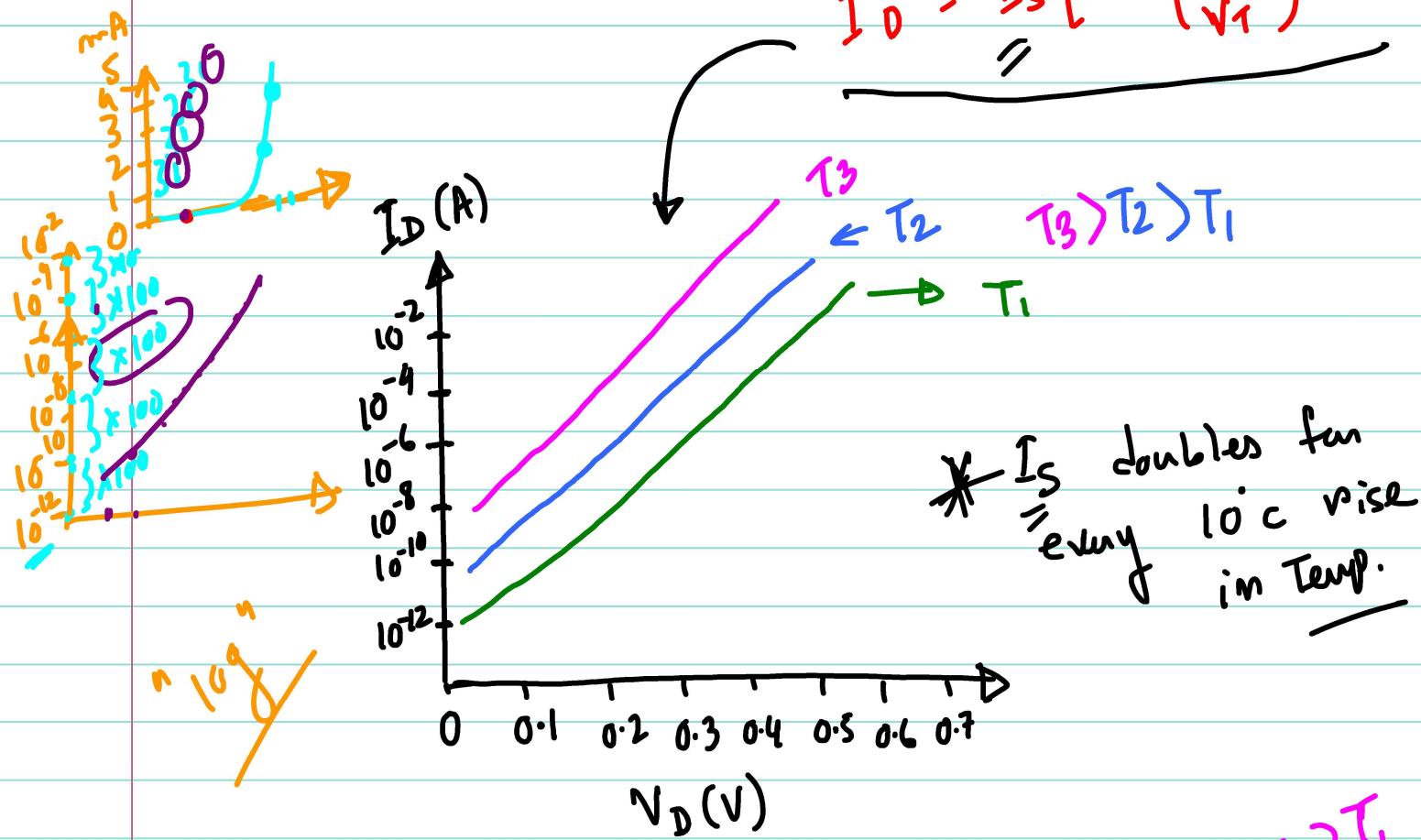

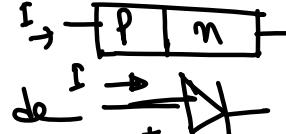
p-n junction diode  ckt. symbol.

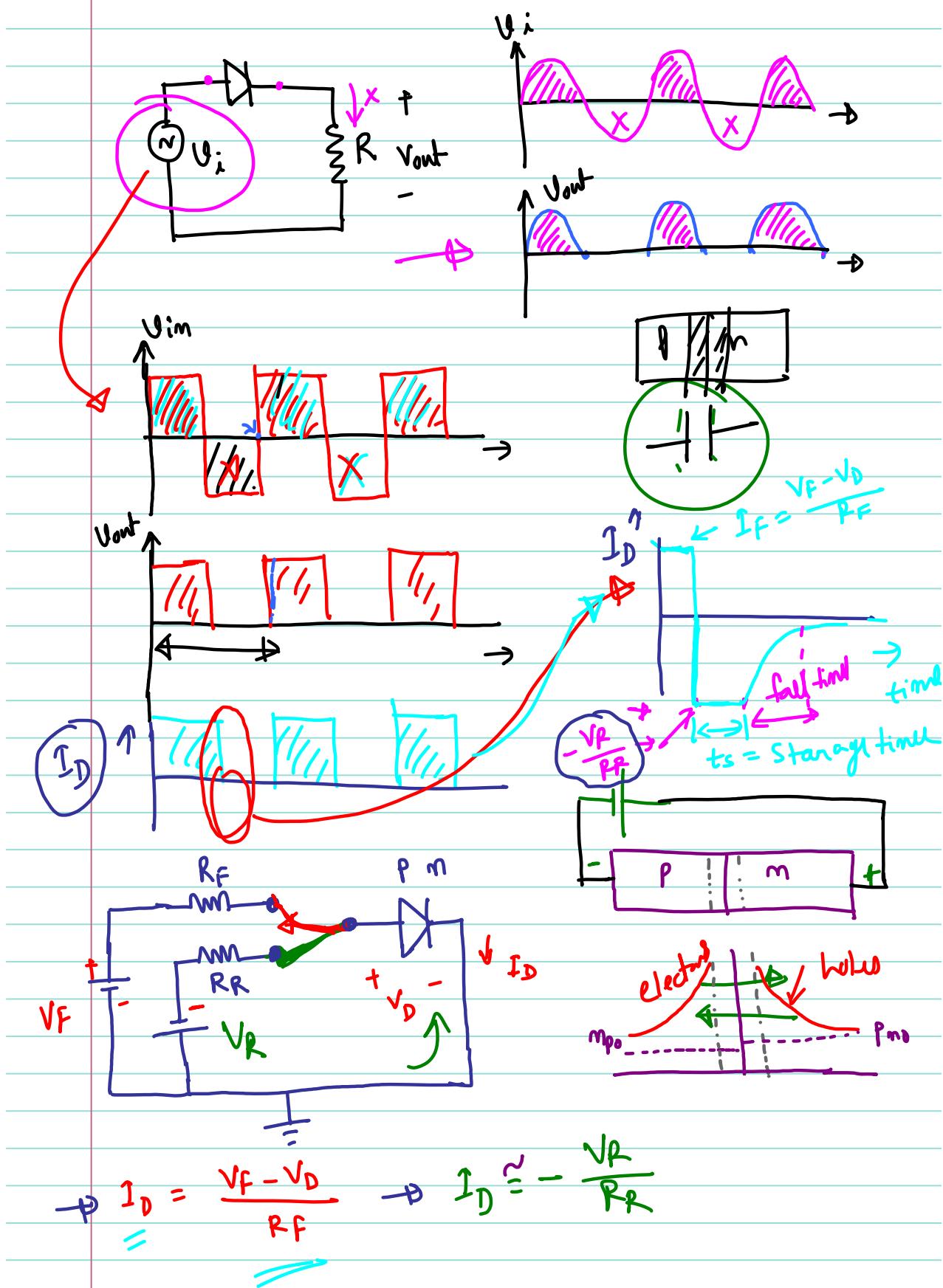

Lec-6

Diode Circuits: DC Analysis.

(i) By Iteration

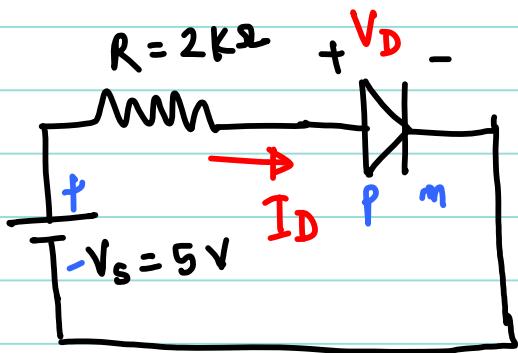

$$V_s = I_D \cdot R + V_D$$

$$I_D = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

$$V_s = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] R + V_D$$

$$I_s = 10^{-13} \text{ A (say)}$$

$$5 = 10^{-13} \times 2 \times 10^3 \times \left[\exp\left(\frac{V_D}{0.026}\right) - 1 \right] + V_D$$


$$\rightarrow V_D = 0.60 \text{ V}$$

$$\rightarrow V_D = 0.65 \text{ V} \rightarrow 15.1 \text{ V}$$

$$\underline{\underline{V_D = 0.619 \text{ V}}}$$

$$I_D = \frac{5 - 0.619}{2 \times 10^3} \text{ A}$$


(ii) Graphical Technique

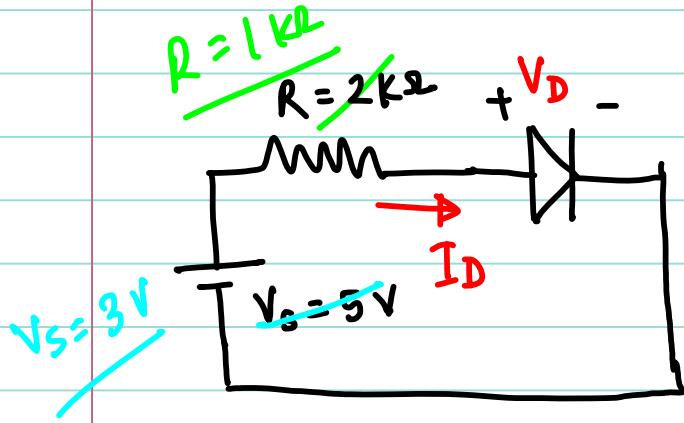



$$V_S = I_D R + V_D$$

$$I_D = \frac{V_S}{R} - \frac{V_D}{R}$$
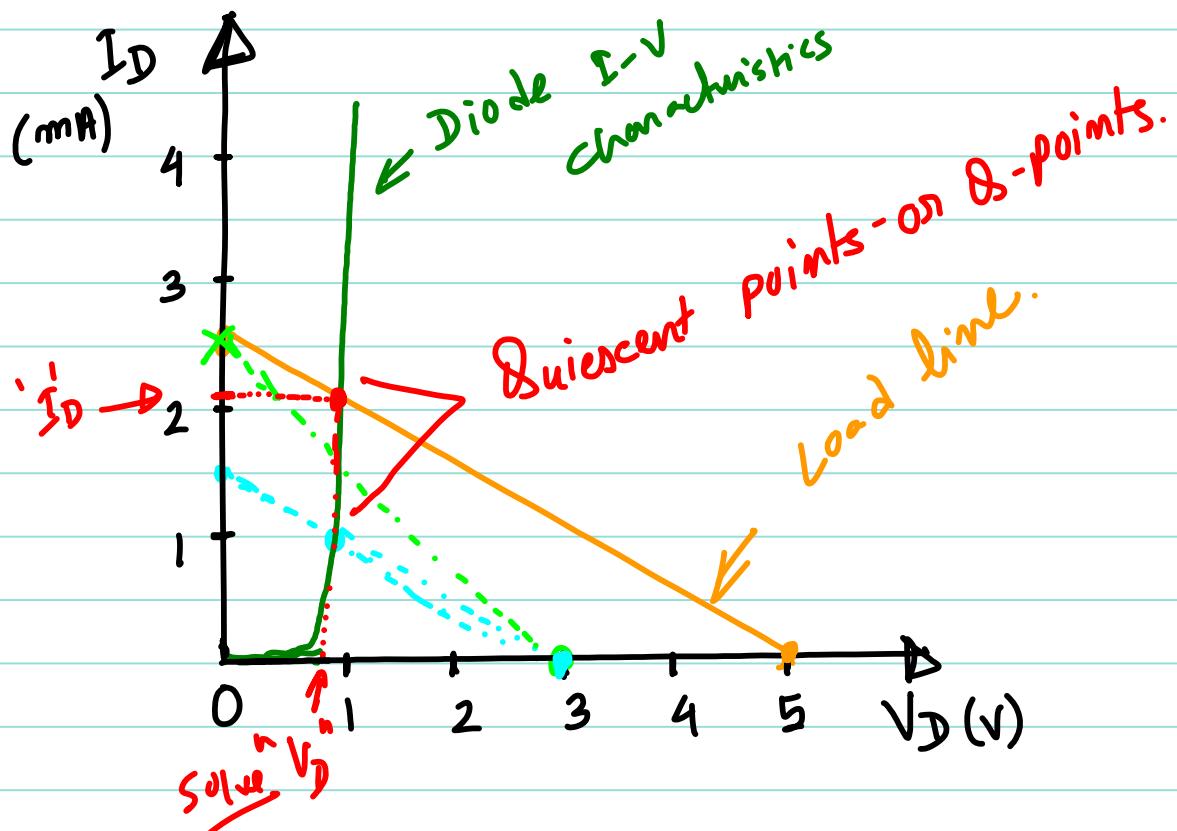
$$\begin{aligned} I_D &= 0, & V_D &= V_S = 5V \\ \underline{V_D = 0}, & \underline{I_D = 2.5 \text{ mA}} \end{aligned}$$



(iii) By using Piecewise Linear Model

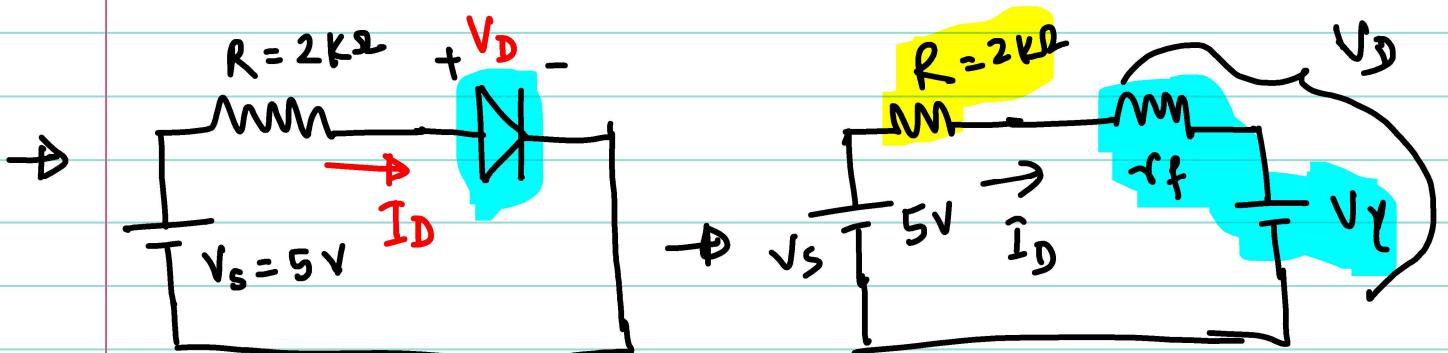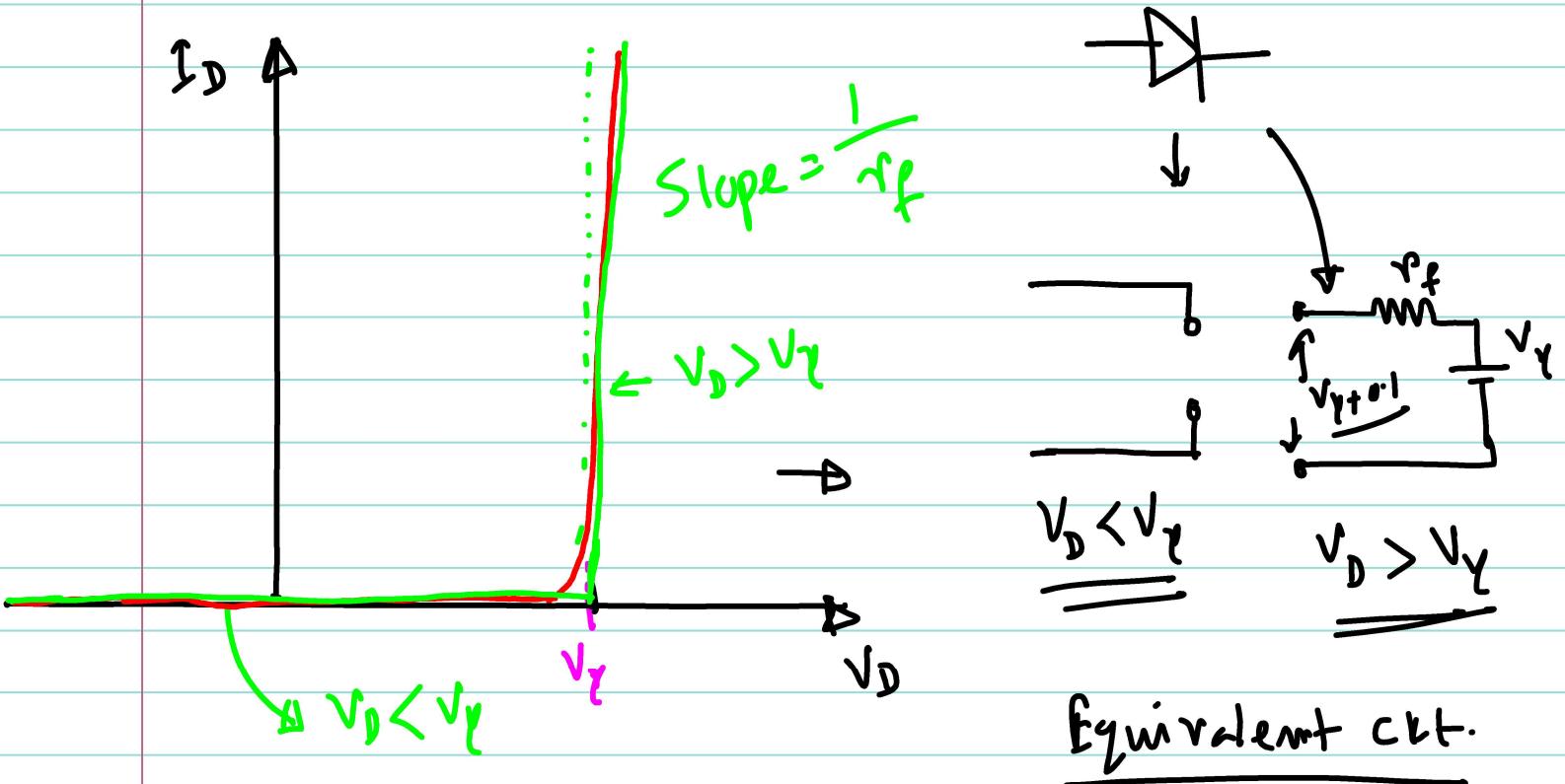

$$V_Y = 0.6V, r_f = 10 \Omega$$

$$I_D = \frac{5 - 0.6}{2k\Omega + 10\Omega}$$

$$= 2.19 \text{ mA}$$

$$V_D = 0.6 + I_D r_f = 0.6 + 2.19 \times 10^{-3} \times 10 = 0.622V$$


$$2.19 \times 10^{-3} \times 10$$

Diode circuit : Example-1

For each diode reverse-saturation current (I_s) is

2×10^{-13} A. Find out the input voltage (V_{in}) such that

output voltage (V_{out}) becomes 0.6 V.

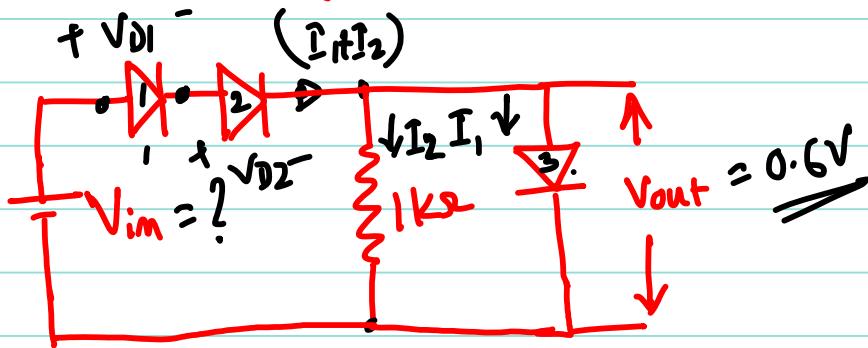

$$I_s = \underline{2 \times 10^{-13} \text{ A}} \quad ; \quad V_{out} = \underline{0.6 \text{ V}}$$

$$I_1 = I_s \exp\left(\frac{0.6}{0.026}\right) = 2.105 \text{ mA}$$

$$I_2 = \frac{0.6}{1 \text{ k}\Omega} = 0.6 \text{ mA}$$







$(I_1 + I_2)$ is flowing through the diode ① and ②
 $\underline{= 2.705 \text{ mA}}$

$$V_{D1} = V_{D2} = V_T \ln\left(\frac{I_1 + I_2}{I_s}\right) = \underline{0.6065 \text{ V.}}$$



$$V_{in} = V_{D1} + V_{D2} \neq V_{out} = \underline{1.81 \text{ V.}}$$

$\left. \begin{array}{l} V_D > 3V_T \\ (-1) \text{ term} \\ \text{can be} \\ \text{neglected} \end{array} \right\}$

Rectifier circuits:

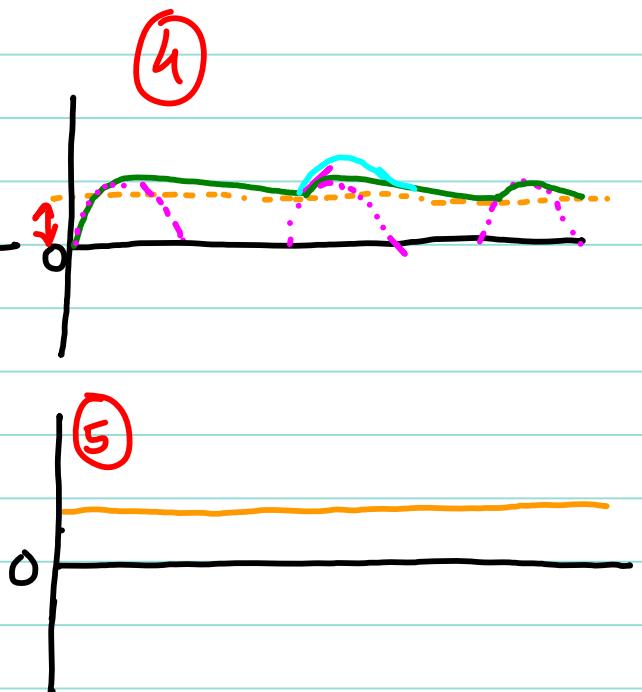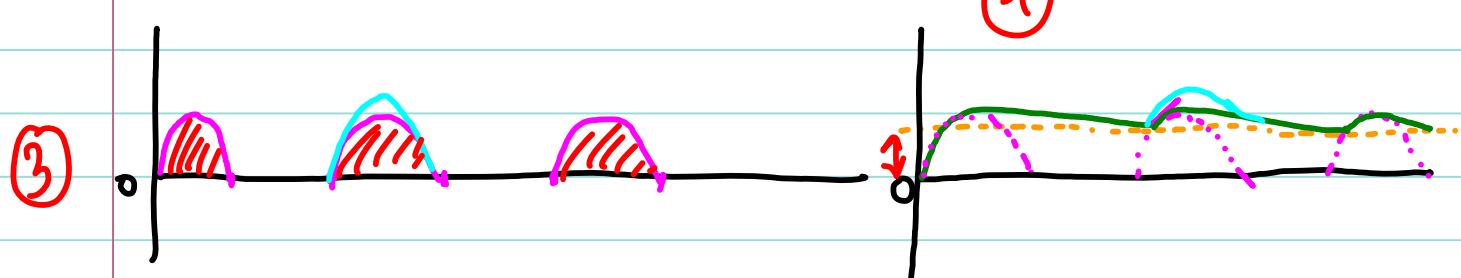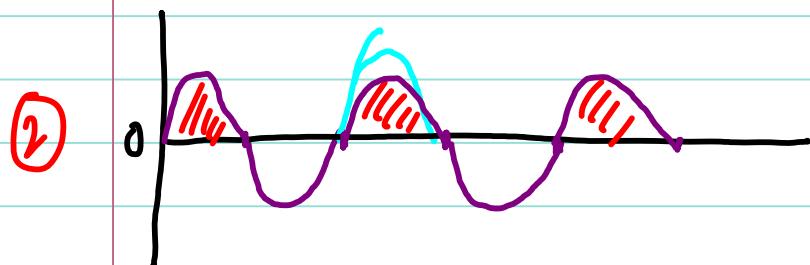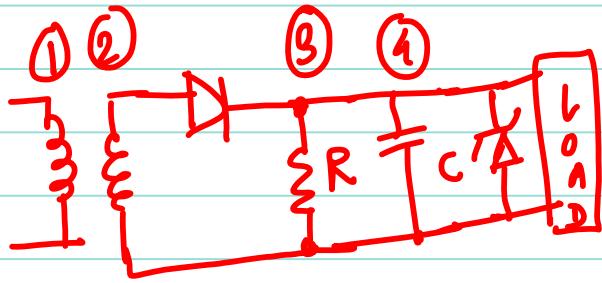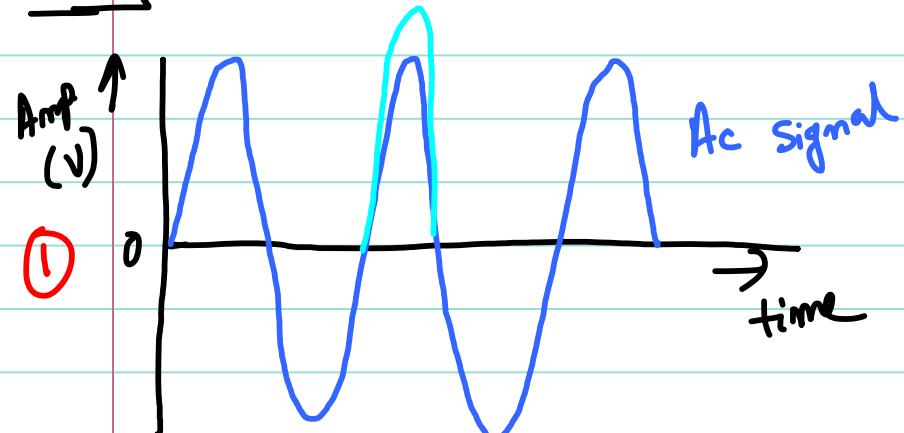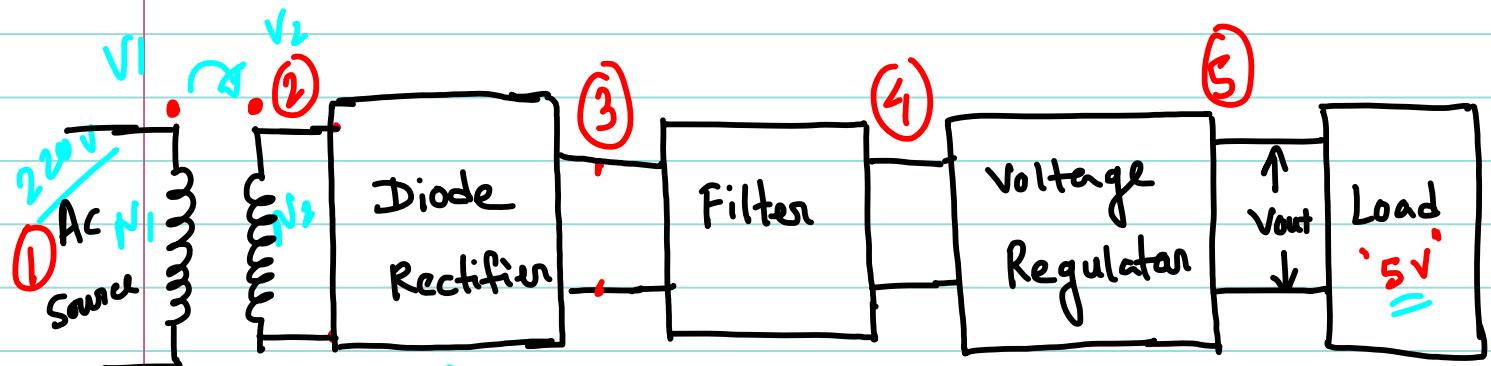

Question

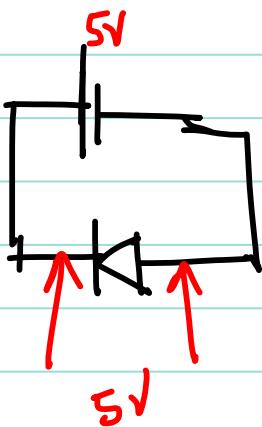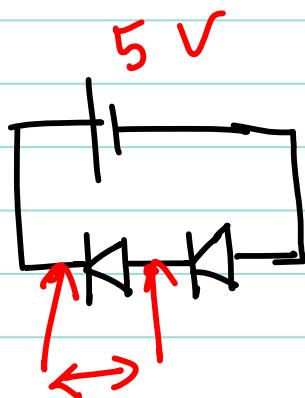

$$I_D = I_s \left[\exp \left(\frac{V_D}{V_T} \right) - 1 \right]$$

