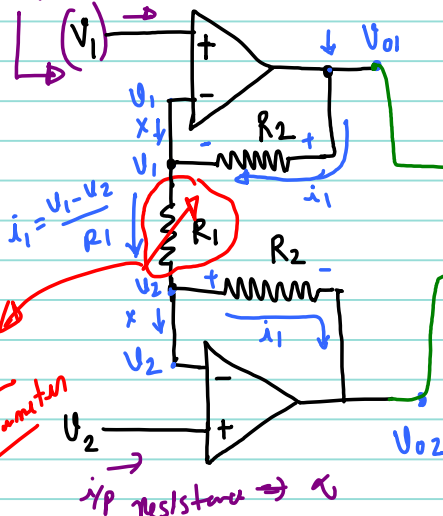


Lec-27

Instrumentation Amplifier:

i/p resistance $\approx \infty$



POT
potentiometer

V_1
 V_2

i/p resistance $\Rightarrow \infty$

$$V_{01} = V_1 + i_1 R_2$$

$$V_{01} = V_1 + \frac{V_1 - V_2}{R_1} \cdot R_2$$

$$V_{02} = V_2 - i_1 R_2$$

$$V_{02} = V_2 - \frac{V_1 - V_2}{R_1} \cdot R_2$$


$$V_o = \frac{R_4}{R_3} (V_{02} - V_{01}) = \frac{R_4}{R_3} \left(V_2 - \frac{V_1 - V_2}{R_1} \cdot R_2 - V_1 - \frac{V_1 - V_2}{R_1} \cdot R_2 \right)$$

$$\Rightarrow V_o = \frac{R_4}{R_3} [V_2 - V_1] \left[1 + \frac{2R_2}{R_1} \right]$$


by changing only this R_1 , you can change the overall gain.

i/p resistance is also ∞
(very high.)

Difference Amp.

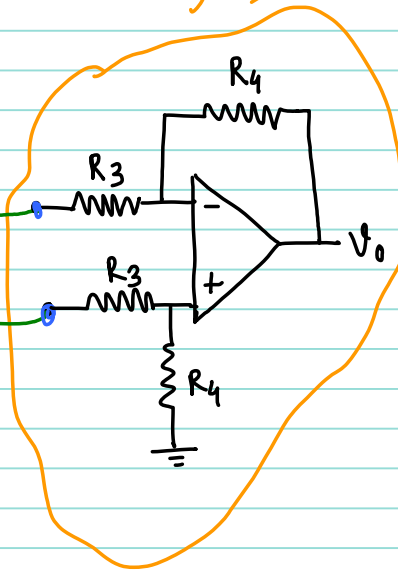

Common mode rejection ratio: (CMRR)

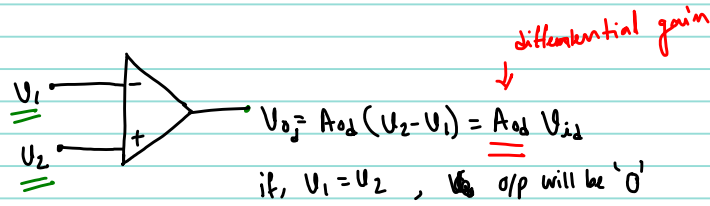

$A_{cm} \rightarrow$ common mode gain.



Common mode signal is generally defined as


$$= \left(\frac{V_1 + V_2}{2} \right)$$

CMRR value is quite high, so it is expressed in 'dB'

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| ; \text{ ideally, } A_{cm} = 0$$

$$CMRR \text{ in dB} = 20 \log \left| \frac{A_d}{A_{cm}} \right|$$

Example
for a Difference Amp:

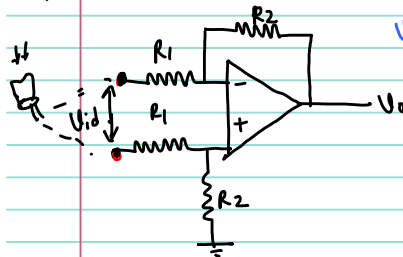

$$V_0 = \frac{R_2}{R_1} (V_2 - V_1) = \frac{R_2}{R_1} V_{id} \left(\frac{V_0}{V_{id}} = \frac{R_2}{R_1} \right)$$

$$V_{id} = 50 \text{ mV}$$

$$R_2 = 10 R_1$$

$$CMRR = 90 \text{ dB}$$

50 Hz Noise (common to both i/p's)
Amplitude = 5 mV

Find out common mode o/p voltage.

$$CMRR = 90 \text{ dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right) \text{ dB}$$

$$\frac{A_d}{A_{cm}} = 10^{4.5} \approx 31,622$$

$$\rightarrow \underline{A_d} = 31,622 \times \underline{A_{cm}} ; A_{cm} = \frac{A_d}{31,622}$$

$$A_d = \frac{R_2}{R_1} = 10$$

$$A_{cm} = \frac{10}{31,622}$$

$$\text{Common mode o/p signal} = A_{cm} \times 5 \text{ mV}$$





Common-mode input = 5 mV

$$= \frac{10}{31,622} \times 5 \text{ mV}$$

$$= \underline{\underline{1.58 \mu\text{V}}}$$


Typical values of CMRR \rightarrow 70 - 100 dB

Precision Half-Wave Rectifier:

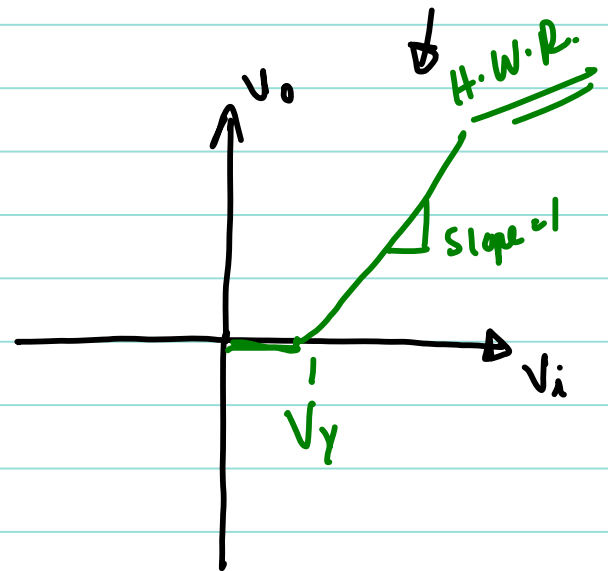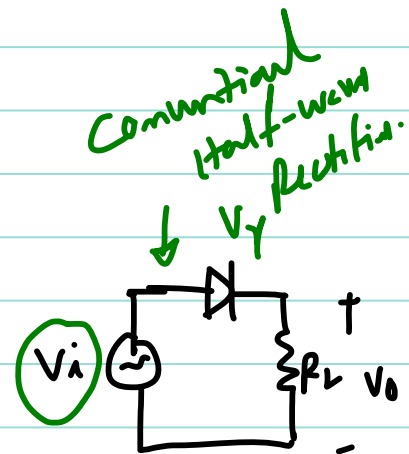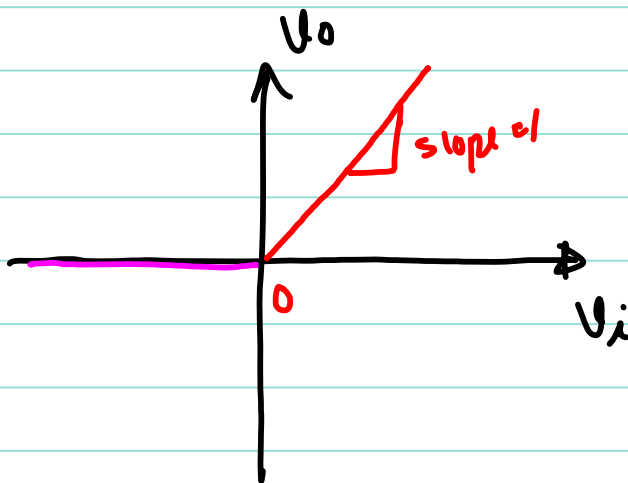
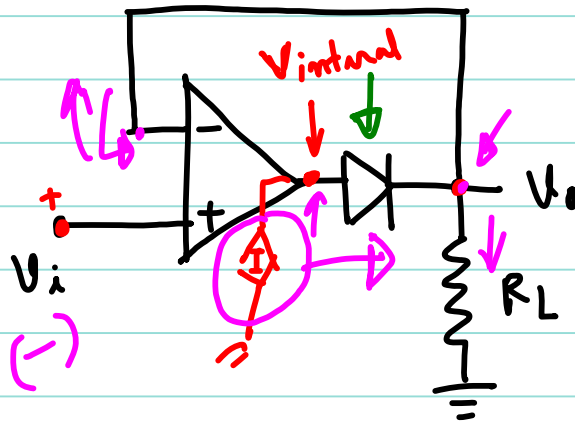


Slew Rate: Maximum rate of change in o/p voltage of an Op-Amp.


Unit \rightarrow V/time, V/ μ Sec.

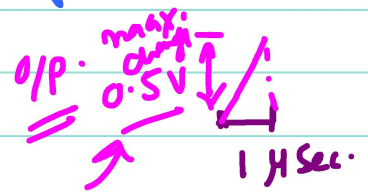

for 741, slew rate = 0.5 V / μ Sec.

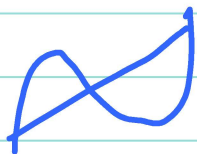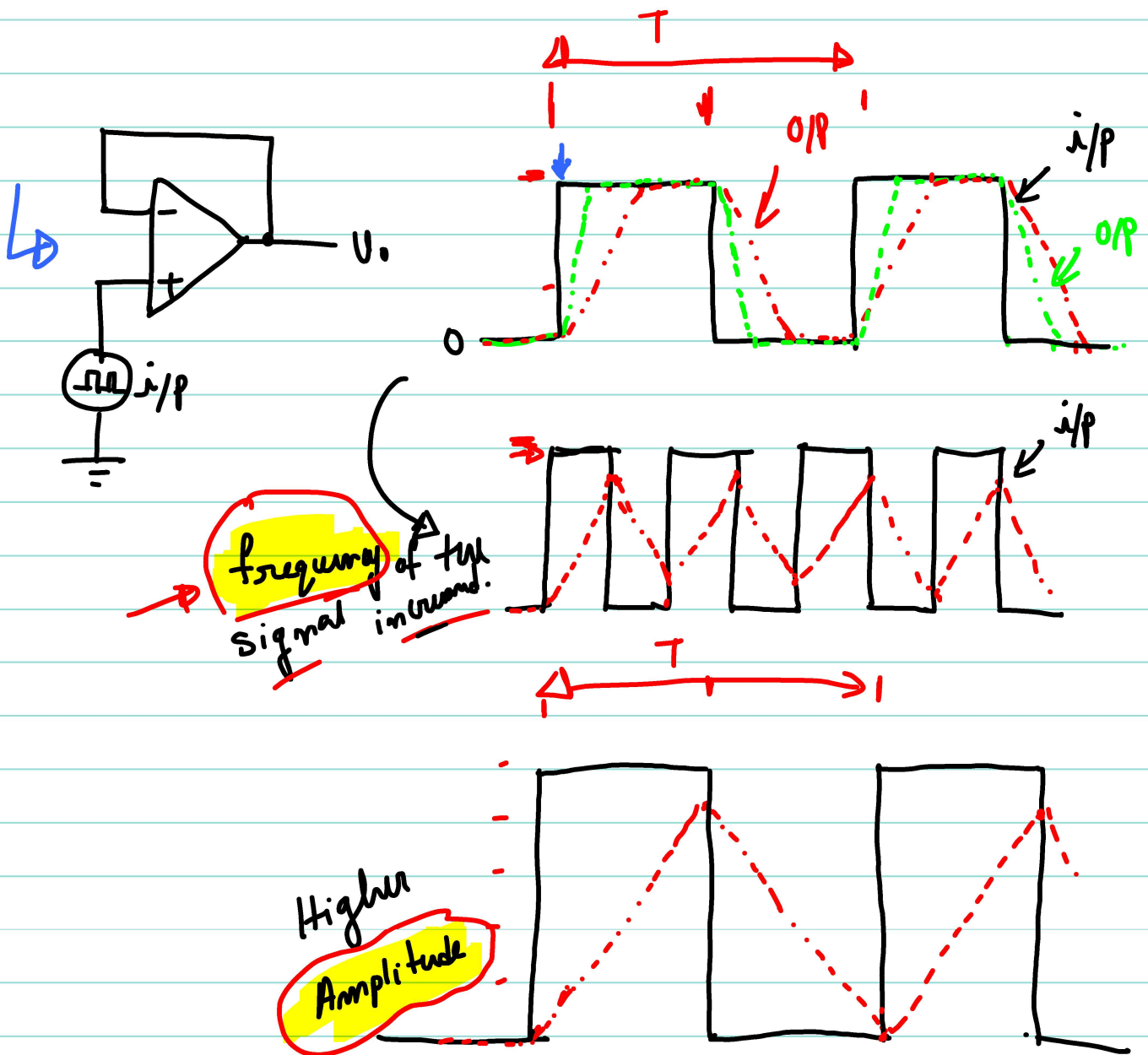

Non-inverting Amp:

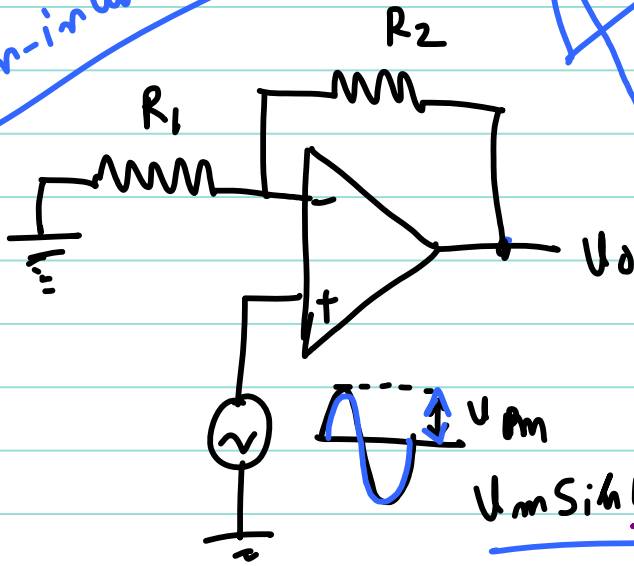

O/P
 $V_o = \left(1 + \frac{R_2}{R_1}\right) u_m \sin \omega t$
i/p signal

$V_o = V_p \sin \omega t$
 $V_p = \left(1 + \frac{R_2}{R_1}\right) u_m$

$V_o = V_p \sin \omega t$

$\frac{dV_o}{dt} = V_p \omega \cos \omega t$

rate of change of o/p. \leq Slew rate (S.R.)

$\omega V_p \cos \omega t \leq \text{S.R.}$
 max. value

$\omega V_p \leq \text{S.R.}$


$2\pi f_{\max} V_p \leq \text{S.R.}$

$f_{\max} \leq \frac{\text{SR}}{2\pi V_p}$

$\omega = 2\pi f_{\max}$


f_{\max} = Full power bandwidth freq.

Off-Set Voltages!

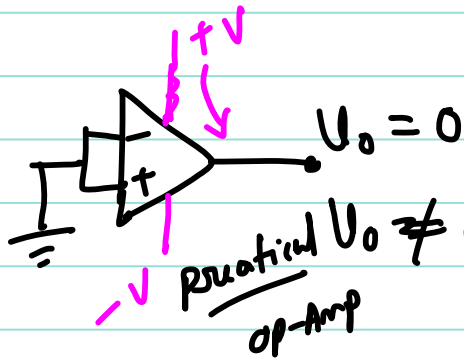

practical $U_o \neq 0$, \rightarrow output dc offset voltage.

op-amp

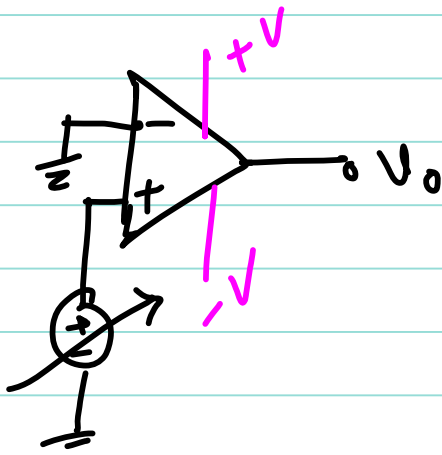

input dc offset voltage