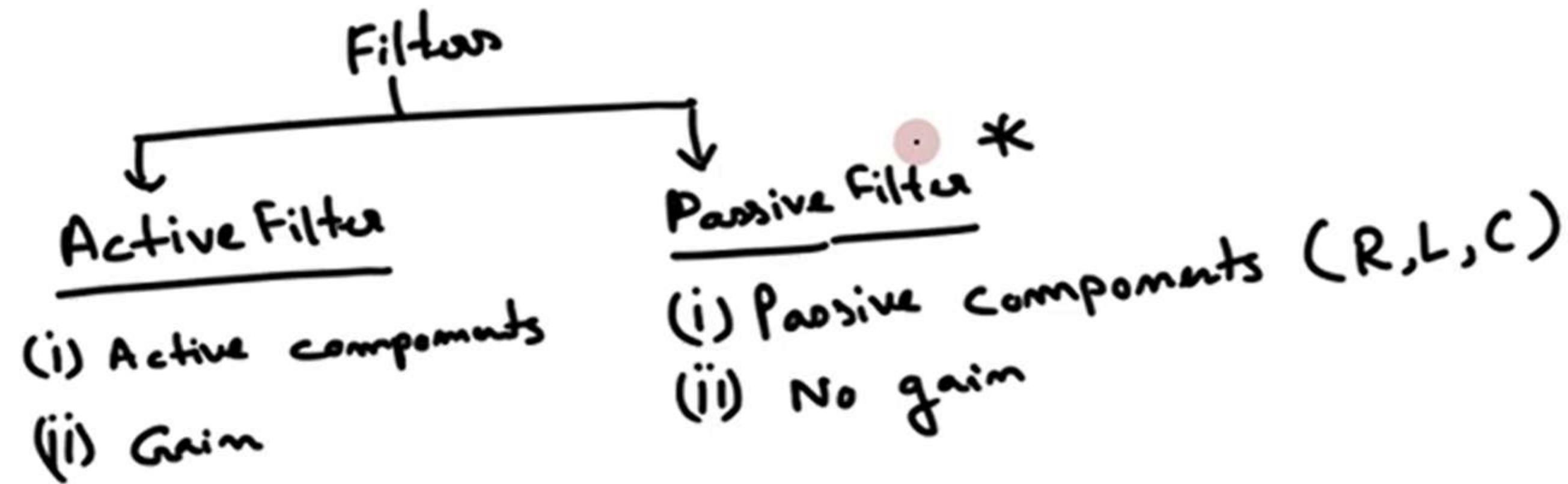



Passive Filters



Passive Filters

Passive filter

(i) Low pass filter (LPF)

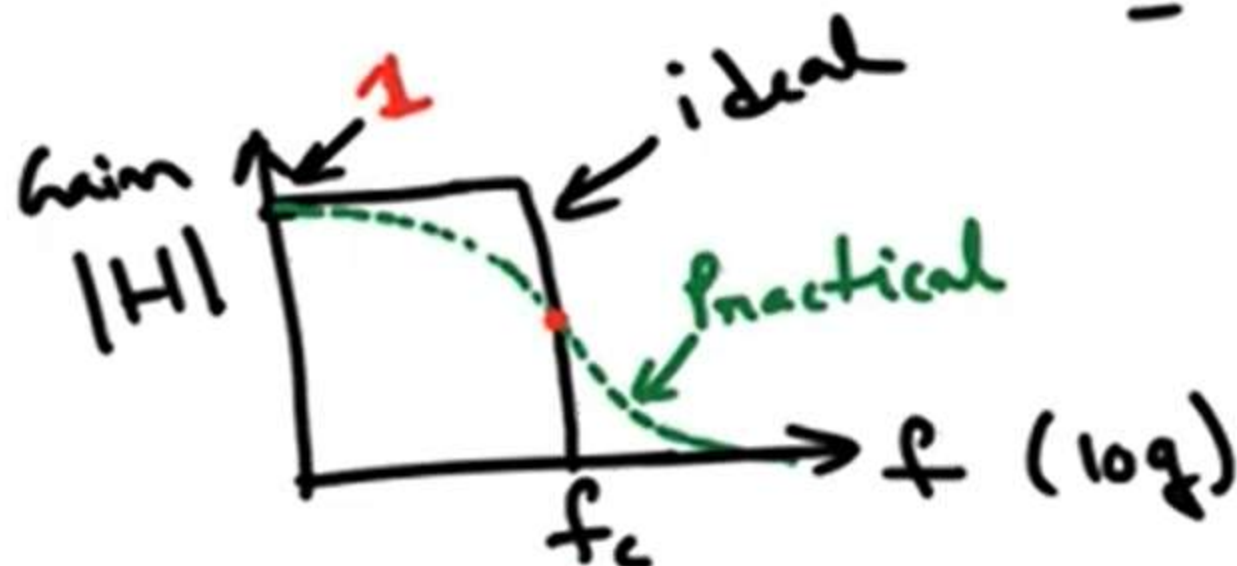


$$V_{in} \rightarrow \text{---} [F] \text{---} \rightarrow V_{out}$$


$$\text{Gain} = \frac{V_{out}}{V_{in}}$$

$$H = \frac{V_{out}}{V_{in}}$$


(ii) High Pass filter (HPF)

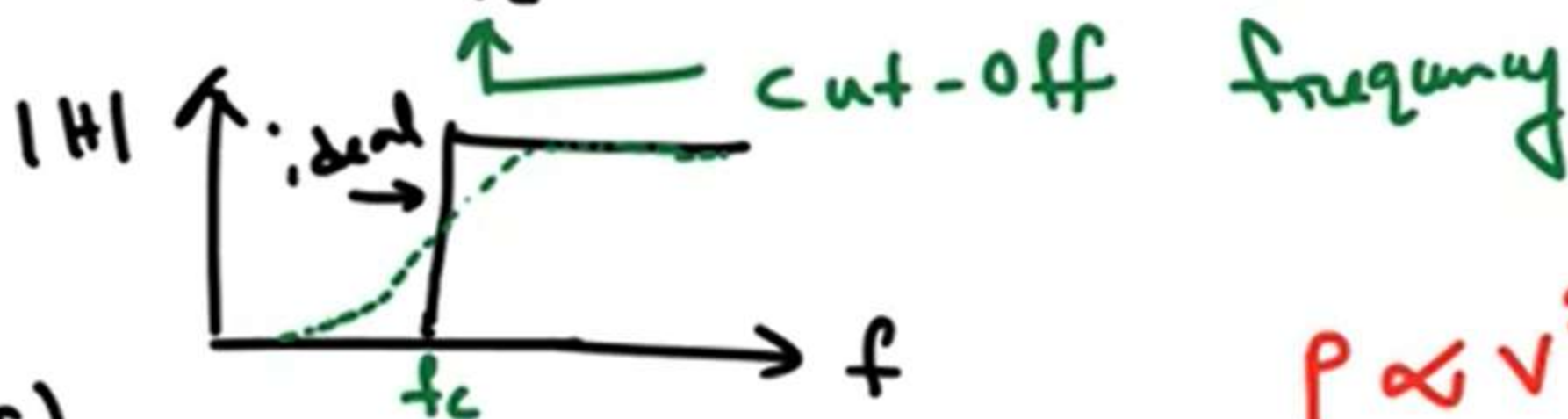

(iii) Band pass filter (BPF)

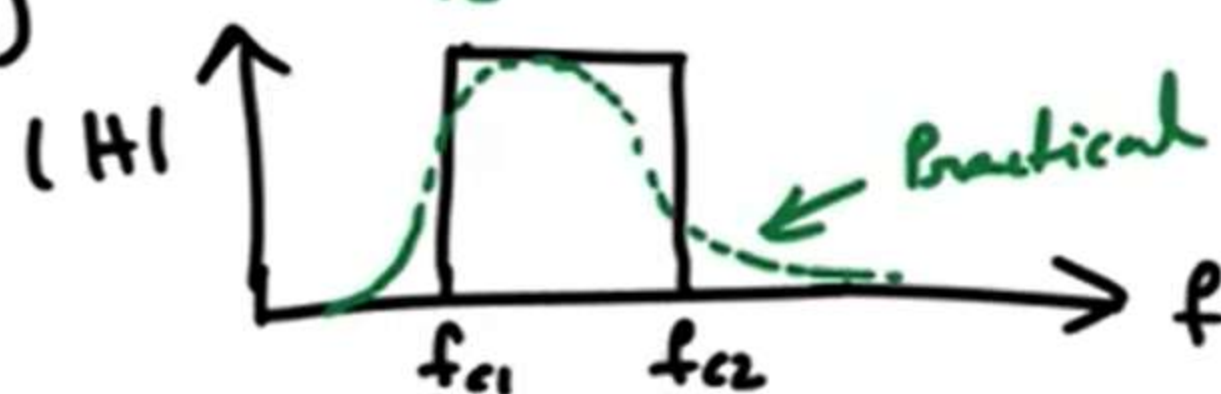

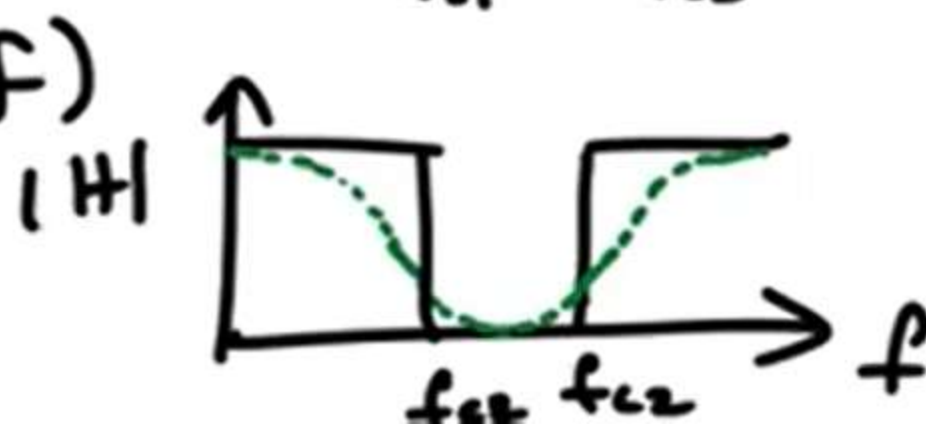(iv) Band-Stop Filter (BSF)
Band-Reject ~



$$P \propto V^2$$


$$V_{out} = \frac{1}{\sqrt{2}} V_{in}$$

$$|H| = \frac{1}{\sqrt{2}}$$

' f_c '

Passive Filters

Low Pass Filter (LPF)

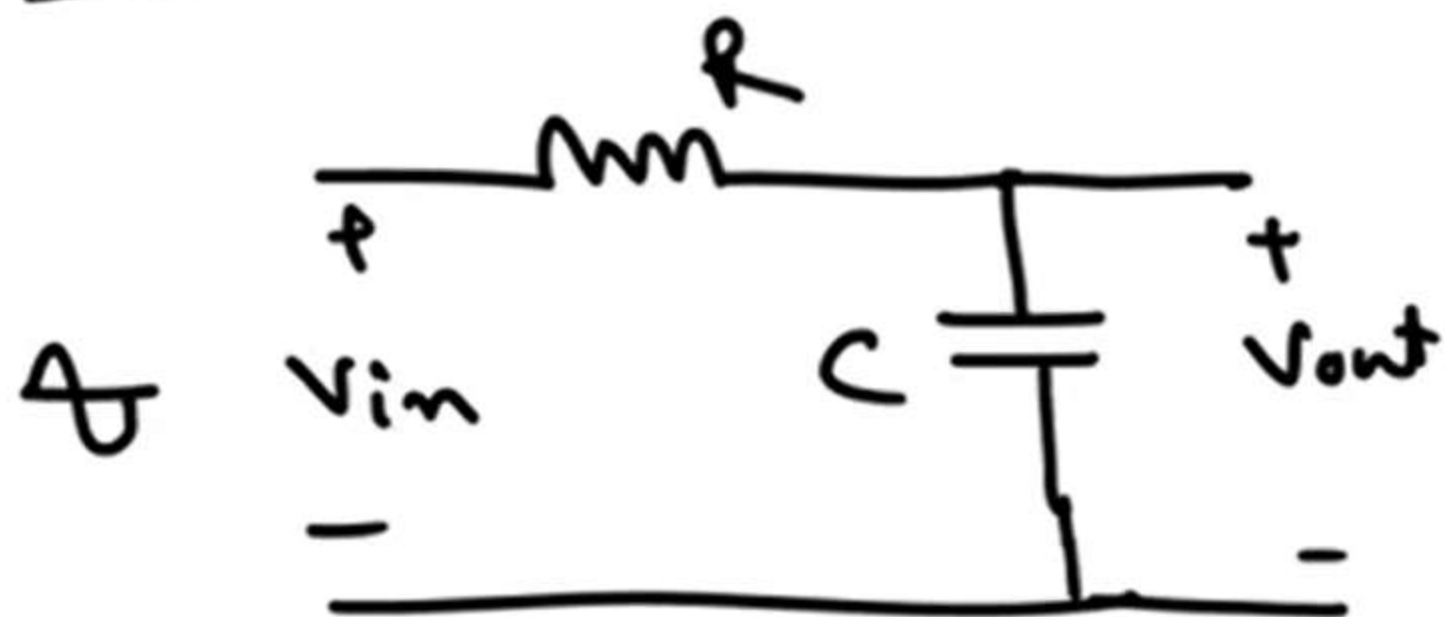

$$\omega_c = \frac{1}{RC} \quad \checkmark$$

$$|H(\omega)| = \frac{1}{\sqrt{2}} \rightarrow \text{cut-off}$$

$$\omega_c = \text{cut-off freq.} = \frac{1}{RC}$$

dB


$$V_{out} = \frac{Z_C}{R + Z_C} V_{in} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in}$$

$$= \frac{1}{1 + j\omega RC} V_{in}$$

$$H = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$$|H| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\omega = 2\pi f$$

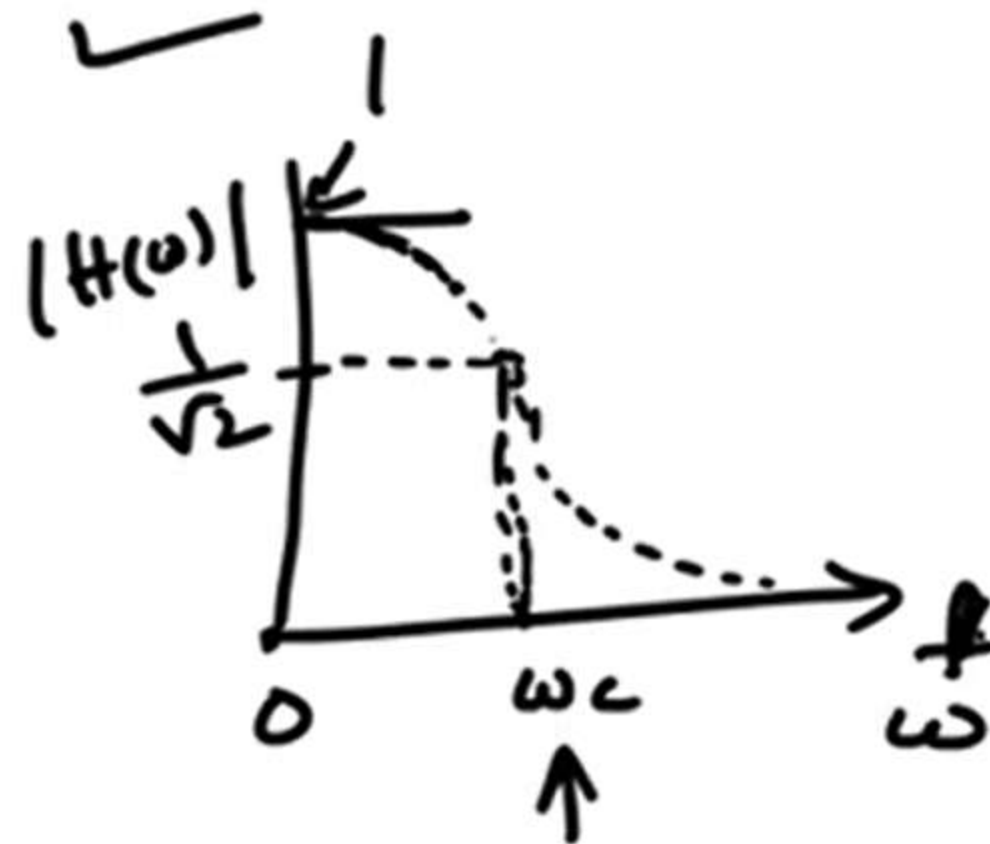

Passive Filters

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$\uparrow \left| \frac{V_{out}}{V_{in}} \right|$

$$10 \log \left(\frac{P_{out}}{P_{in}} \right) = 10 \log \left(\frac{V_{out}^2}{V_{in}^2} \right) = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$$

dB $\rightarrow 20 \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

\downarrow
??


$$\omega = \omega_c = \frac{1}{RC}$$

\uparrow
Cut-off
freq.

$$20 \log \frac{1}{\sqrt{1+1}}$$

$$= \underline{\underline{-3 \text{ dB}} \text{ freq.}}$$

$H(\omega)$
dB \uparrow

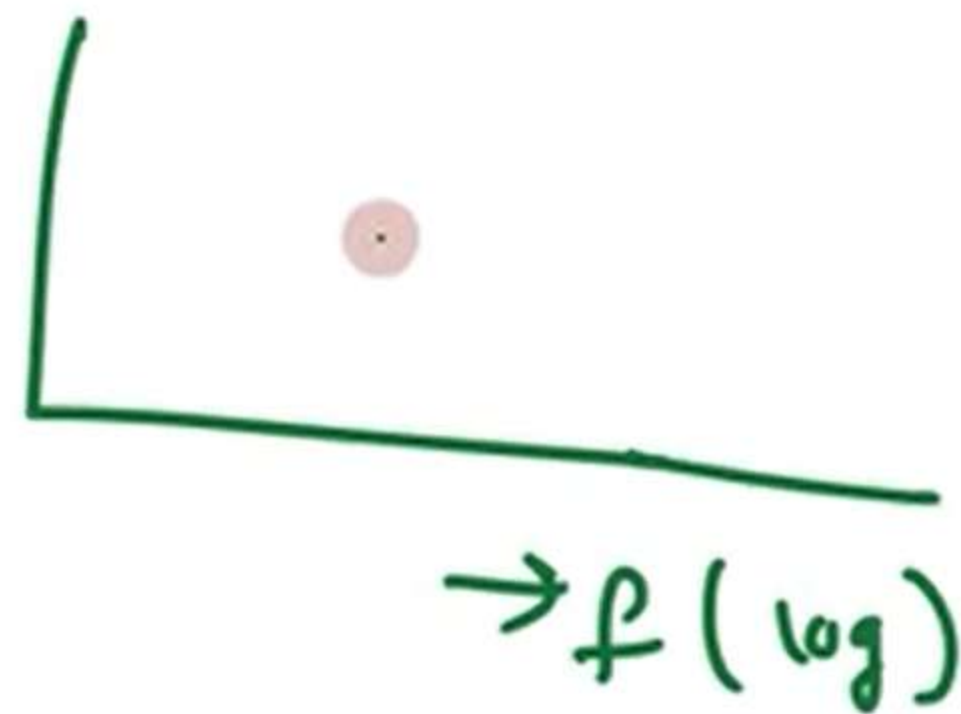

Passive Filters


V_o Phase??

$$|H(\omega)|_{dB} = 20 \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

at $\omega=0$, $|H(\omega)|_{dB} = 0$

$\omega = \omega_c$, $|H(\omega)|_{dB} = -3 \text{ dB}$

$\omega_c = 1/RC$

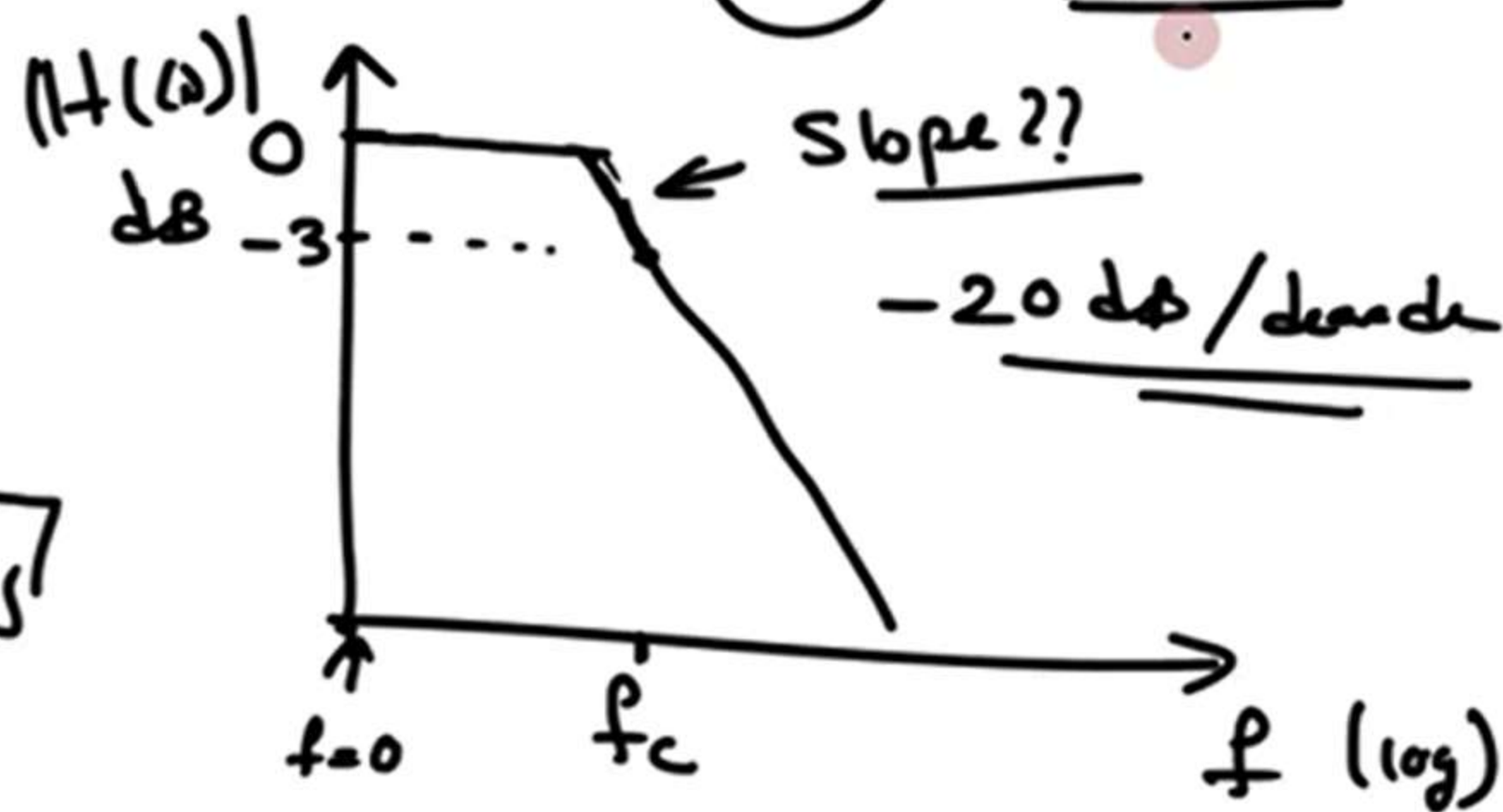

$$|H(\omega)|_{dB} = 20 \log \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}}$$

Slope = -20 dB/decade

$\omega = 10\omega_c$
decade

$$\begin{aligned} |H(\omega)|_{dB} &= 20 \log \frac{1}{\sqrt{1 + (\frac{10}{1})^2}} \\ &= 20 \log(\frac{1}{10}) = -20 \text{ dB} \end{aligned}$$

Passive Filters

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$\Phi = -\tan^{-1}(\omega RC)$$




phase
 $\Phi = -\tan^{-1}(\omega RC)$

$$\omega = 0, \Phi = 0$$

$$\omega = \omega_c = \frac{1}{RC}, \Phi = -\frac{\pi}{4}$$

$$\omega \rightarrow \infty, \Phi = -\frac{\pi}{2}$$

(Φ)

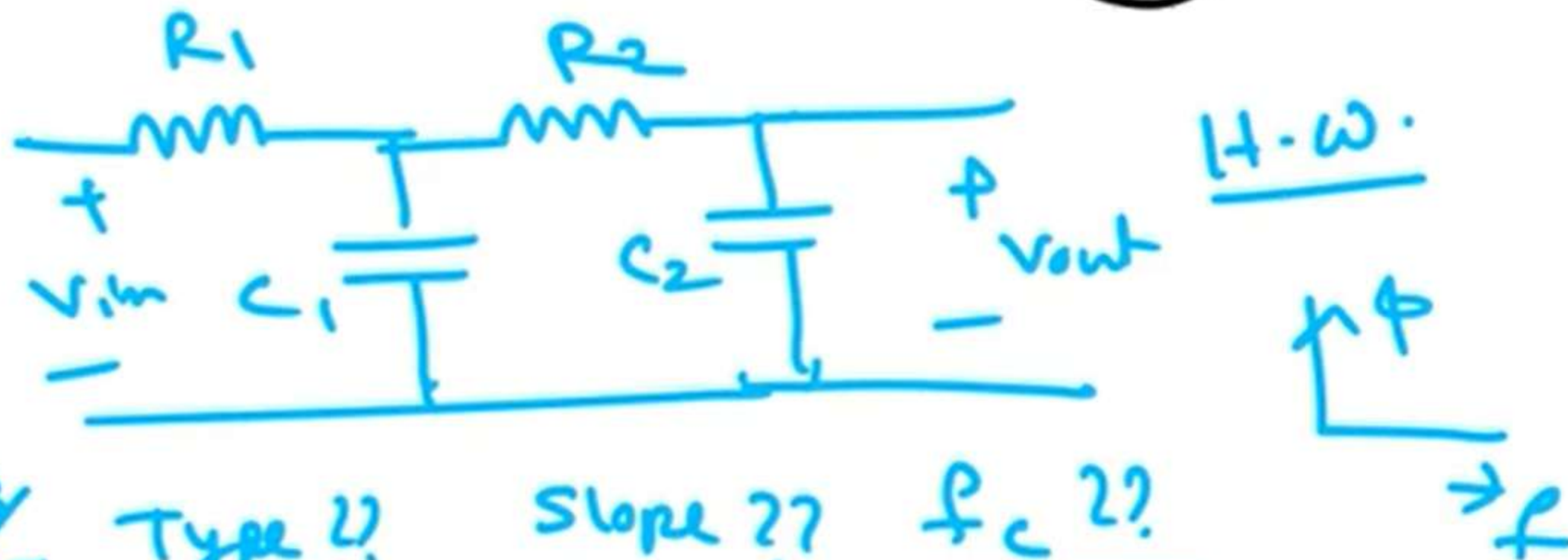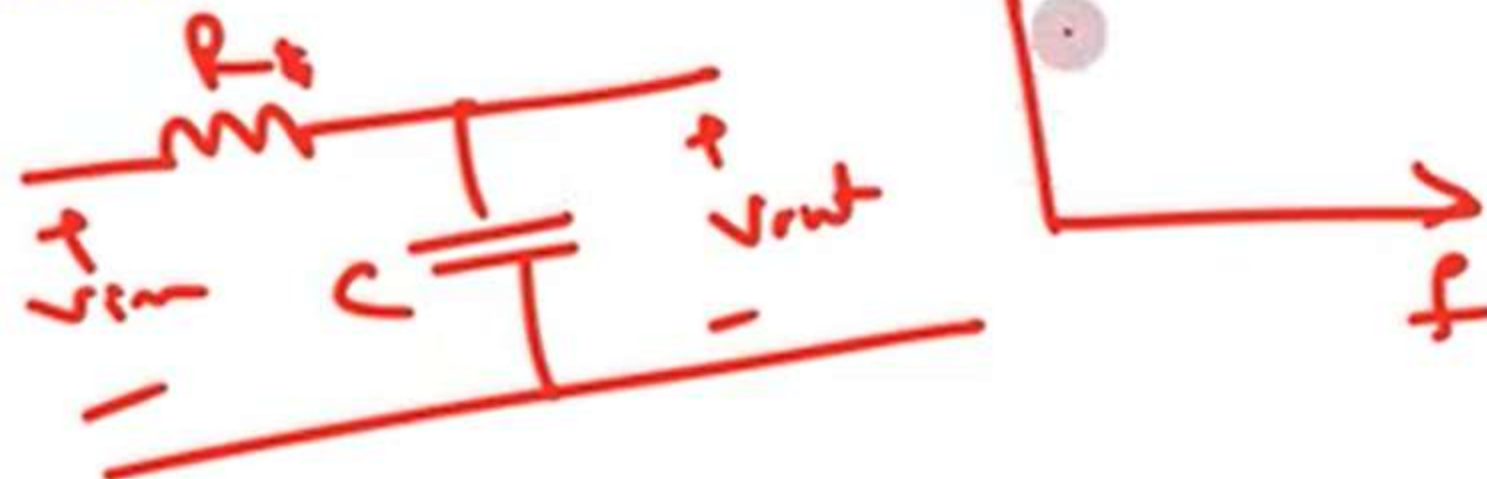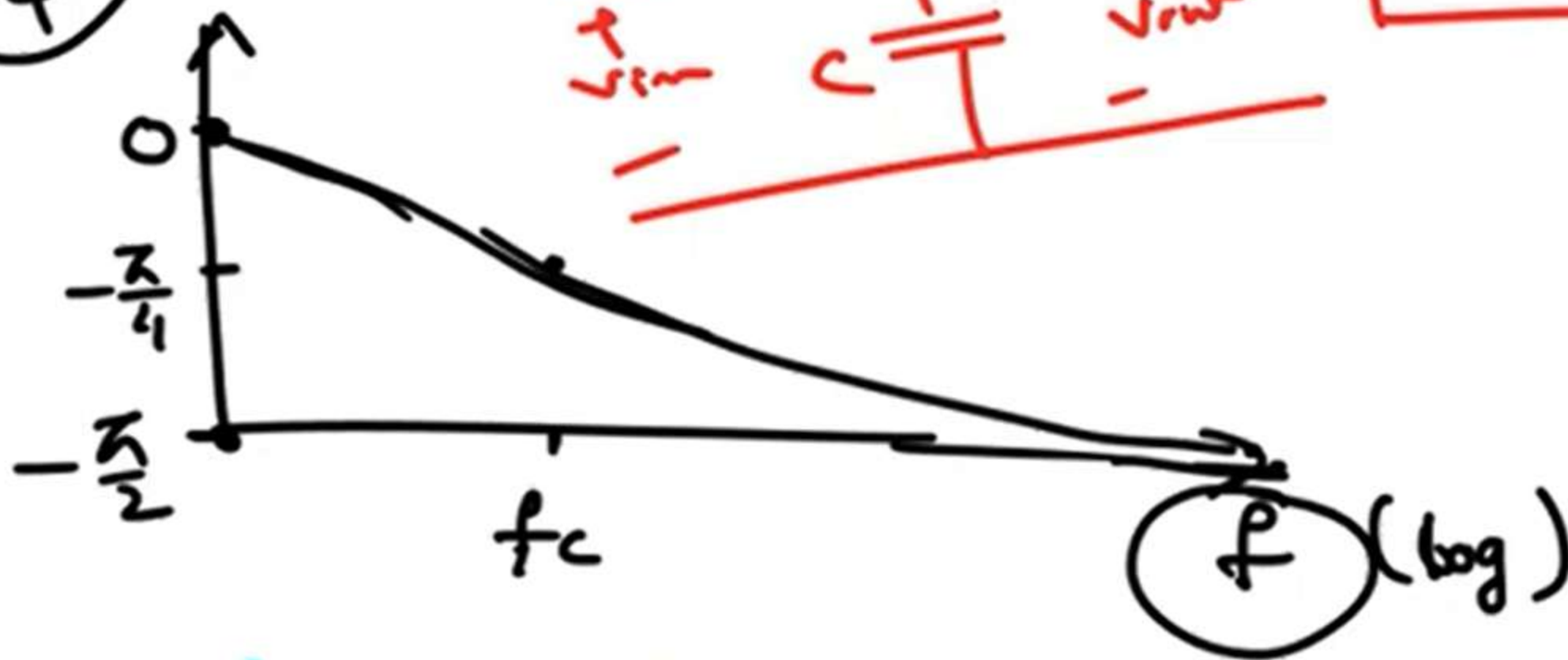

$\leftarrow -20 \frac{dB}{dec}$


Type 2?

Slope ??



fc ??

$\uparrow \Phi$
 $\rightarrow f$



Passive Filters

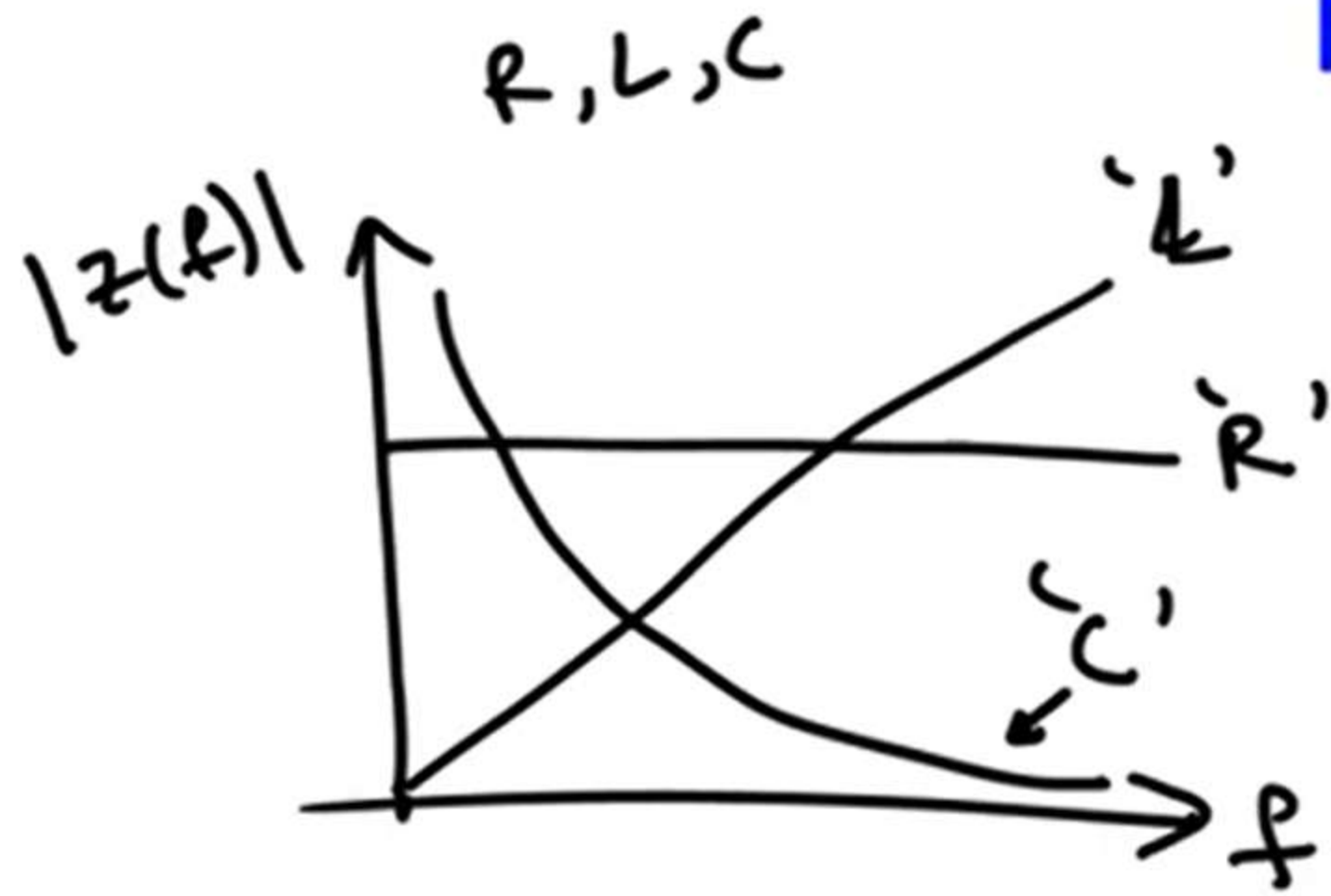
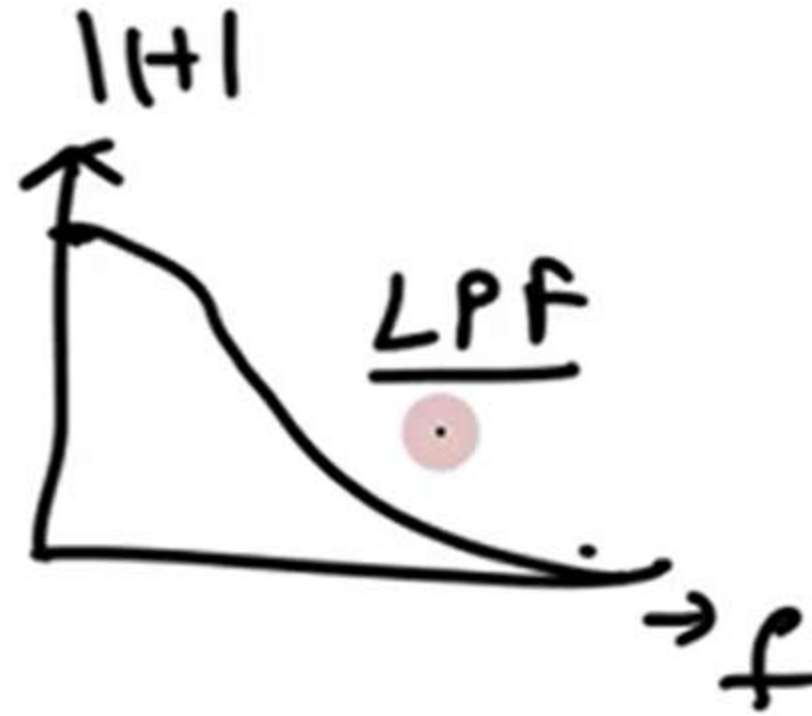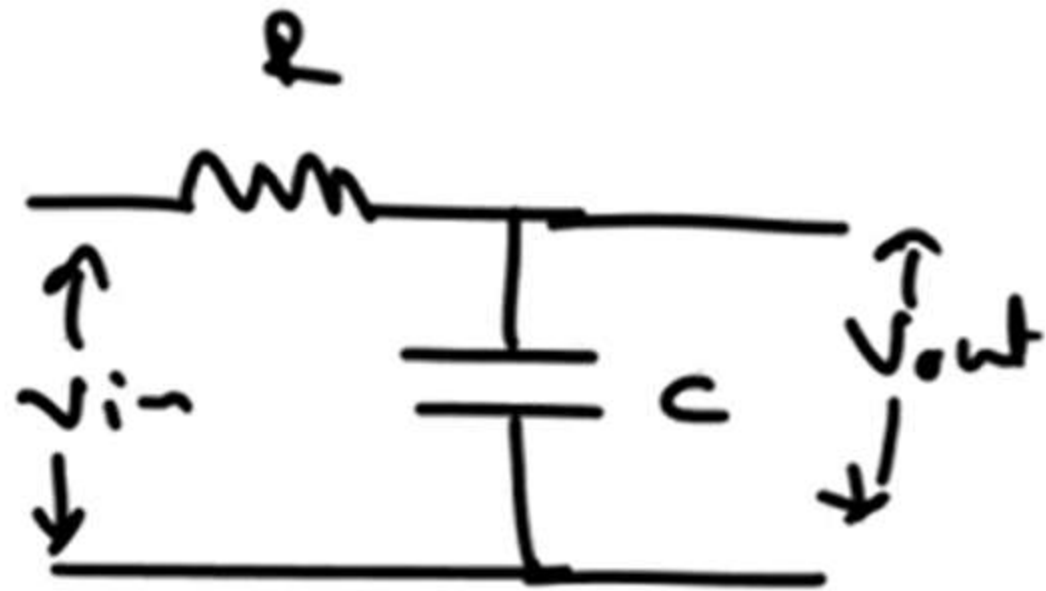
$$X_L = j\omega L$$
$$X_C = \frac{1}{j\omega C}$$




Passive Filters

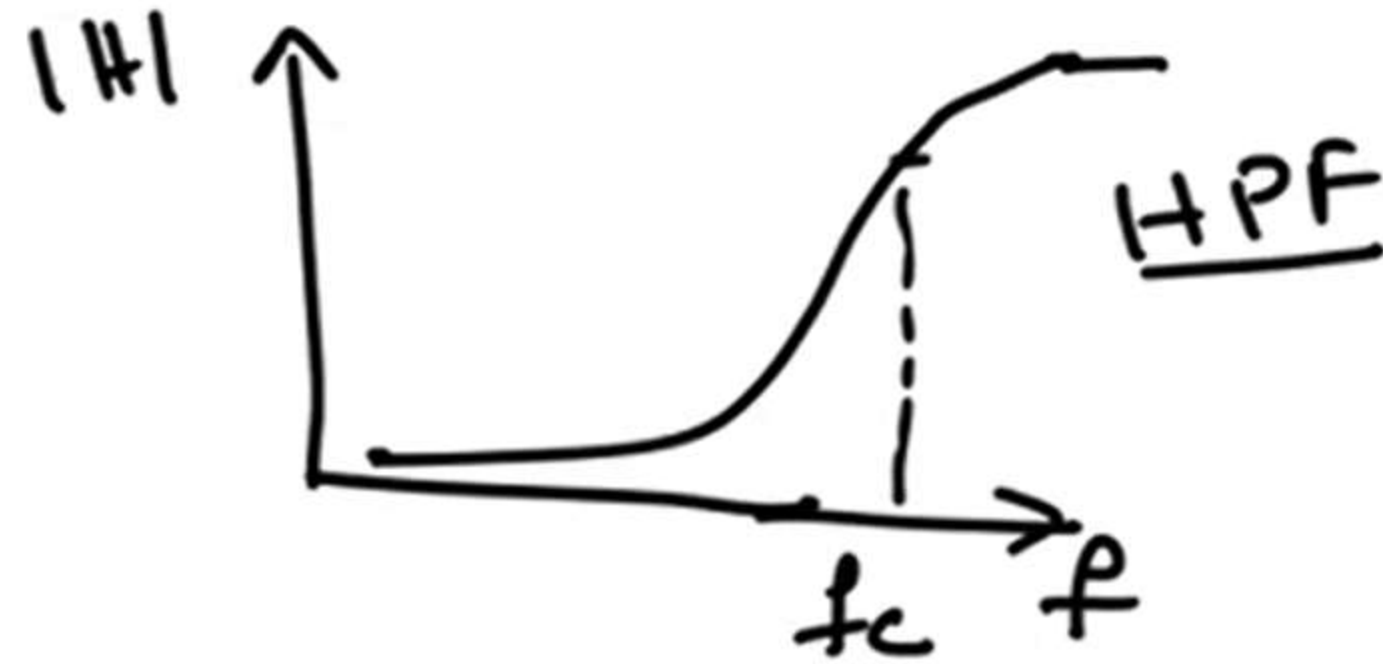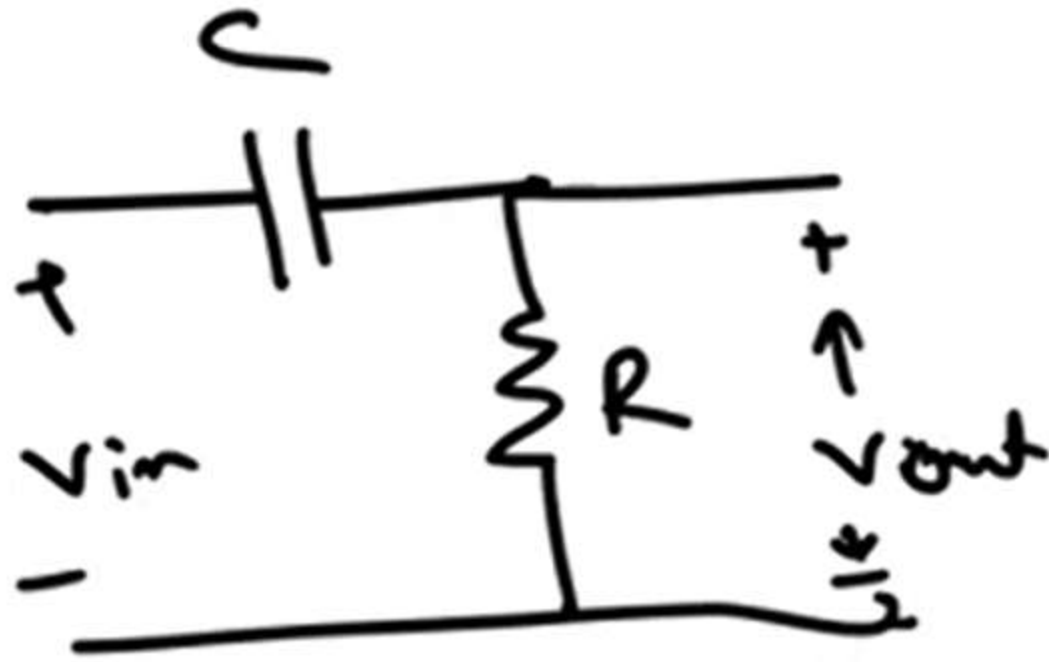

$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$= \frac{Rj\omega C}{Rj\omega C + 1}$$




$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R\omega C}{\sqrt{1 + R^2\omega^2 C^2}}$$

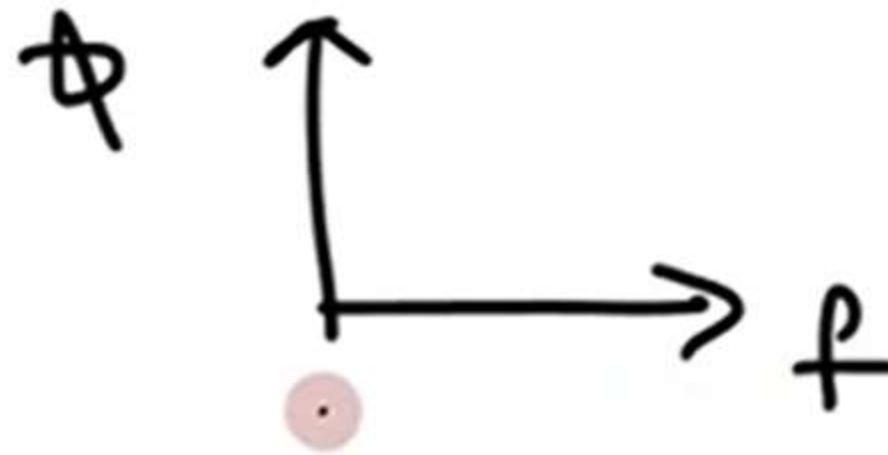





$$\omega = \frac{1}{RC} \quad , \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$$

↑
ω_c


Passive Filters

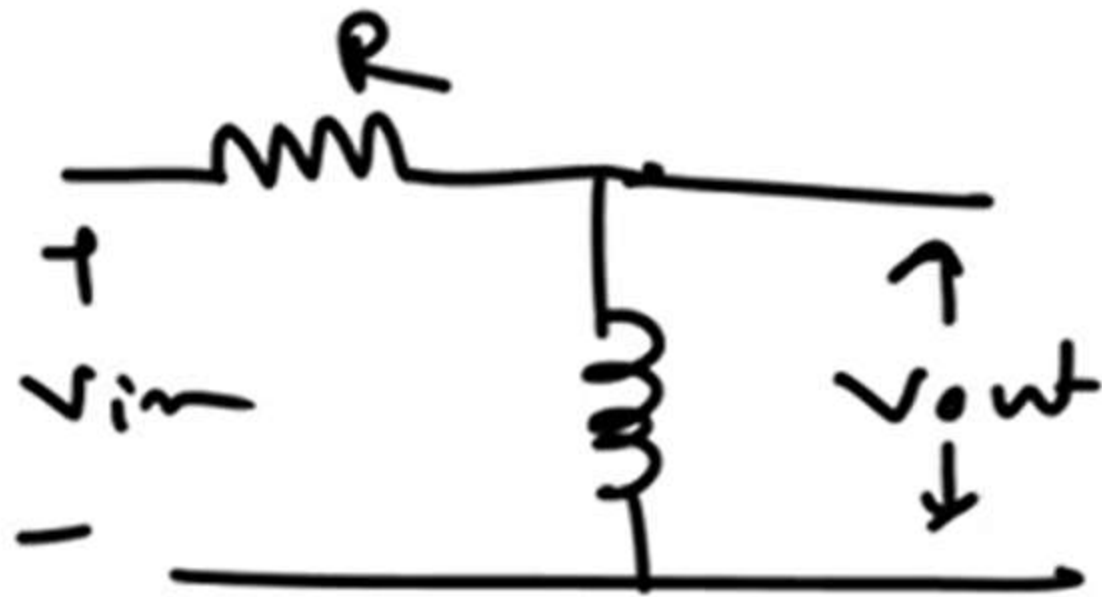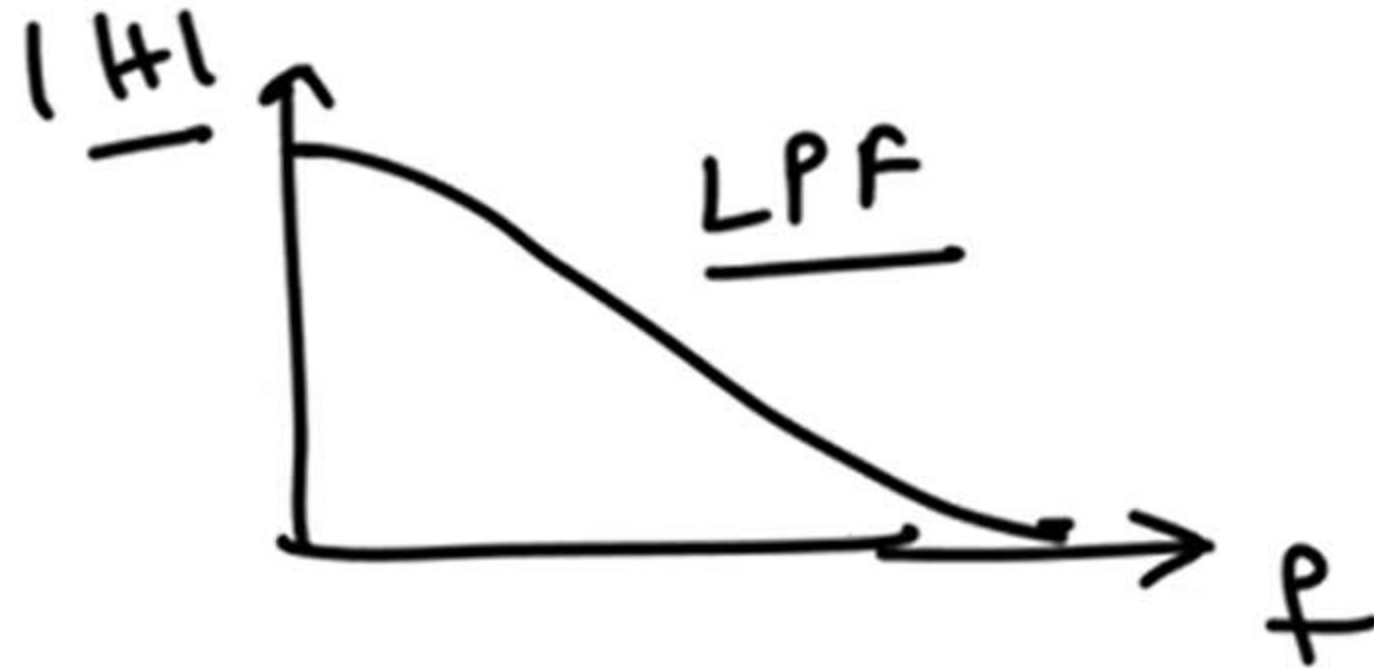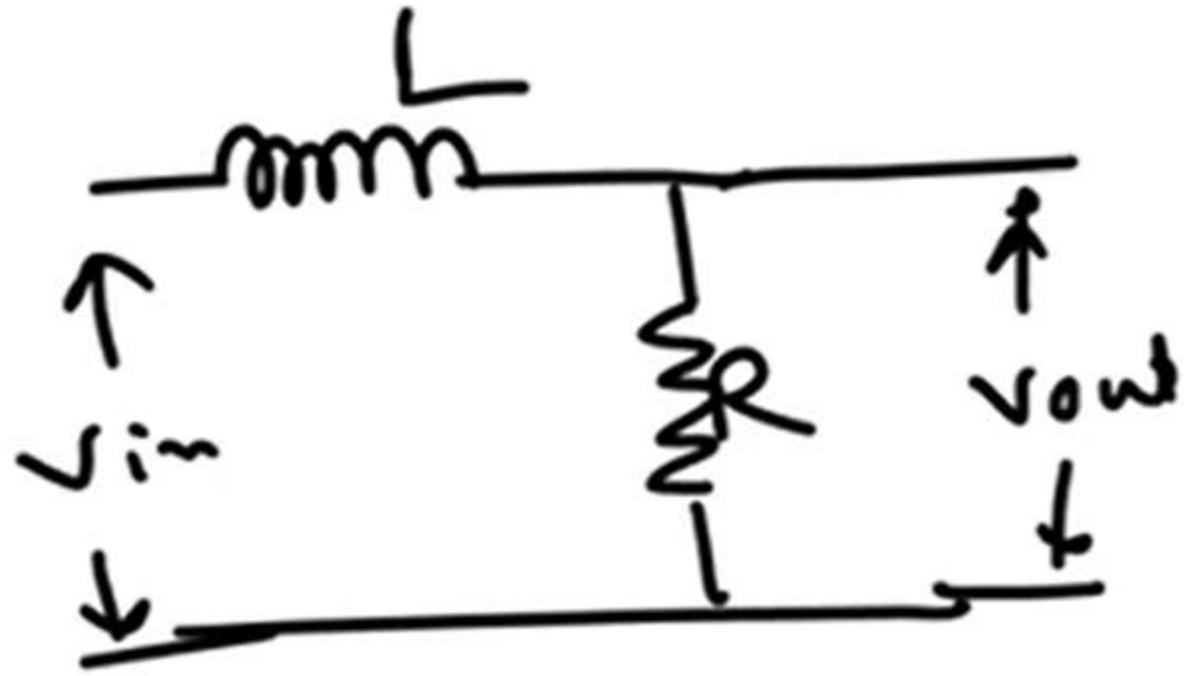

Passive Filters

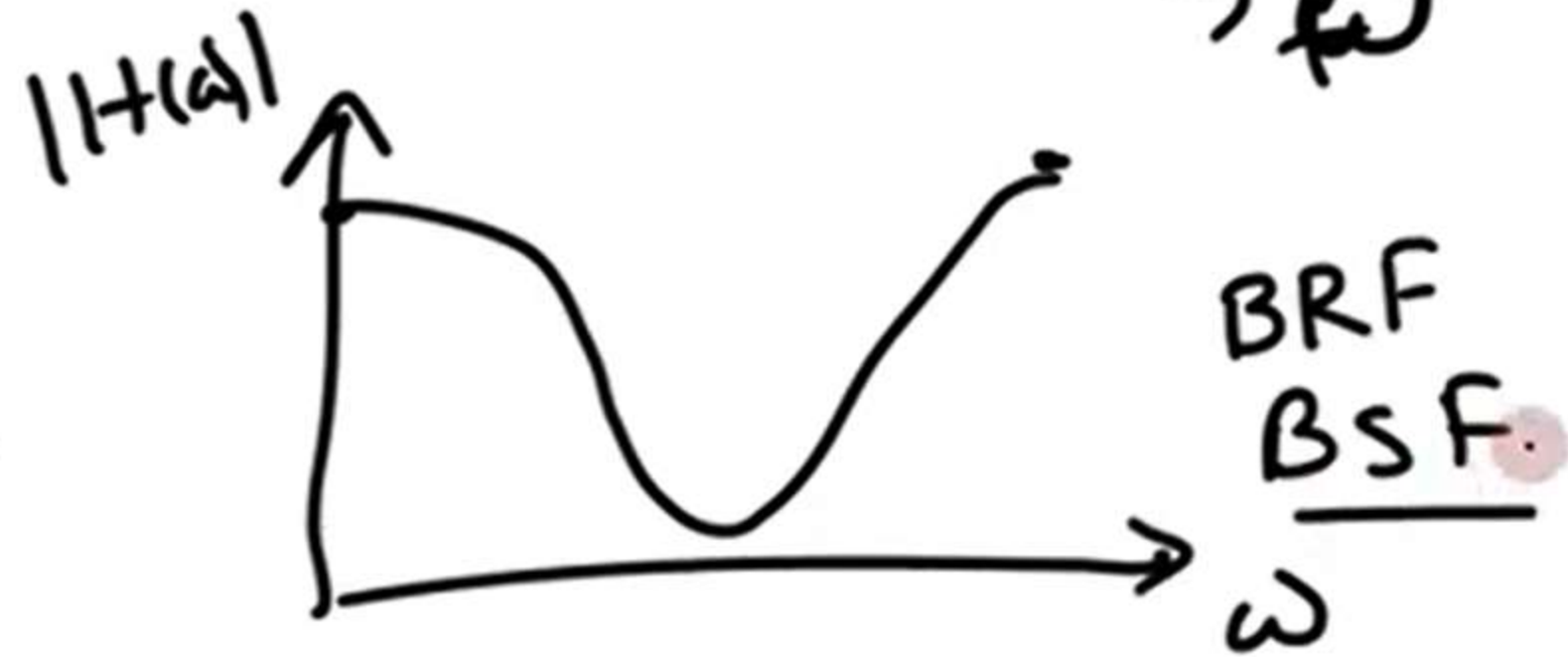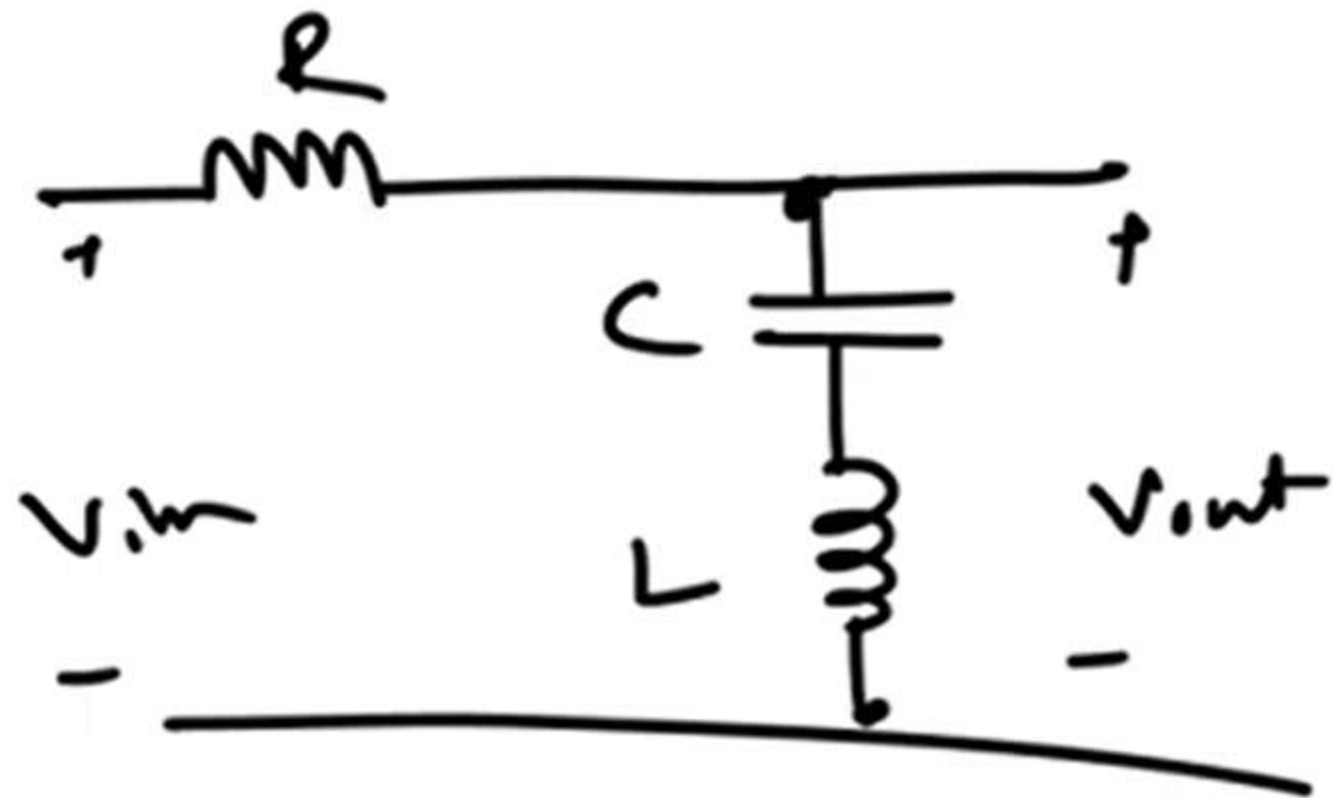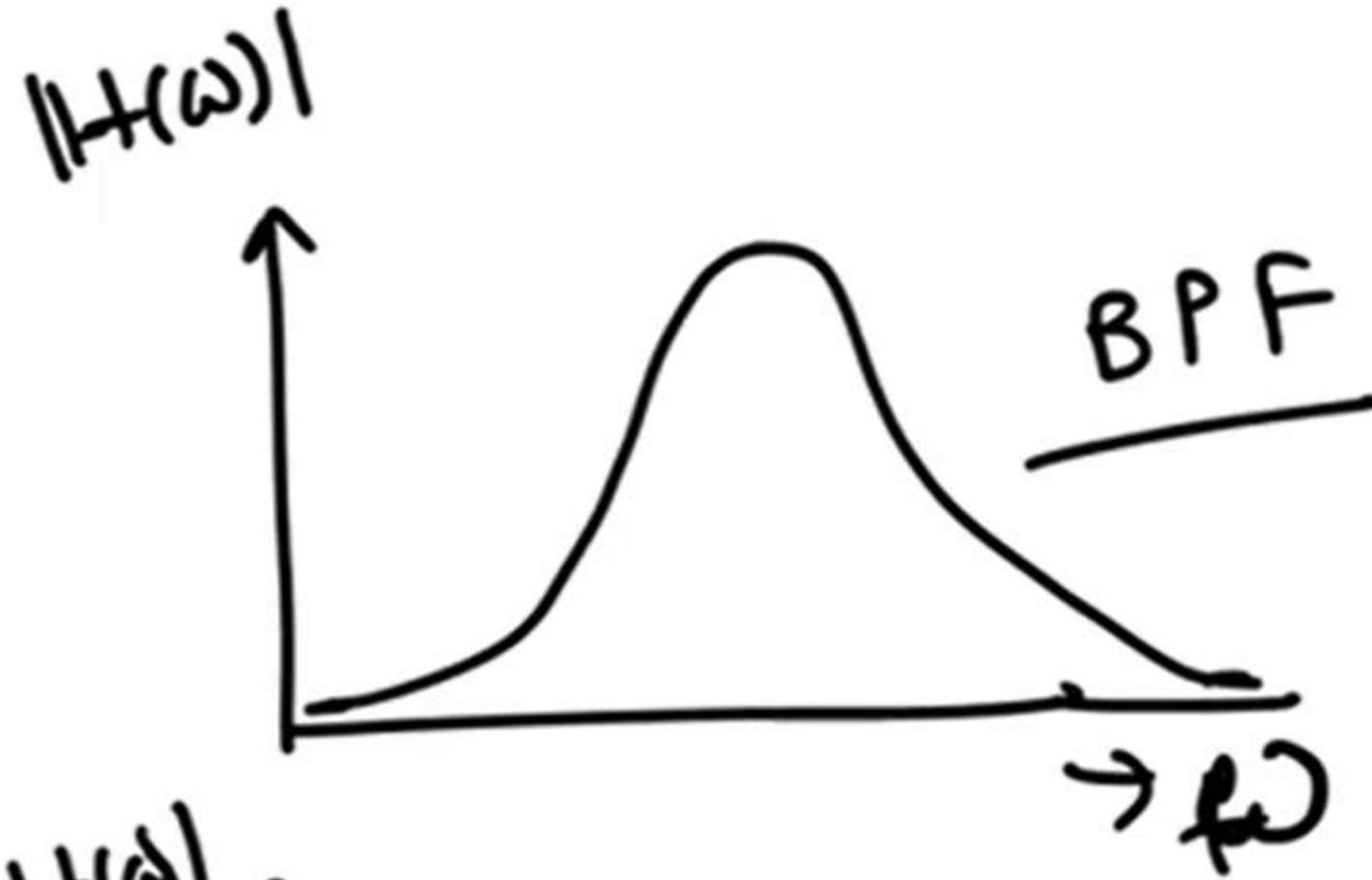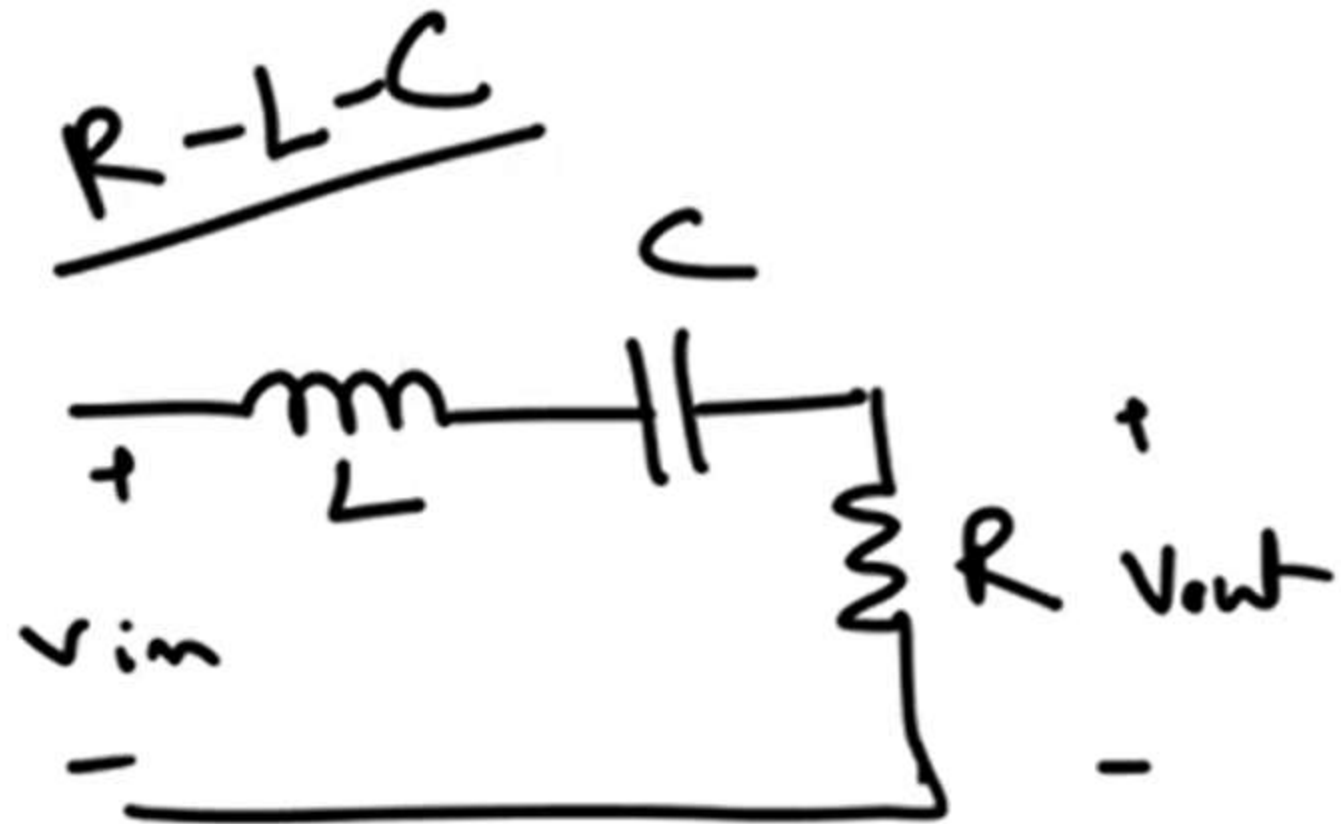

Passive Filters

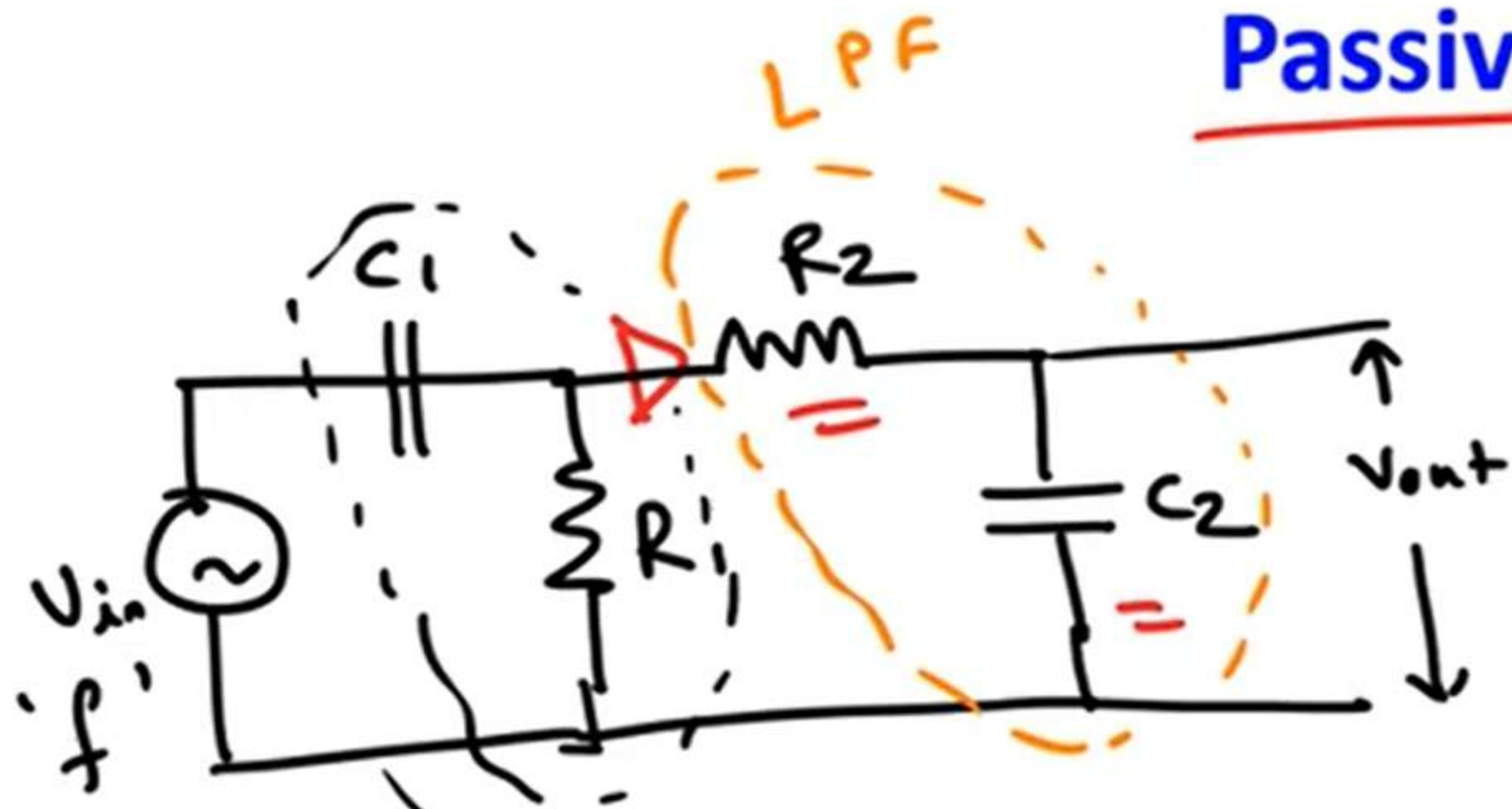

LPF $\rightarrow f_{c2}$
HPF $\rightarrow f_{c1}$ } $f_{c2} > f_{c1}$

