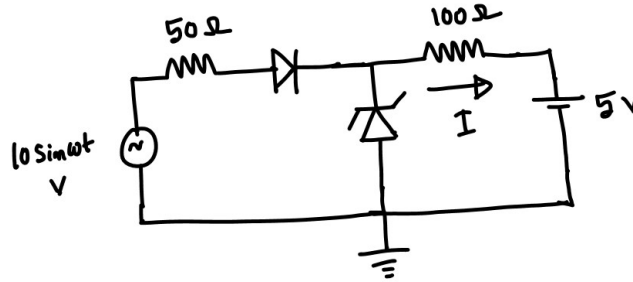



## Basic Electronics (Test – 1, Part - B)

[Please follow the instructions as mentioned in the Part-A of this question paper.]

5. In the following circuit find the magnitude of current  $I$  in mA if the input voltage is  $10 \sin(\omega t)$  V. Consider the diodes are ideal ( $V_f = 0$ ) and Zener breakdown voltage ( $V_z$ ) is 5 V. [2]



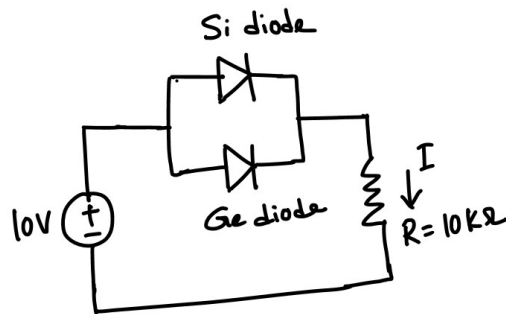6. Two different diodes are connected as shown the following figure. Estimate the current flowing through 10 kohm resistor. Given that, cut-in voltage for Si and Ge diodes are 0.7 V and 0.3 V respectively at  $T = 300$  K. [2]



7. For the following low pass filter circuit, estimate the cut-off frequency. Find the magnitude of the output voltage if the frequency of the input signal is 3 kHz. [1+2]

