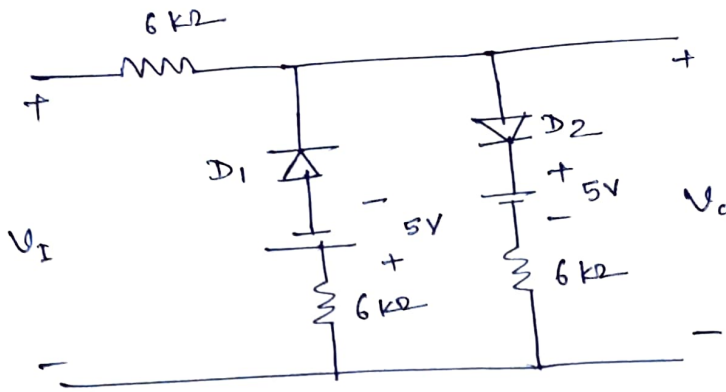


①



$$\frac{V_T = 0}{\text{given.}}$$

for, $-5V \leq V_I \leq 5V$ both D_1 and D_2 are OFF.

So, $V_O = V_I$ ①


output voltage for three conditions

for $V_I \leq -5V$, D_1 is only ON.


$$V_O = \frac{V_I - (-5V)}{6+6} \times 6 - 5V$$
 ①

$$V_O = \frac{1}{2} V_I - 2.5V$$

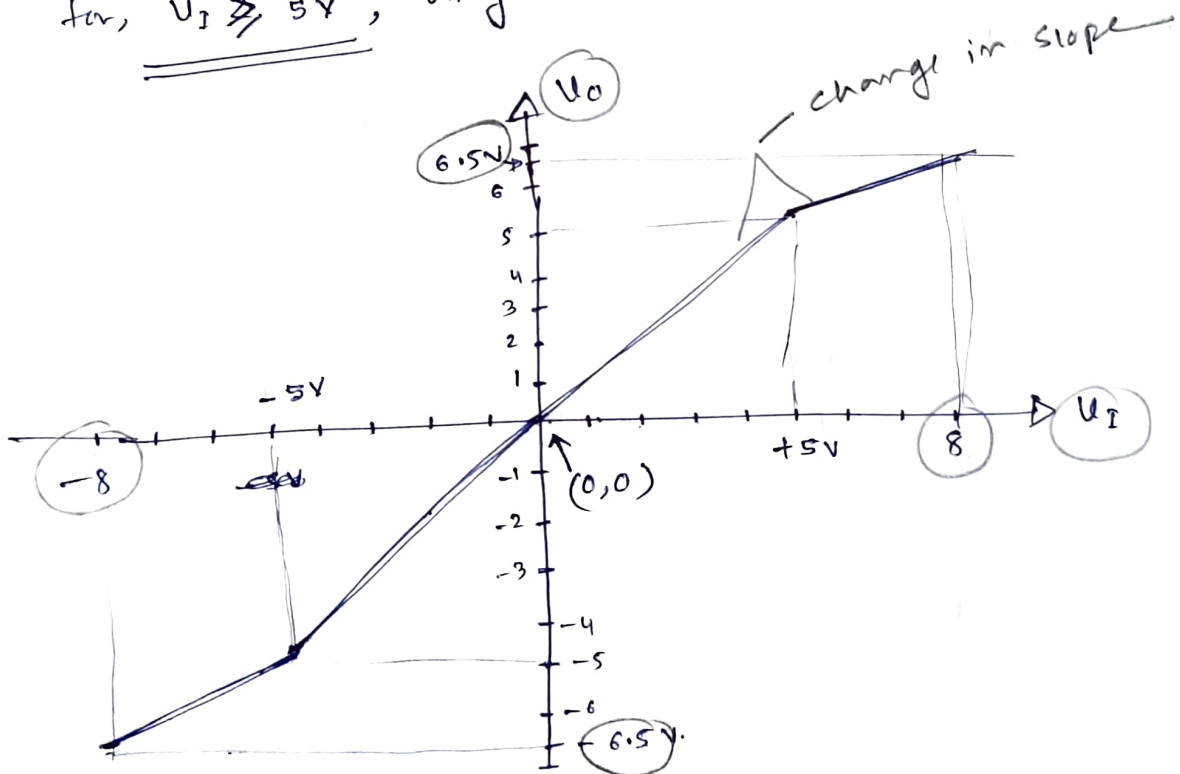for, $V_I \geq 5V$, only D_2 is ON, $V_O = \frac{1}{2} V_I + 2.5V$. ①



2

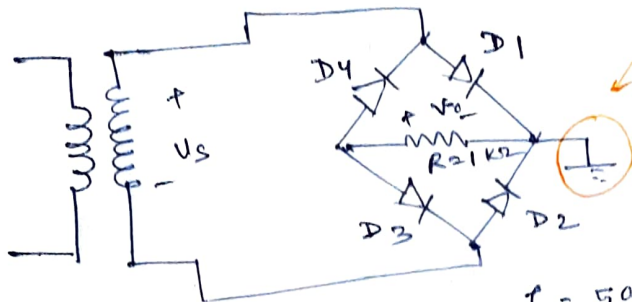

important for waveform plot of \$V_o\$
\$V_\gamma = 0.6\text{ V}\$

$$V_s = 5 \sin(314t) \text{ V}$$

$$f = 50 \text{ Hz}$$

$$T = \frac{1}{50 \text{ Hz}} = 20 \text{ ms}$$

$$\omega t = 314t$$

$$2\pi f = 314$$

$$f = 50 \text{ Hz}$$

$$V_s(t) = 5 \sin 314t$$

for each cycle 2 diodes will be ON, so voltage drop across diodes = $2 \times 0.6 \text{ V} = 1.2 \text{ V}$.


diodes will conduct, only when $V_s > 1.2 \text{ V}$.

Let's find t_{p-off}

$$5 \sin 314t_{p-off} = 1.2$$

$$314t_{p-off} = \sin^{-1}\left(\frac{1.2}{5}\right)$$
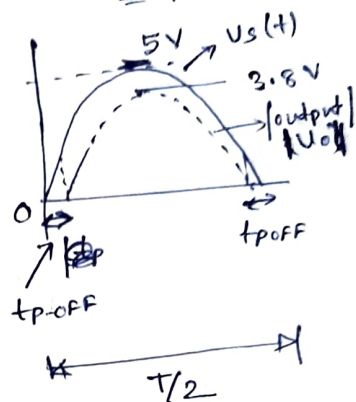
$$t_{p-off} = \frac{0.237}{314} \approx 0.77 \text{ ms}$$




for one time period (T) of the i/p signal, t_{p-off} occurs four times.

So, the time duration during which diodes are conducting = $T - 4t_{p-off}$

$$= 20 - 4 \times 0.77$$

$$= 16.92 \text{ ms}$$

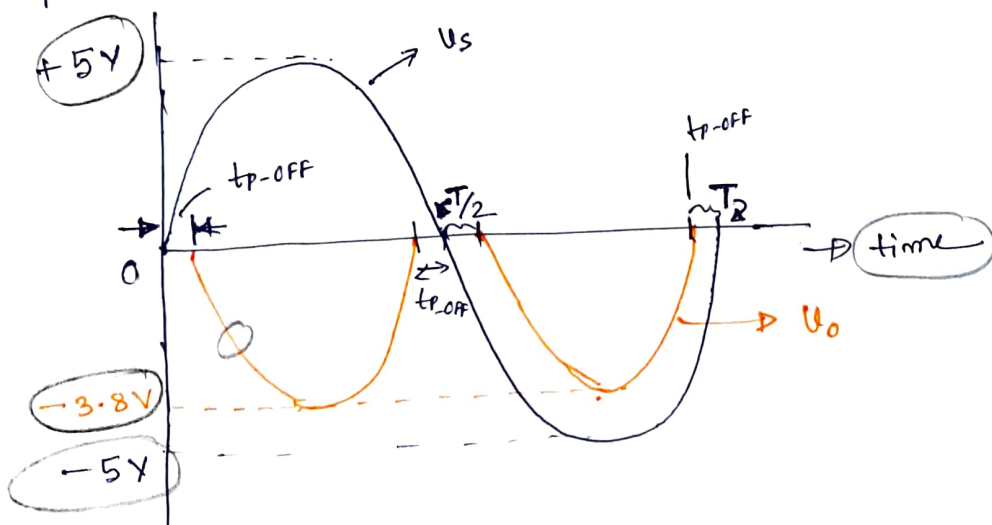

$$\text{PIV of diode } D_3 = |V_{s \text{ max}}| - V_\gamma = 5 - 0.6$$

$$= 4.4 \text{ V}$$

3) n-type semiconductor $n \gg p$
 $n \approx N_D$

resistivity $\rho = 0.65 \Omega\text{-cm}$

conductivity $\sigma = \frac{1}{\rho} = \frac{1}{0.65} = 1.538 (\Omega\text{-cm})^{-1}$

$$\sigma = N_D q \cdot \mu_n \quad ; \quad \mu_n = 1250 \text{ cm}^2/\text{V-s}$$


$$N_D = \frac{\sigma}{q \times \mu_n} = \frac{1.538}{1.6 \times 10^{-19} \times 1250}$$

$$\boxed{N_D = 7.69 \times 10^{15} \text{ cm}^{-3}}$$


$$J = \sigma E$$

$$160 \text{ A/cm}^2 = 1.538 \times E$$
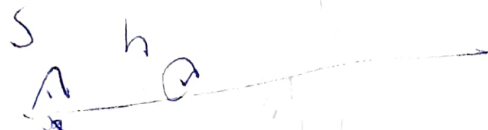
$$E = \frac{160}{1.538} = \boxed{104.03 \text{ V/cm}}$$




(4)

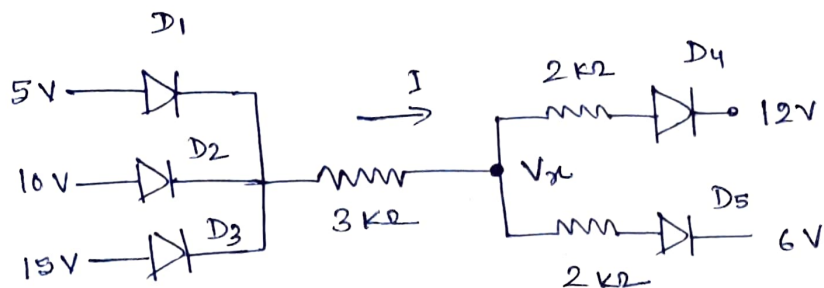

for D_1 , D_2 and D_3 , cathode is common and $V_F = 0$ given, so
only D_3 will be ON.

then ckt. reduces to,

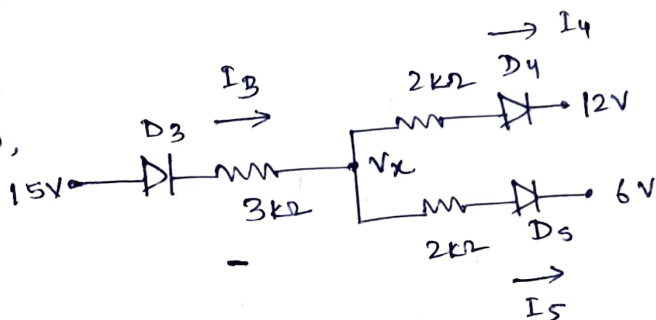

Assuming, D_4 and D_5 both are in ON state,

KCL at node 'x',

$$I_3 = I_4 + I_5$$


$$\therefore \frac{15 - V_x}{3} = \frac{V_x - 12}{2} + \frac{V_x - 6}{2}$$

$$V_x = 10.5V$$

for our assumption to be true, $V_x > 12V$.

So, D_4 is OFF


then the ckt further reduces to.

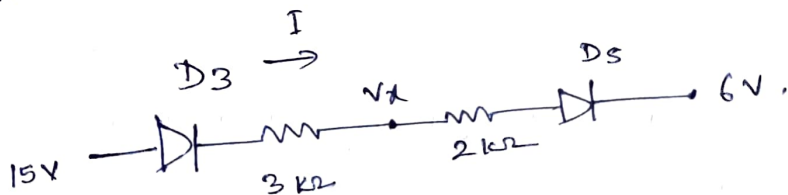

$$\text{So, } I = \frac{15 - 6}{3 + 2} = \boxed{1.8 \text{ mA.}}$$

Ans.

5

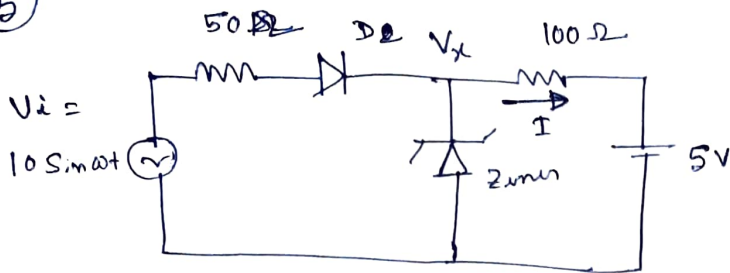


if, $V_i < 5V$, then both diodes are OFF, $I = 0$, $V_x = 0.5V$.

When, $V_i > 5V$, then diode D is ON.

and Zener diode is in breakdown.

equivalent ckt

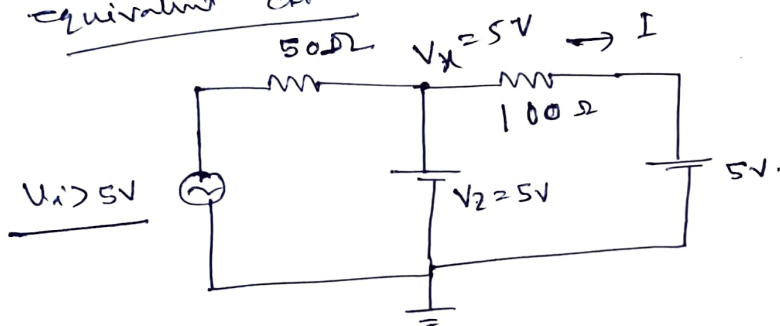


again here,

$I = 0$

Si diode

6

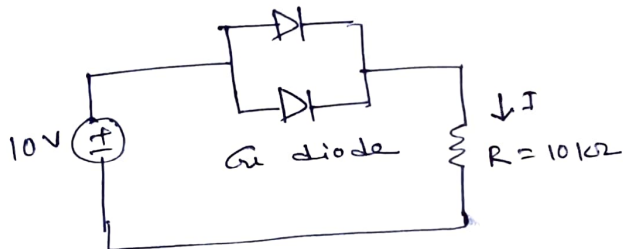


$V_{x_{Si}} = 0.7V$, $V_{x_{Ge}} = 0.3V$.

So, both diodes are in forward bias.

but as, $V_{x_{Ge}} = 0.3V$. equiv ckt, Ge diode will be conducting most of amt.

$I = \frac{(10 - 0.3)V}{10k\Omega} = 0.97mA$

7

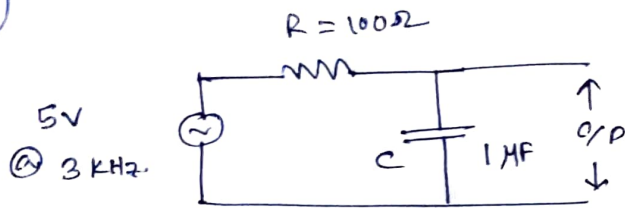

$$\text{Cut-off } f_{\text{cut}} = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 100 \times 1 \times 10^{-6}} = 1.592 \times 10^3 \text{ Hz}$$

$$= \underline{1.592 \text{ kHz.}} \quad \text{Ans}$$

$$V_{\text{out at } 3 \text{ kHz}} = \frac{|X_c|}{\sqrt{R^2 + X_c^2}} \times V_{\text{in}}$$

$$\Rightarrow X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 3 \times 10^3 \times 1 \times 10^{-6}}$$

$$X_c = 53.07 \Omega$$

$$V_{\text{out at } 3 \text{ kHz}} = \frac{53.07}{\sqrt{100^2 + 53.07^2}} = \underline{0.46 \text{ V.}} \quad \text{Ans}$$