

## Basic Electronics (Test – 2, Part - A)

- **Instructions:** Please mention these on the first page of your answer script (your name, roll no., subject name, your signature and date); Insert page no. in every page; The final answer(s) (numerical values with unit) should be enclosed within a box ; Show the necessary steps in your answers and with supported explanation; All waveform sketches / diagrams must be neatly drawn and clearly labelled; At the end of this test, you have to upload a single PDF file of your hand-written answer script (Max file size 10 MB); Please note that, this question paper has two parts: Part A and Part B; For any doubt, please feel free to ask the instructor during the test.

Consider the following whenever required,

For BJT,  $|V_{BE\_ON}| = 0.7\text{ V}$ ;  $V_A$  is very high if not stated explicitly

For diode,  $V_f = 0.7\text{ V}$  and forward resistance is negligible

**Symbols have their usual meaning**

**Q1.** Find the Q-point ( $V_{CEQ}$  and  $I_{CQ}$ ) for the following circuit (Fig. 1). Given that CE current gain of the BJT is 200. [4]

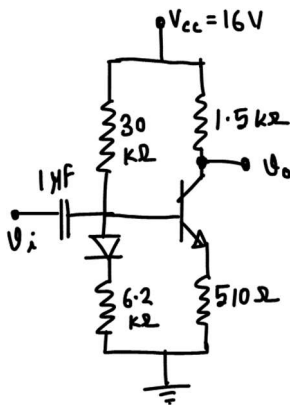


Figure 1

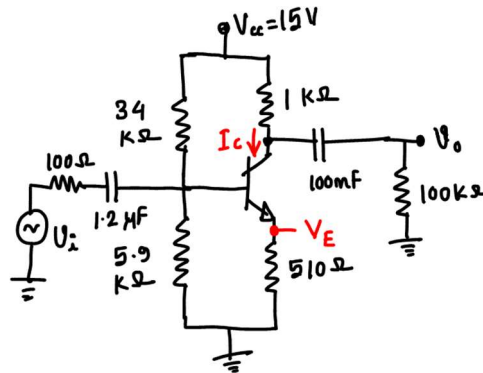


Figure 2

**Q2.** For the amplifier circuit shown in Fig. 2,  $\beta = 200$  and  $V_A = 150\text{ V}$ . Find  $I_C$  and  $V_E$  as indicated in the figure. Estimate the small signal parameters ( $g_m$ ,  $r_{\pi}$ ,  $r_o$ ) and evaluate the small-signal gain of the amplifier. Ignore the Early effect during DC calculations. [2+3+3]

**Q3.** Find the value of  $R_B$  and  $R_C$  to establish the Q-point as indicated in the transistor characteristics. [4]

