



# INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR

## Mid-Autumn Semester Examination 2022-23

Date of Examination: \_\_\_\_\_ Session: (FN/AN) \_\_\_\_\_ Duration: 2 hrs Full Marks: 100  
Subject No.: EC 21201 Subject: Basic Electronics  
Department/Center/School: Electronics & Electrical Communication Engg  
Specific charts, graph paper, log book etc., required No  
Special Instructions (if any): \_\_\_\_\_

Answer all questions. The marks for the individual parts of a question are indicated on the right.

1. A half-wave rectifier such as shown in Figure 1 has a load of  $R = 2 \text{ k}\Omega$ . The input is a 120 V (rms), 60 Hz signal and the transformer is a 10:1 stepdown transformer. The diode has a cut-in voltage of  $V_\gamma = 0.7 \text{ V}$  with  $r_f = 0 \Omega$ .
- (a) What is the peak output voltage? [3]
  - (b) Determine the peak diode current. [2]
  - (c) What is the fraction (percent) of a cycle that  $v_o > 0$ . [6]
  - (d) Determine the average output voltage. [6]
  - (e) Find the average current in the load. [3]

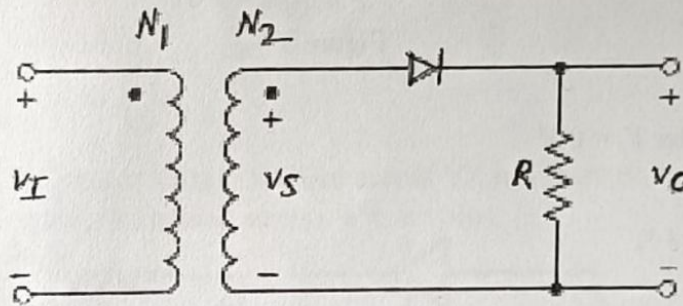


Figure 1

2. (a) Determine the steady-state output voltage  $v_o$  for the circuit in Figure 2(a), if the input waveform is as shown in Figure 2(b). Assume that the diode cut-in voltage is  $V_\gamma = 0$ . [8]

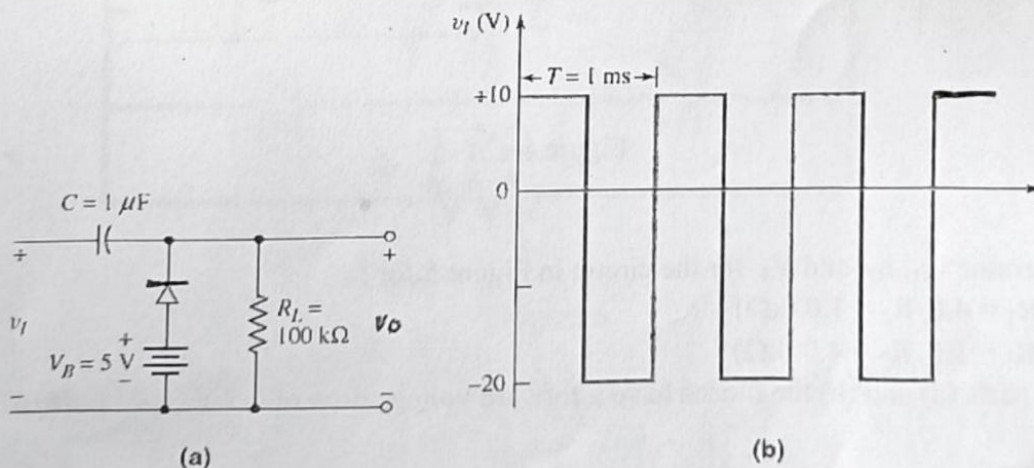


Figure 2

(b) Draw the output voltage versus time waveform for the following circuits in Figures 3 and 4 with the waveforms appropriately labelled for the input signal shown on the left.

[6]

I. Consider  $V_f = 0.6 \text{ V}$

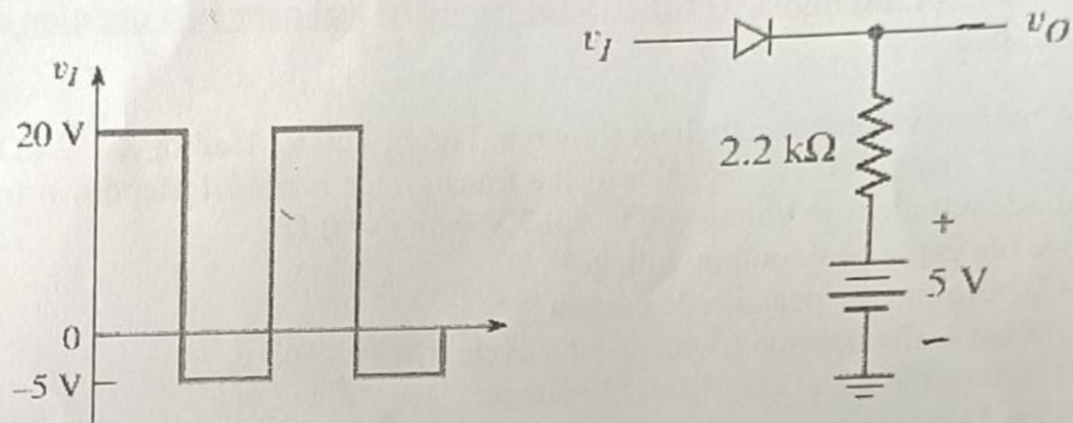


Figure 3

II. Consider  $V_f = 0 \text{ V}$

[6]

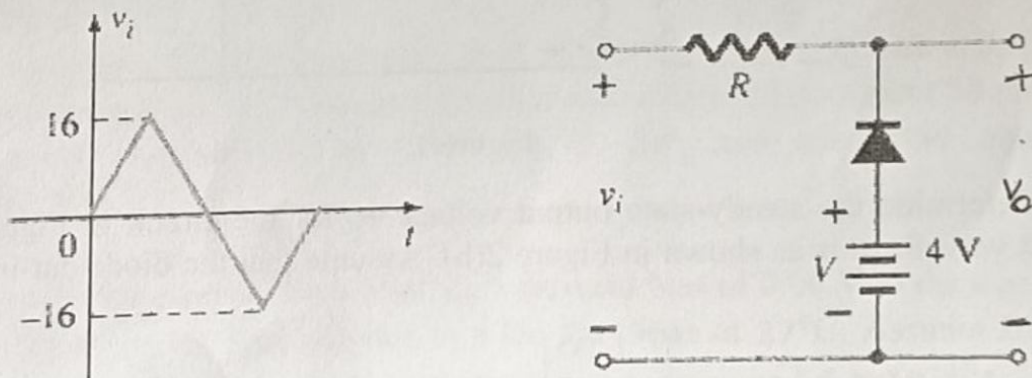


Figure 4

3. Determine  $I_{D1}$ ,  $I_{D2}$  and  $V_4$  for the circuit in Figure 5 for :

(a)  $R_1 = 4.0$ ,  $R_2 = 1.0 \text{ (k}\Omega\text{)}$

(b)  $R_1 = 1.0$ ,  $R_2 = 4.0 \text{ (k}\Omega\text{)}$

For parts (a) and (b) the diodes have a forward voltage drop of 0.7 V

[6+6]



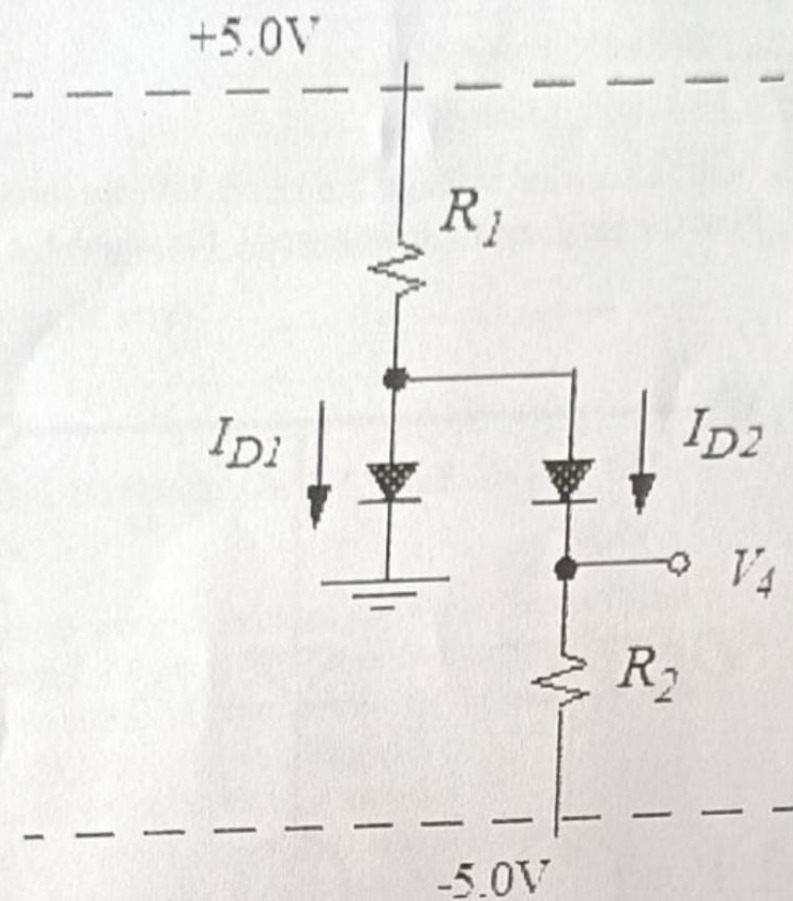


Figure 5

(c) A voltage  $1000 \sin(\omega t)$  volts is applied across YZ in Figure 6. Assuming ideal diodes, find the voltage measured across WX in volts. [2]

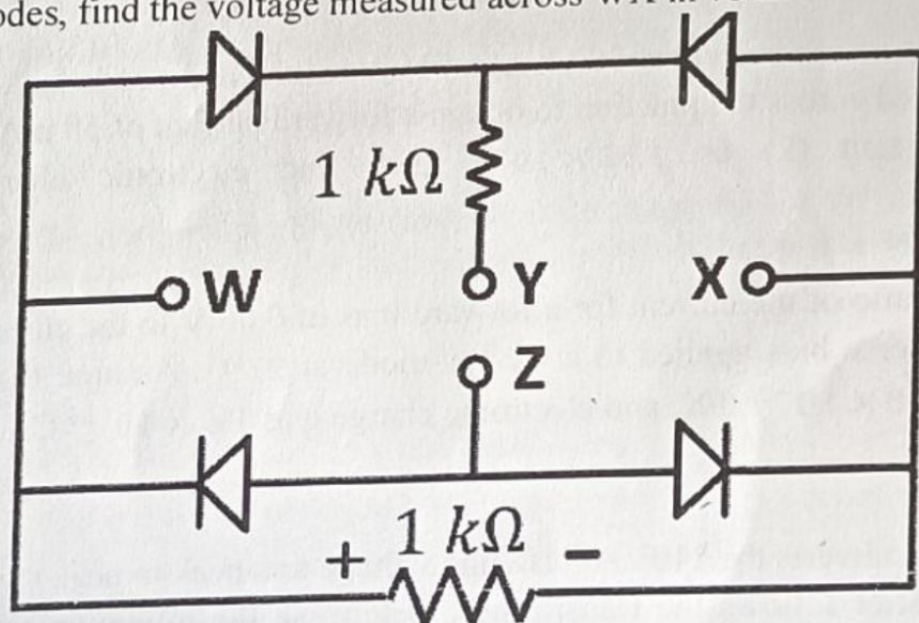


Figure 6

(d) Two silicon diodes, with a forward voltage drop of 0.7 V, are used in the circuit shown in the Figure 7. Find the range of input voltage  $V_i$  for which the output voltage  $V_o = V_i$  [6]

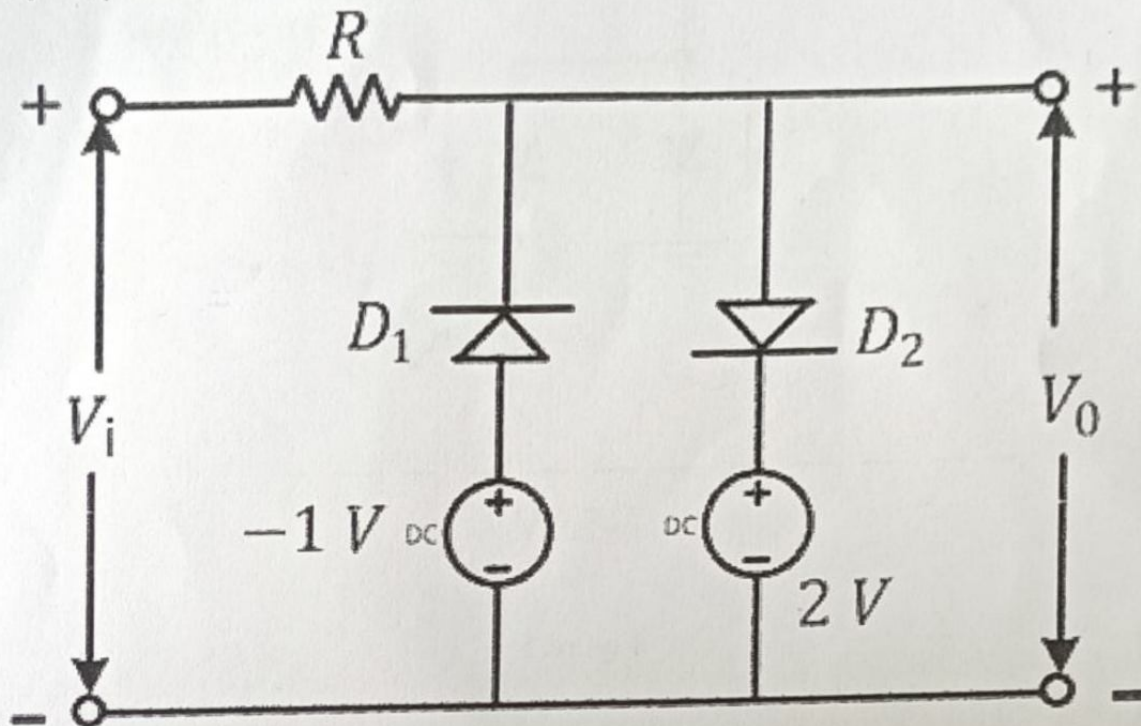


Figure 7

4. (a) The reverse saturation current at 300 K of a PN-junction Ge diode is  $5\mu\text{A}$ . Find the voltage to be applied across the junction to obtain a forward current of 50 mA. Assume Boltzmann's constant ( $k$ ) as  $1.38 \times 10^{-23}$  J/K, and electronic charge  $q$  as  $1.6 \times 10^{-19}$  C. [10]

(b) Calculate the ratio of the current for a forward bias of 0.06 V to the current for the same value of reverse bias applied to a Ge PN-diode at  $27^\circ\text{C}$ . Assume Boltzmann's constant ( $k$ ) as  $1.38 \times 10^{-23}$  J/K, and electronic charge  $q$  as  $1.6 \times 10^{-19}$  C. [10]

5. (a) A transformer converts the 110V, 60 Hz line voltage to a peak to peak swing of 9V. A half-wave rectifier follows the transformer. Determine the minimum value of the filter capacitor that maintains the ripple below 0.1 V. Assume cut-in voltage of diode  $V_\gamma = 0.8\text{V}$  and load resistance  $R_L = 0.436$  ohm. [10]

(b) A piece of Si is  $2\mu\text{m}$  long. The electron concentration is decaying exponentially (due to concentration gradient) from  $x=0$  to  $x=2\mu\text{m}$  as  $n(x) = N \exp(-x)$ . Find out the current in the semiconductor at  $x=2\mu\text{m}$ . Assume cross sectional area as  $1\mu\text{m} \times 1\mu\text{m}$ , concentration of electron at  $x=0$  as  $5 \times 10^{16}/\text{cm}^3$ , and diffusion coefficient of electron as  $34\text{ cm}^2/\text{sec}$ . Consider electronic charge  $q$  as  $1.6 \times 10^{-19}$  C. [10]