
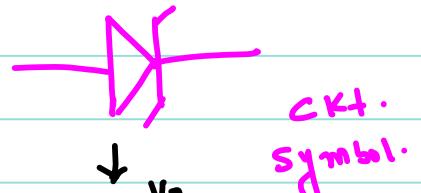
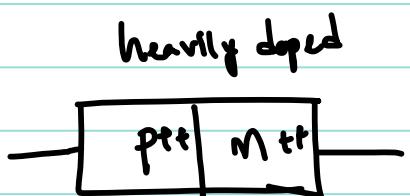


Lec-9


Zener Diode:

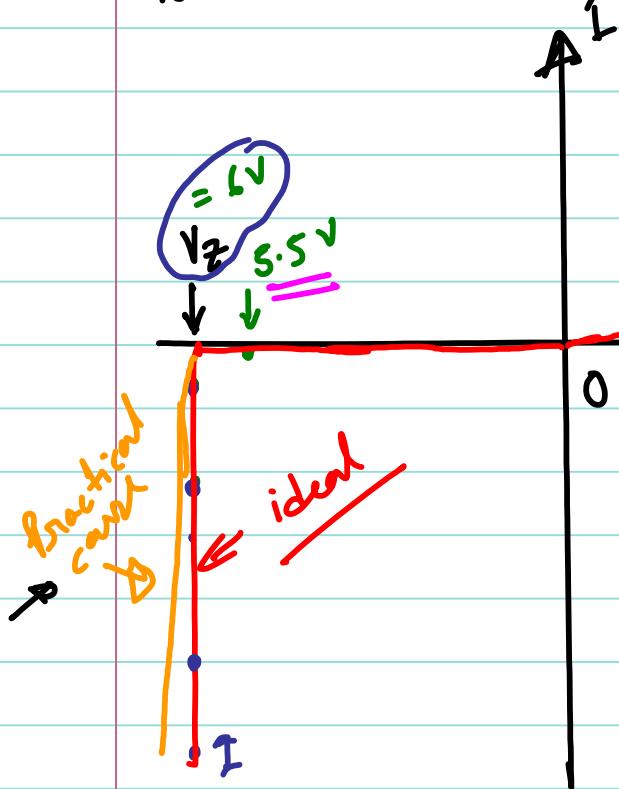


$$I_z \times V_z = 1A \times 5V = 5W$$

$$\frac{V_i - V_z}{R} = I$$


Current limiting resistor.

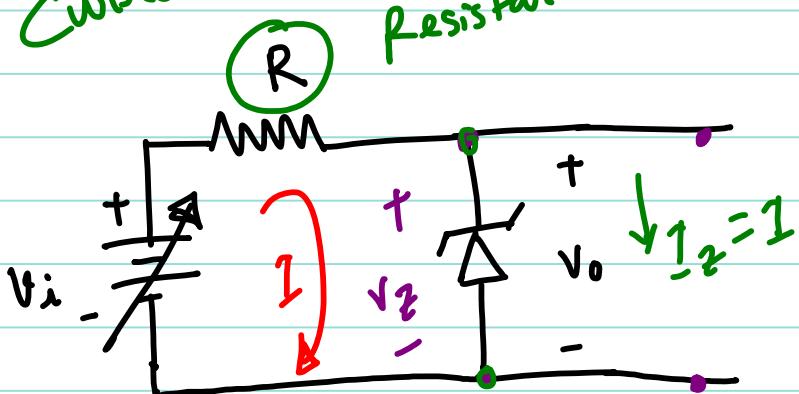

Zener diode as voltage regulator:

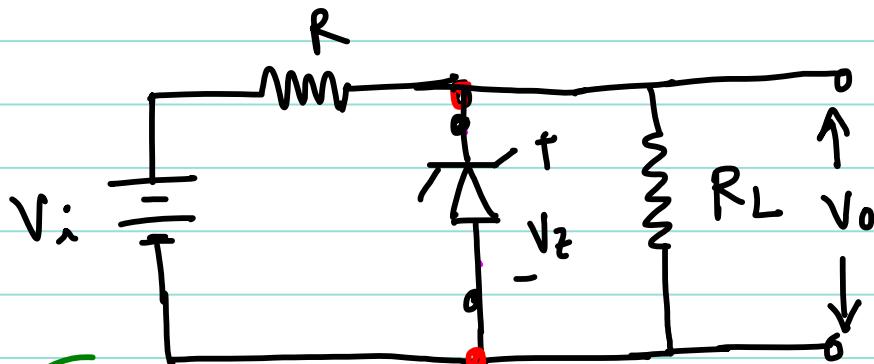


Zener must be operating in breakdown

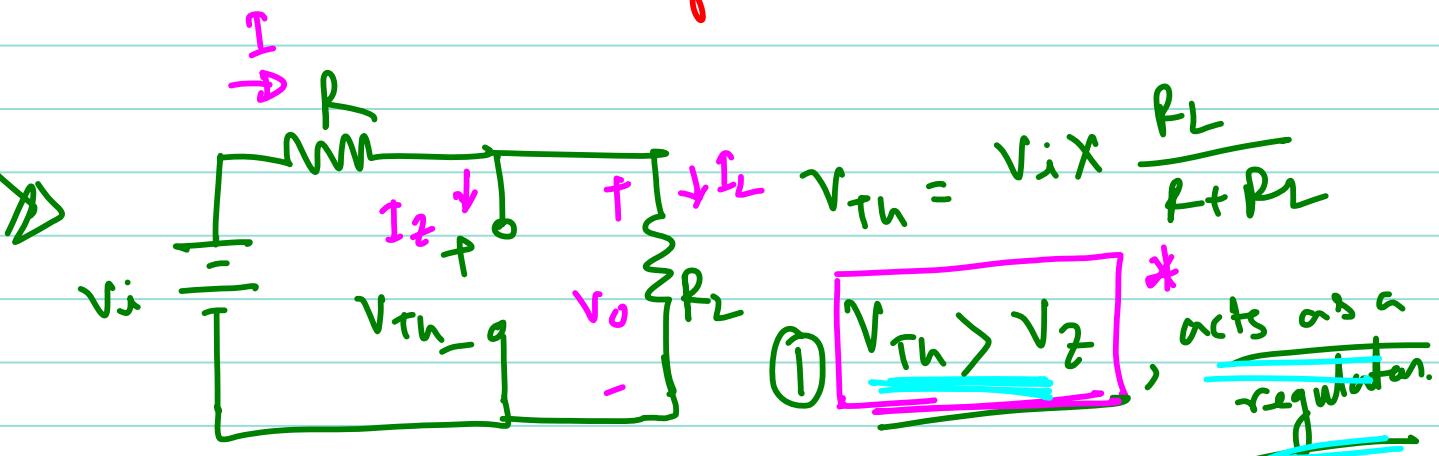

② $V_{Th} < V_z$, then No Breakdown, No regulation
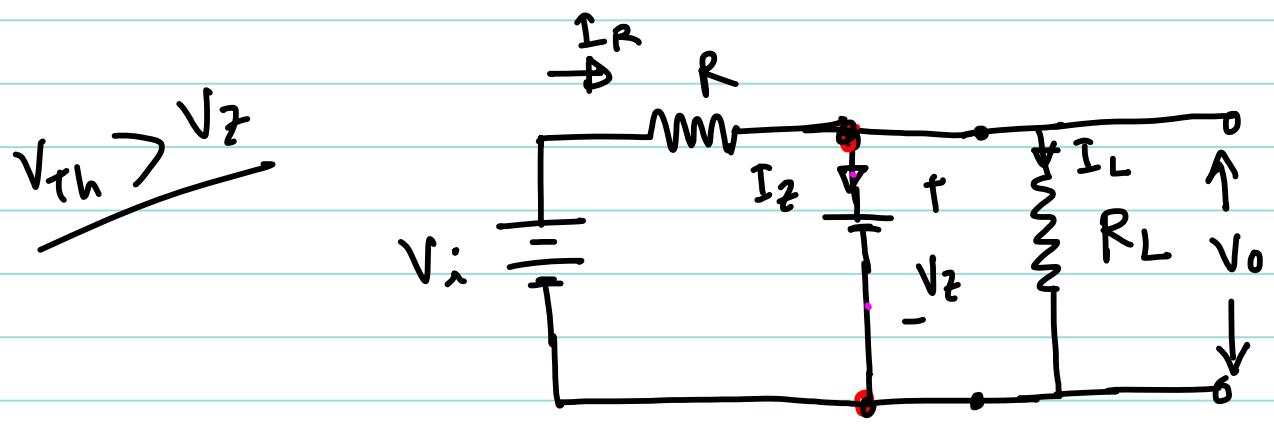
$$I_L = \frac{V_i}{R + R_L} ; V_0 = I_L \times R_L = \frac{V_i}{R + R_L} \times R_L$$



$$I_R = I_Z + I_L ; \quad I_Z = I_R - I_L \quad \checkmark$$

$$I_R = \frac{V_i - V_z}{R} ; \quad I_L = \frac{V_z}{R_L}$$

$$I_Z = \frac{V_i - V_z}{R} - \frac{V_z}{R_L}$$

↑


$$\begin{aligned} \text{Power dissipation across Zener} &= I_Z \cdot V_z = P_Z \\ &= = = = \end{aligned}$$


$$\underline{P_Z < P_{Z, \text{rated}}}$$

$P_{Z, \text{rated}}$

$= 2W$

$1.5W$

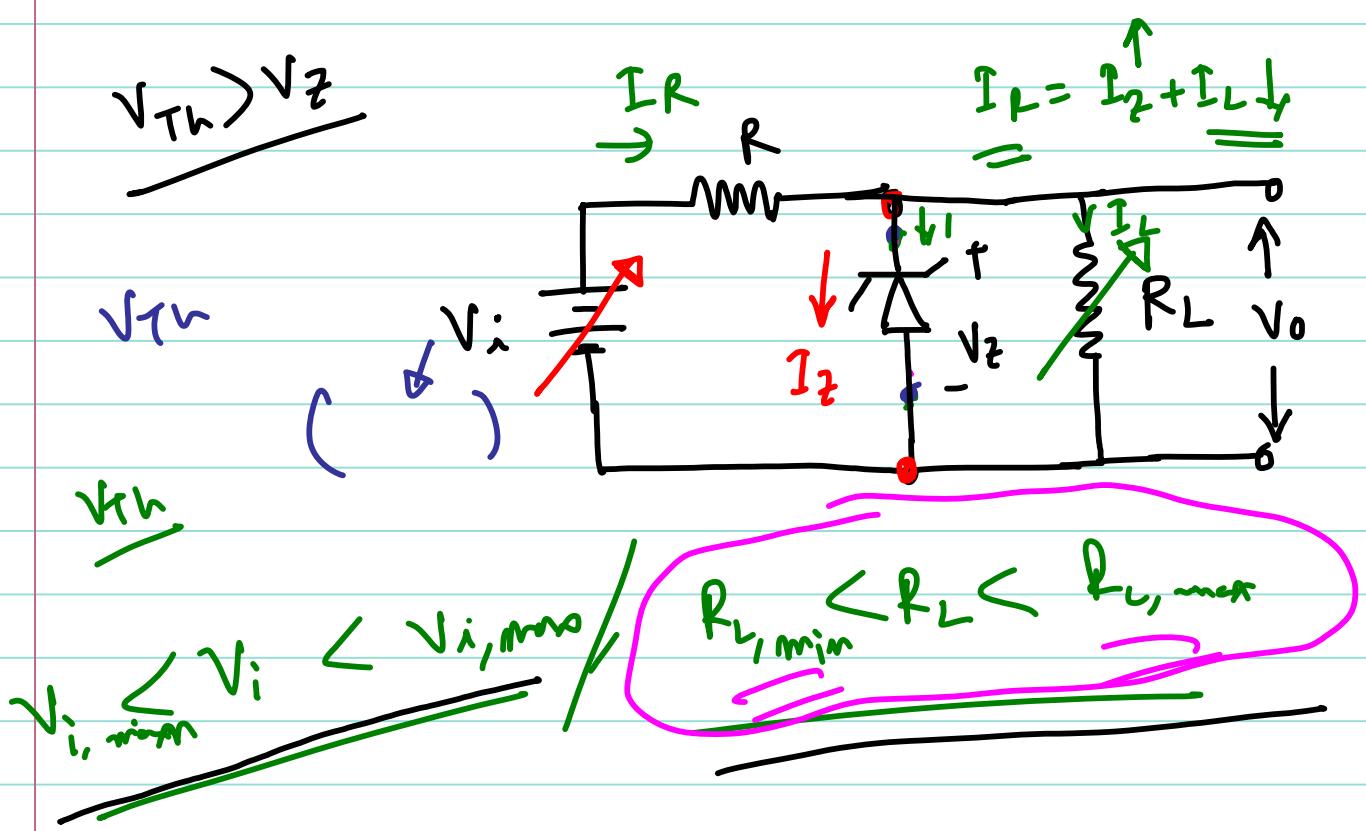

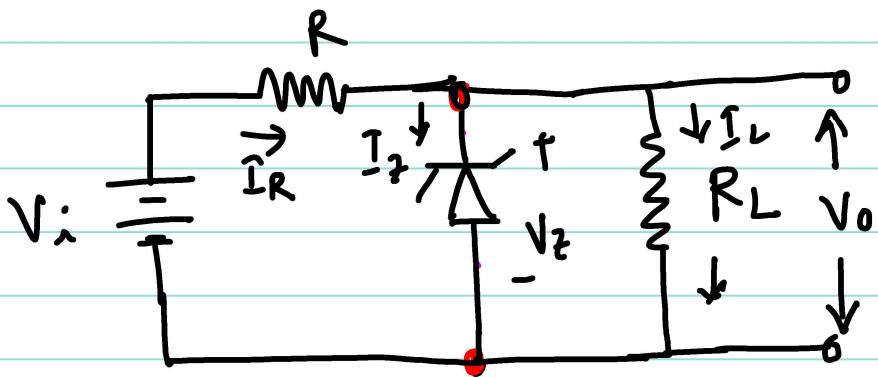

Considering, R_L is variable, find, $\{R_{L,\min}, R_{L,\max}\}$

→ for regulation, voltage across Z ener should be $\geq V_Z$

$$V_{Th} = V_i \times \frac{R_L}{R + R_L} = V_Z \quad \text{for min value of } R_L$$


$$\rightarrow R_{L,\min} = \frac{V_Z \cdot R}{V_i - V_Z}$$


When, R_L is min, I_L is max, $(I_{L,\max} = \frac{V_Z}{R_{L,\min}})$

$$I_R = I_Z + I_L \quad ; \quad I_R = \frac{V_i - V_Z}{R}$$

min \Downarrow max. max.

$P_{Z,\min} = V_Z \cdot I_{Z,\min}$

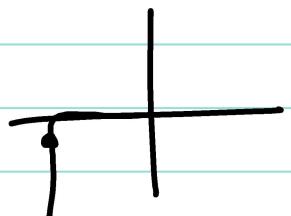

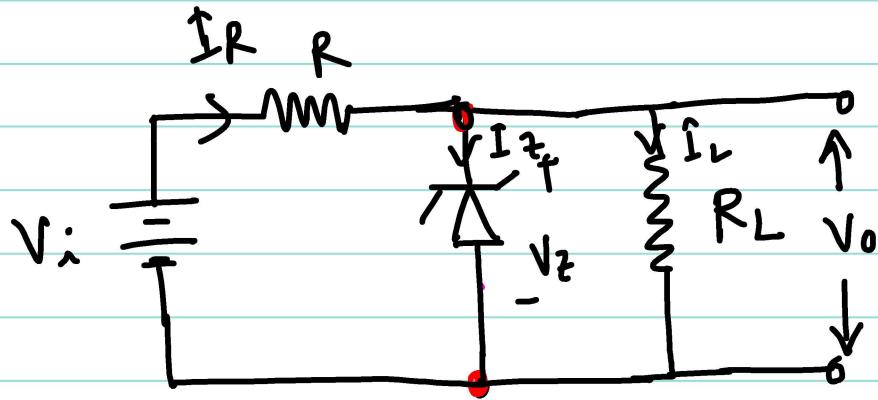

When R_L is max., I_L is min., I_z is max.


$$I_{z, \text{max}} = \frac{P_{z, \text{max}}}{V_z}$$

$$R_{L, \text{max}} = \frac{V_z}{I_{L, \text{min}}}$$

$$\begin{aligned} I_{z, \text{max}} + I_{L, \text{min}} &= I_R \\ &= \frac{V_i - V_z}{R} \end{aligned}$$

→ $V_{i, \text{min}} < V_i < V_{i, \text{max}}$

H.W.

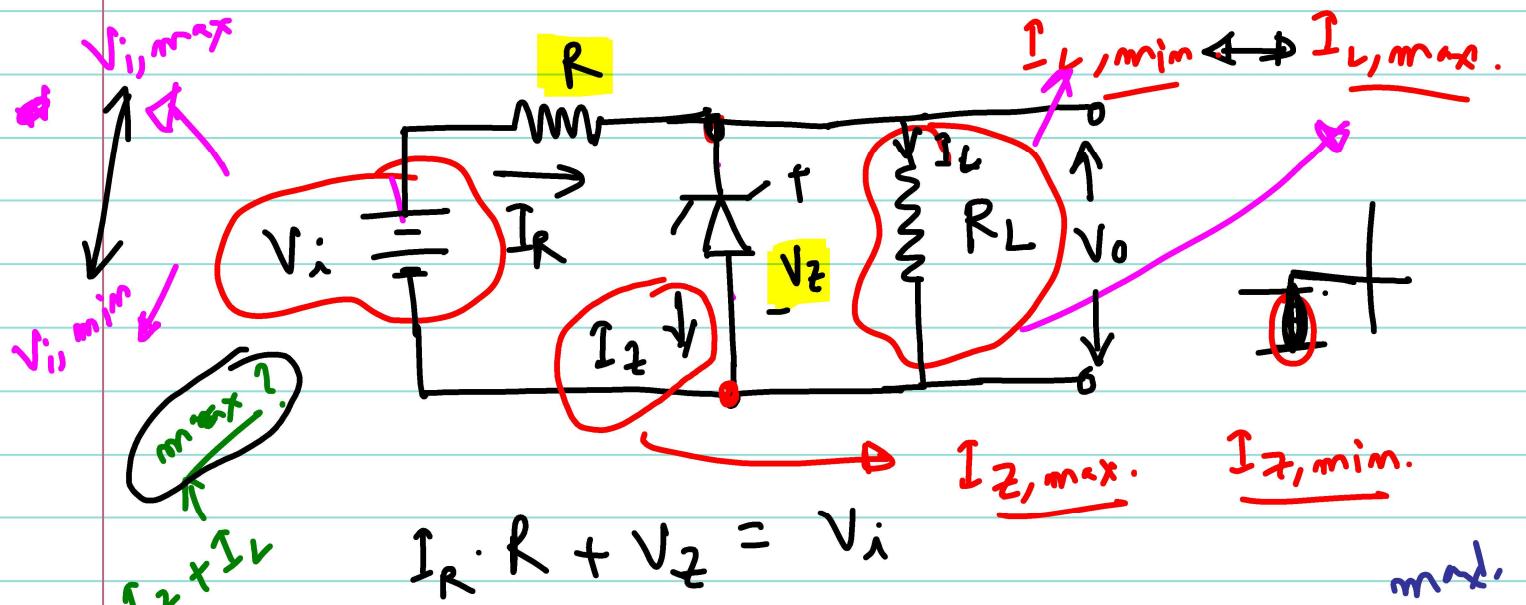

$$R = \frac{V_i - V_Z}{I_R} = \frac{V_i - V_Z}{I_Z + I_L}$$

$\xrightarrow{\text{max.}}$
 $\xrightarrow{\text{min.}}$
 $I_L + I_Z = I_R$

$$\rightarrow I_Z = \frac{V_i - V_Z}{R} - \frac{V_Z}{R_L} ; I_Z = I_R - I_L$$

$\xrightarrow{\text{min.}}$
 $\xrightarrow{\text{max.}}$

$$D_R = \frac{V_i(\min) - V_Z}{I_Z(\min) + I_L(\max)}$$


$\xrightarrow{\text{Vi is min}}$

$$I_Z(\min) + I_L(\max)$$

$$R = \frac{V_i(\max) - V_Z}{I_Z(\max) + I_L(\min)}$$




$\xrightarrow{\text{Vi, max}}$
 $\xrightarrow{\text{I_L is min}}$
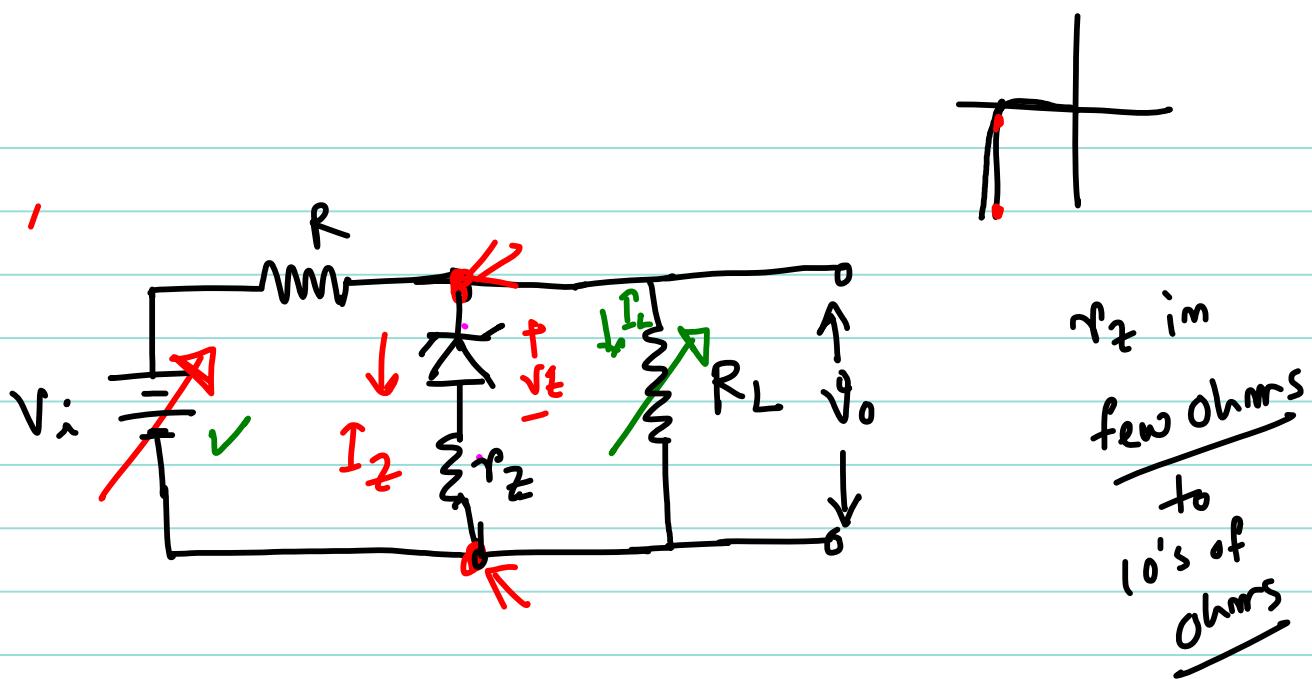
$$I_{Z(\min)} = I_{Z(\max)} \times 10\%$$



$$\rightarrow \text{Source Regulation} = \frac{\Delta V_o}{\Delta U_i} \times 100\% ; \text{ No load}$$
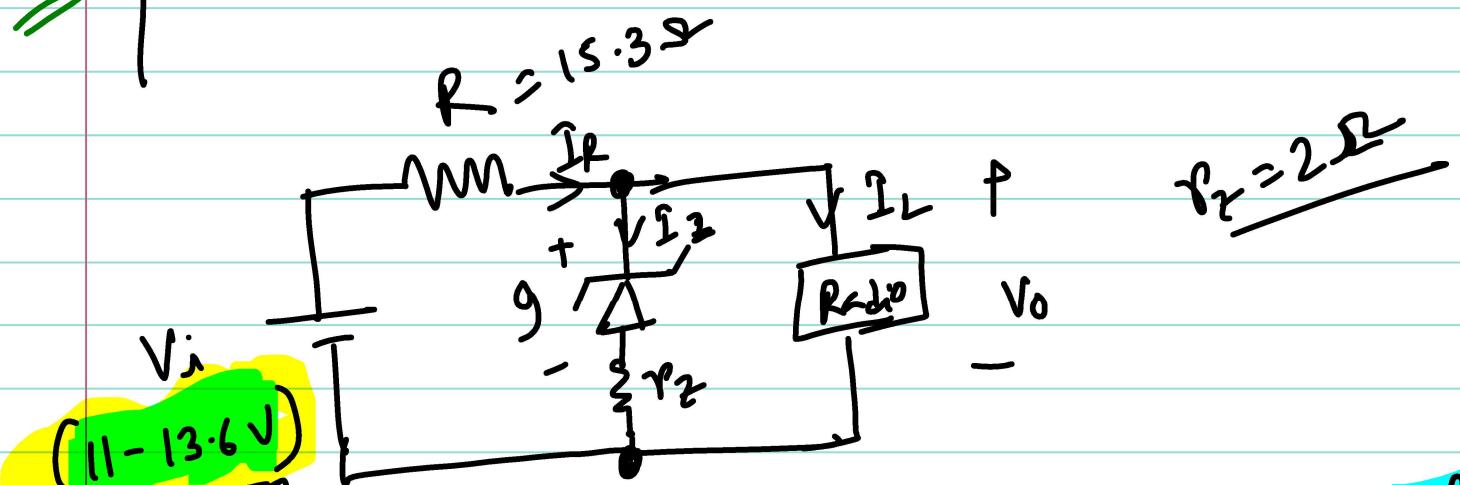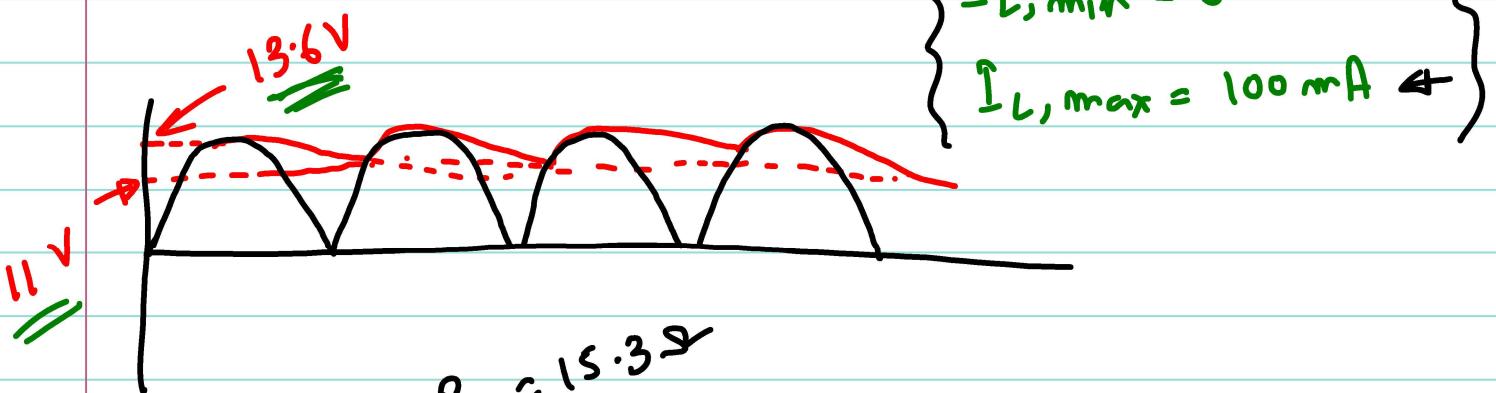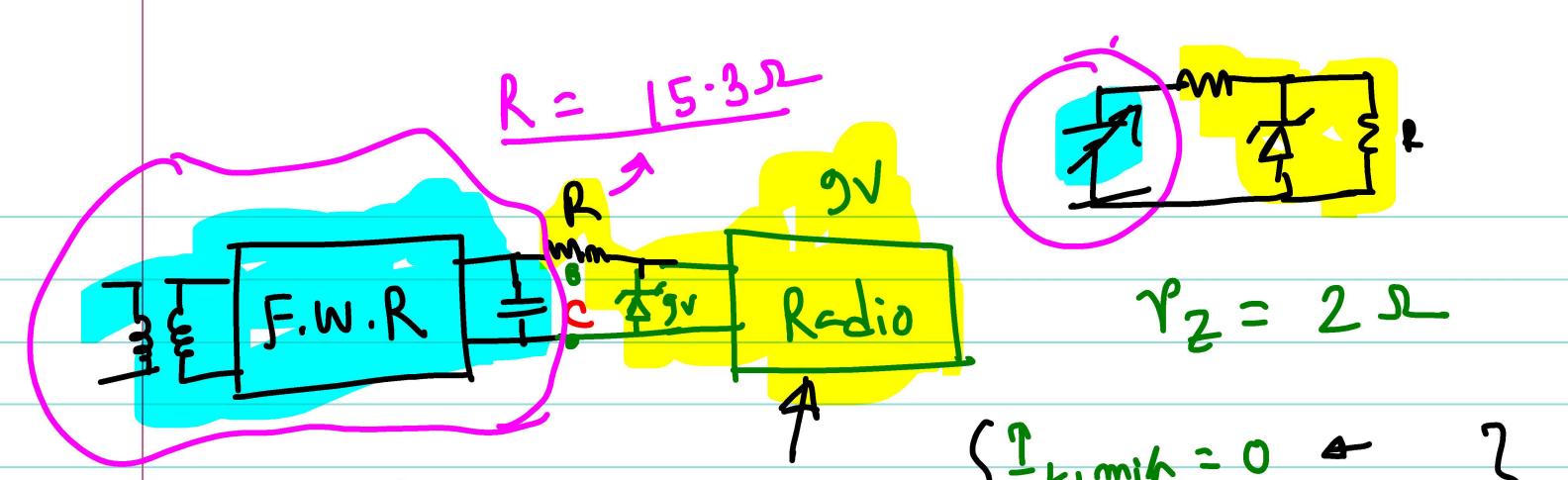
$$\rightarrow \text{Load regulation} = \frac{V_o, \text{ no load} - V_o, \text{ full load}}{V_o, \text{ full load}} \times 100\%$$



$$\Delta V_o = \frac{2.6V}{13.6V} , \quad I_2 = \frac{13.6 - 9}{R + r_2} = \frac{13.6 - 9}{17.3} = 0.265A.$$

$$V_o = 9 + I_2 \cdot r_2 = 9.532V.$$

$$I_2 = \frac{11 - 9}{17.3} = 0.1156A.$$

$$\text{Source Regulation} = \frac{\Delta V_o}{\Delta V_{in}} \times 100\% = \frac{9.532 - 9.231}{13.6 - 11} \times 100\% = 11.1\%$$

