



# INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR

End-Autumn Semester Examination 2022-23

Date of Examination: \_\_\_\_\_ Session: (FN/AN) \_\_\_\_\_ Duration: 3 hrs. Full Marks: 120

Subject No.: EC 21201 Subject: Basic Electronics

Department/Center/School: E&ECE

Specific charts, graph paper, log book etc., required None

Special Instructions (if any): \_\_\_\_\_

Answer all questions. Marks for the questions are indicated on the right.

1. In Figure 1, what is the minimum allowable value of  $V_{DD}$  if  $M_1$  must not enter the triode region? (assume  $\lambda=0$ , threshold voltage =  $0.4V$ ,  $\mu C_{ox}=200 \mu A/V^2$ ) [5]

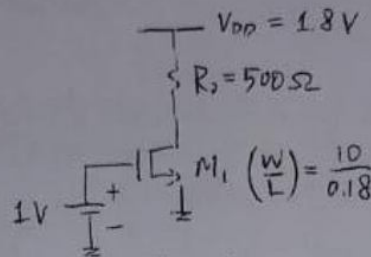


Figure 1

- ii. In the circuit in Figure 2, assume the transistor acts as a linear resistor. Determine (W/L) of the transistor such that the circuit attenuates the signal by only 5%. Assume  $V_G=1.8V$ ,  $R_L=100 \Omega$ , threshold voltage =  $0.4V$ ,  $\mu C_{ox}=200 \mu A/V^2$ . [5]

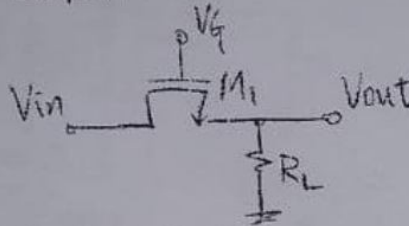


Figure 2

Sketch  $I_x$  as a function of  $V_x$  for the two circuits in Figure 3. Assume  $V_x$  goes from 0 to  $V_{DD}=1.8V$ . Also show in the plot at what value of  $V_x$  the device changes its region of operation (assume  $V_{TH}=0.4V$ ) [5]

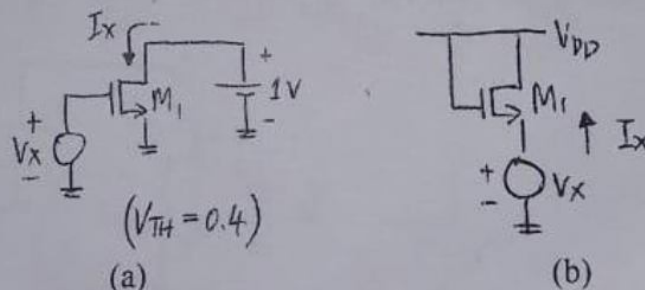


Figure 3

- iv. Find out MOSFET current ( $I_{DS}$ ) and gate source voltage ( $V_{GS}$ ) for the circuit in Figure 4. Assume  $\lambda=0$ , threshold voltage  $= 1\text{ V}$ ,  $\mu C_{ox}(W/L) = 1\text{ mA/V}^2$ . [5]

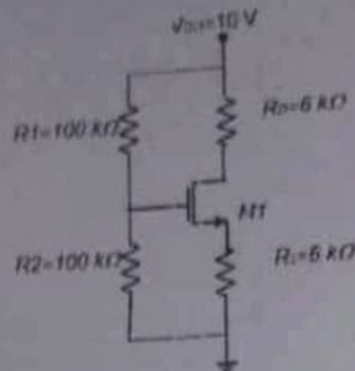


Figure 4

2. i. For the transistor in the circuit in Figure 5,  $\beta=200$ . Find  $I_E$  (emitter current) and  $V_C$  (voltage at collector) for (a)  $V_B=0\text{V}$ , (b)  $V_B=1\text{V}$  and (c)  $V_B=2\text{V}$ . (Assume that if transistor is on  $V_{BE}=0.7\text{V}$  and if transistor is in saturation  $V_{CE}=0.2\text{V}$ ) [10]

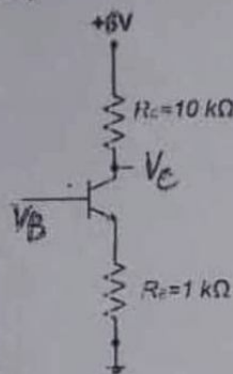


Figure 5

- ii. Consider a common emitter circuit using a npn BJT having  $I_S=10^{-15}\text{A}$  at room temperature (assume thermal voltage  $26\text{ mV}$ ), a collector resistance  $R_C=6.8\text{ k}\Omega$ , and a power supply  $V_{CC}=10\text{V}$ . Determine the value of the bias voltage  $V_{BE}$  required to operate the transistor at  $V_{CE}=3.2\text{V}$ . [5]
- iii. In the circuit in Figure 6, base collector is at  $200\text{ mV}$  reverse bias,  $V_{CC}=2.5\text{V}$  and  $R_E=1\text{ k}\Omega$ . Find emitter current  $I_E$  (assume  $V_{BE}=0.7\text{V}$ ). [5]

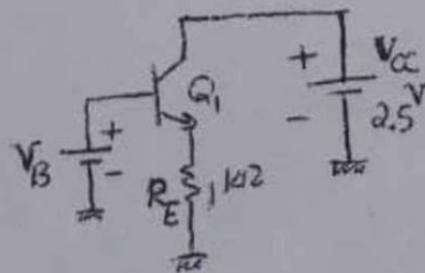


Figure 6

3. For the circuit in Figure 7,  $\beta = 100$ ,  $V_{BE} = 0.7\text{ V}$ ,  $kT/q = 25\text{ mV}$ . Assume BJT output resistance ( $r_o$ ) is very high.
- Find out the operating point of the BJT. [10]
  - Draw the  $g_m - \pi$  model of the BJT and find out the voltage gain. [10]

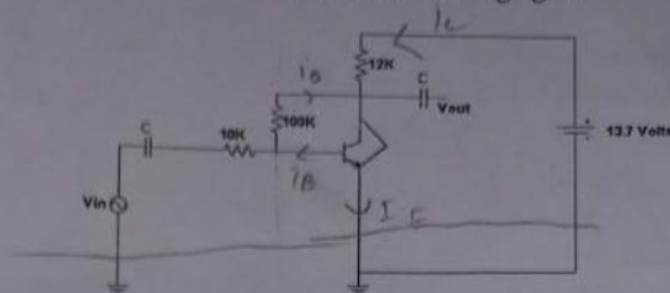


Figure 7

4. In the circuit in Figure 8, the transistor possesses a  $\beta = 65$ , Early Voltage  $V_A = 75\text{ V}$  with  $V_T = 26\text{ mV}$ . Find the transistor parameters  $r_n$ ,  $r_o$  &  $g_m$ . [10]

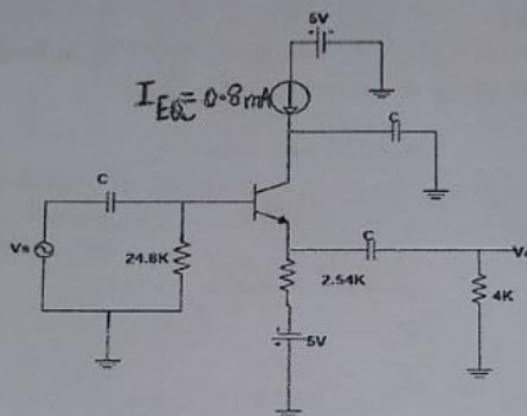


Figure 8

- ii. In the circuit in Figure 9, given that  $\beta = 120$ ,  $r_o = \infty$ ,  $V_{BE} = 0.7\text{ V}$  and  $V_T = 26\text{ mV}$ . Draw the  $g_m - \pi$  model of the BJT and find out the voltage gain. [10]

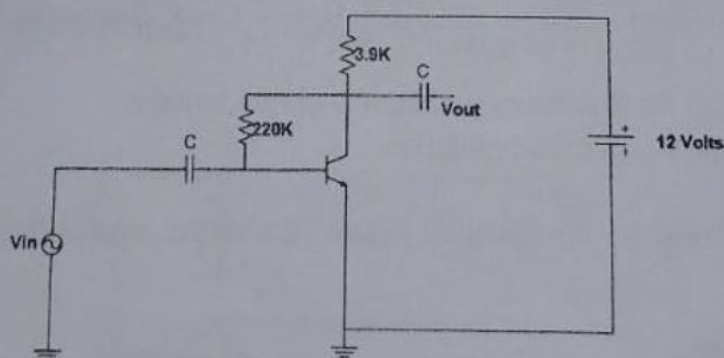


Figure 9

5. The parameters in the circuit in Figure 10 are  $V_\gamma = 0.7$  V,  $V_{Z1} = 2.3$  V, and  $V_{Z2} = 5.6$  V. Determine  $v_O$  versus  $v_I$  over the range of  $-10 \leq v_I \leq +10$  V. [10]

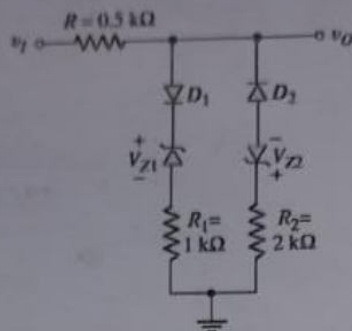


Figure 10

- ii. For the circuit in Figure 11,  
 (a) plot  $v_O$  versus  $v_I$  for  $0 \leq v_I \leq 15$  V. Assume  $V_\gamma = 0.7$  V. Indicate all breakpoints.  
 (b) Plot  $i_D$  over the same range of input voltage. [10]

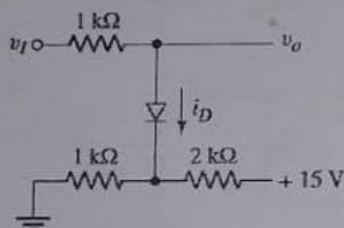


Figure 11

6. i. A voltage regulator is to have a nominal output voltage of 10 V. The specified Zener diode has a rating of 1 W, has a 10 V drop at  $I_Z = 25$  mA, and has a Zener resistance of  $r_z = 5$  Ω. The input power supply has a nominal value of  $V_{PS} = 20$  V and can vary by  $\pm 25$  percent. The output load current is to vary between  $I_L = 0$  and 20 mA. [10]  
 (a) If the minimum Zener current is to be  $I_Z = 5$  mA, determine the required input resistance  $R_i$ .  
 (b) Determine the maximum variation in output voltage.  
 (c) Determine the percent regulation.

- ii. Sketch  $v_O$  versus time for the circuit in Figure 12 with the input shown. Assume  $V_\gamma = 0$ . [10]

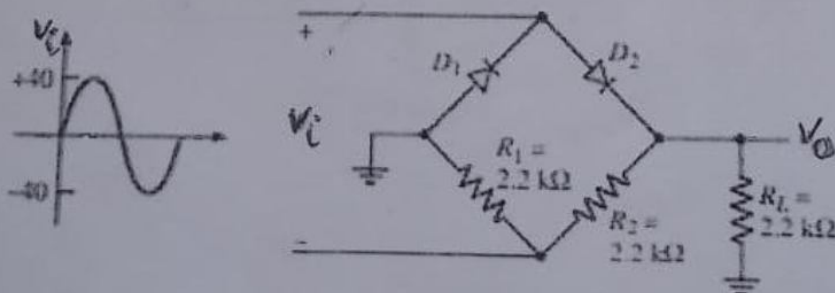


Figure 12