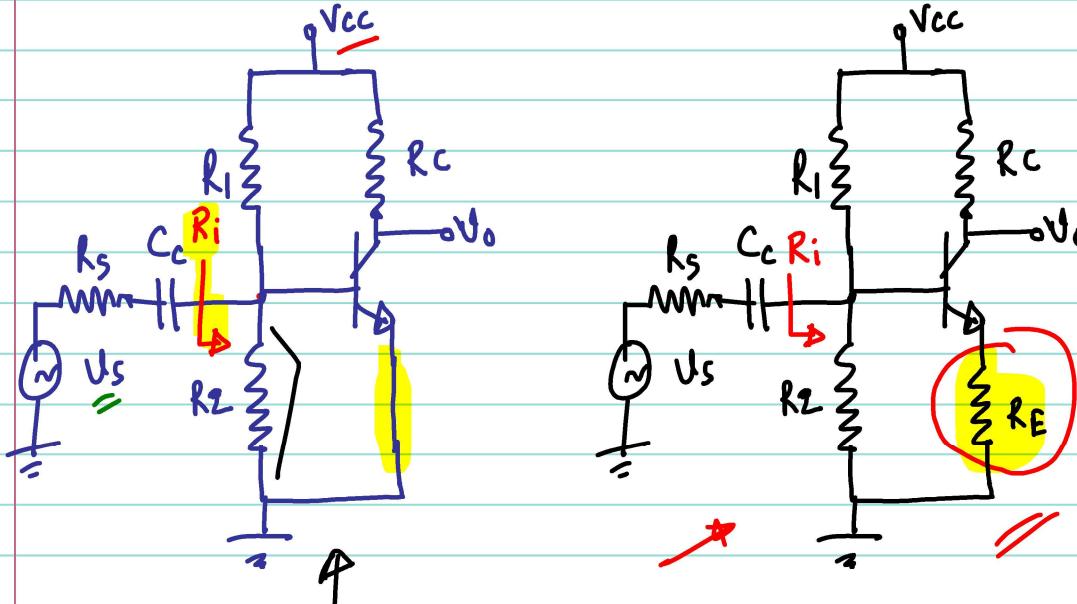


Lec-19

CE Amplifier with/without emitter resistor:




Input resistance R_i

$$R_i = R_1 \parallel R_2 \parallel r_{\pi}$$

typical values, $T_n = \text{few k}\Omega$

$$\begin{aligned} R_1 &= \text{tens of k}\Omega \\ R_2 &= \text{a few k}\Omega \end{aligned} \quad \left. \begin{aligned} R_1 &> R_2 \\ R_1 &\parallel R_2 \end{aligned} \right\} R_i > R_2$$
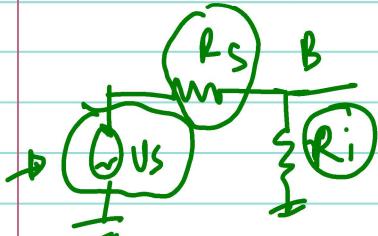
$$\text{gain} = -g_m \cdot (R_C \parallel r_o) \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi} + R_s}$$



$$R_i = R_1 \parallel R_2 \parallel [r_{\pi} + (1 + \beta)R_E]$$

$$\text{gain} = -\frac{\beta R_C}{r_{\pi} + (1 + \beta)R_E} \left(\frac{R_i}{R_i + R_s} \right) \approx -\frac{R_C}{R_E}$$

$R_E \uparrow$, gain \downarrow
 $R_E \downarrow$, gain \uparrow .

$$\beta_1 \text{ gain} = -\frac{\beta R_C}{r_{\pi} + (1 + \beta)R_E}$$


$$r_{\pi} \ll (1 + \beta)R_E$$

$$\text{gain} = \frac{R_i}{R_i + R_s}$$

$$\text{gain} = -\frac{R_C}{R_E}$$

CE Amplifier with emitter bypass capacitor.

Notice
Dual
Supply
 (x) $(-)$

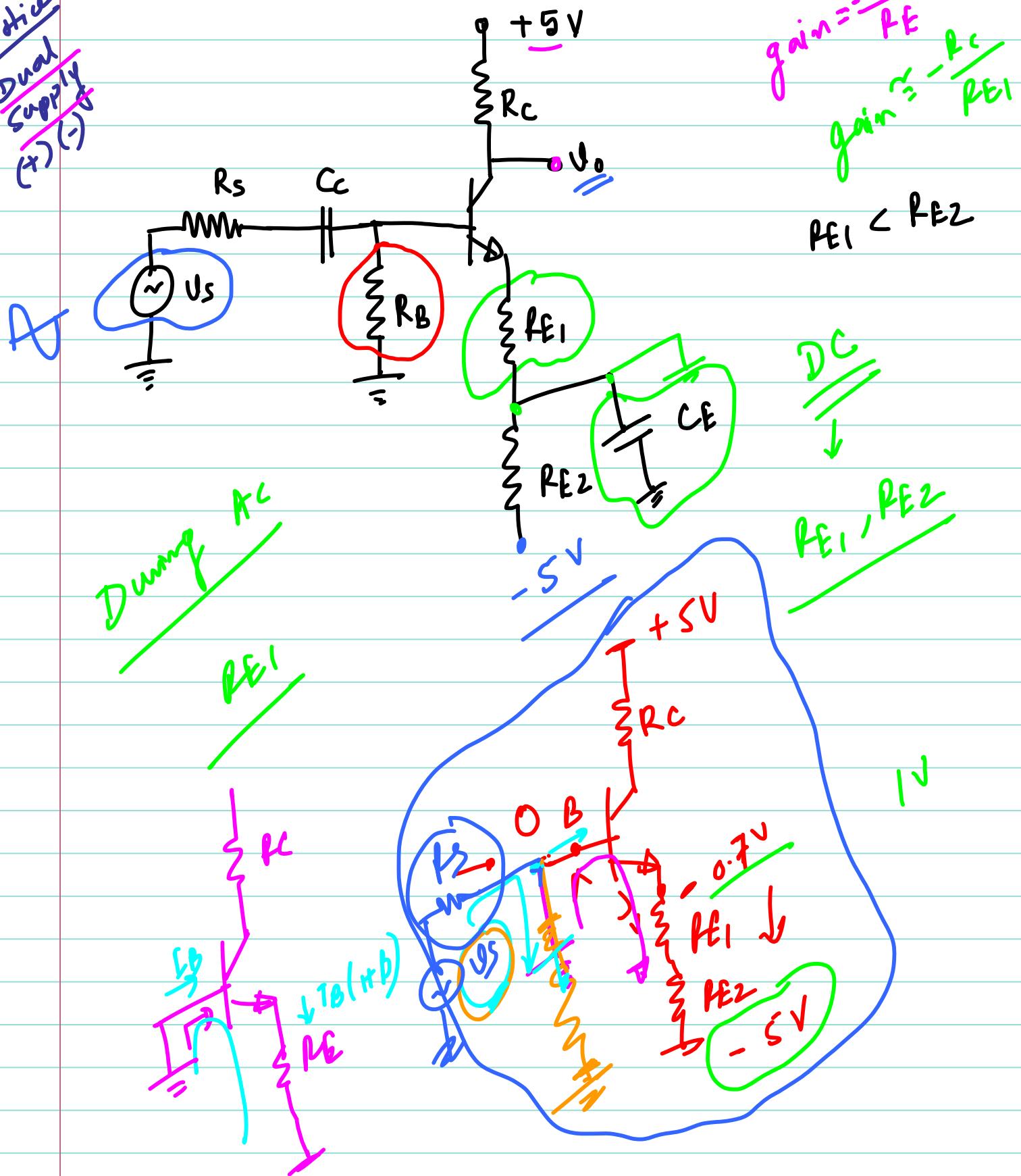

Example

Design the BJT based amplifier:


$\rightarrow V_s \rightarrow 12 \text{ mV}$ Sinusoidal signal
 $\rightarrow V_o \rightarrow 0.4 \text{ V}$ " (expected)

$$I_E \approx 0.2 \text{ mA} \approx I_C$$

$$V_{CEQ} \approx 4 \text{ V}$$

Given, $\beta = 100$ (75-125)
 $V_{BE-ON} = 0.7 \text{ V}$

$$R_B = 100 \text{ k}\Omega$$

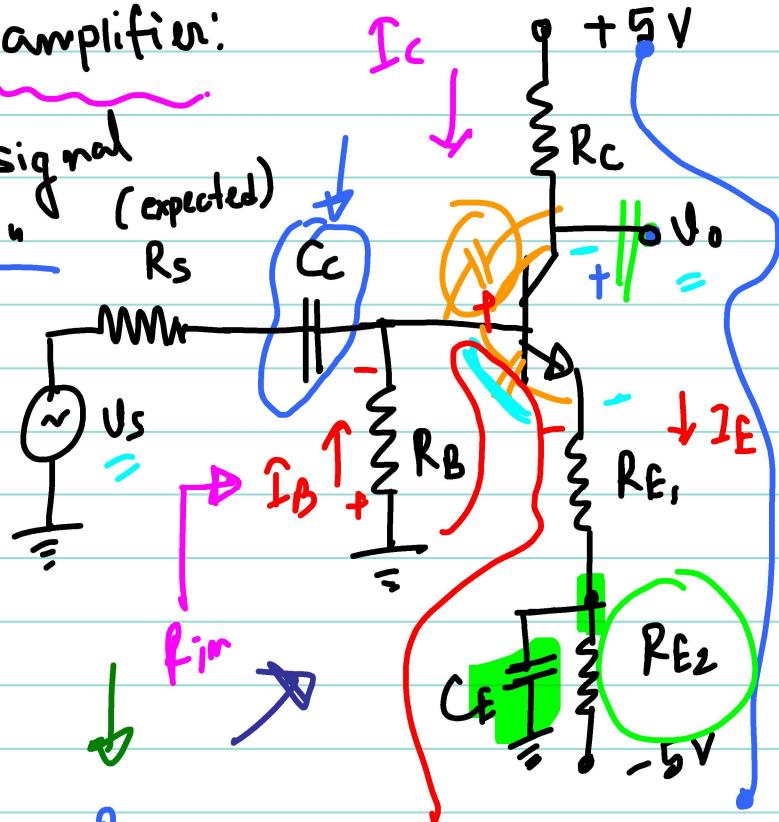

$$|\text{Gain}| = \frac{0.4 \text{ V}}{0.012 \text{ V}} = 33.3 \approx +\frac{R_C}{R_{E1}} \rightarrow 150 \text{ }\Omega$$

$$\frac{R_C}{R_{E1}} > 33.3 ; \left(\frac{R_C}{R_{E1}} \right) = 40, R_C = 40 R_{E1}$$

$$-I_B R_B - V_{BE-ON} - I_E (R_{E1} + R_{E2}) = -5 \text{ V} ; I_E = (1 + \beta) I_B$$

$$(1 + \beta) I_B \quad R_{E1} + R_{E2} = 20.5 \text{ k}\Omega$$

$$5 - I_C R_C - V_{CE} - I_E (R_{E1} + R_{E2}) = -5 ; R_C = 9.5 \text{ k}\Omega$$

$$\frac{R_C}{R_{E1}} = 40, R_C = 9.5 \text{ k}\Omega, R_{E1} = 0.238 \text{ k}\Omega \quad \frac{238 \text{ }\Omega}{20.3 \text{ k}\Omega}$$

$$\rightarrow R_{E1} = 240 \Omega, R_{E2} = 20 k\Omega, R_C = 10 k\Omega$$

DC analysis:

$$I_{C1}$$

DC

AC Analysis

γ_A, g_m
gain \rightarrow

$\gamma_A \ll (1+\beta) \beta F$

Expected

$$|A_V| = 33.3$$

$$V_o = 0.40 V.$$

$$\beta_F = \beta_{F1} = 240 \Omega$$

$$(1+\beta) 240 \Omega = 24.24 k\Omega$$

$$\gamma_A = \frac{I_S}{\beta V_T} = \frac{0.2 \mu A}{10 \times 0.001} = 200 \Omega$$

$$\gamma_A \approx 13 k\Omega$$

β

$I_{C8} (\text{mA})$

$|A_V|$

$V_o (V)$

$\rightarrow 100$

0.201

26.4

0.317

33.3

AC load line and its use:

