

BJT DC Analysis: (n-p-n)

(i) Assume BJT is in forward active mode

$$V_{BE} = V_{BE(on)} \approx 0.7 \text{ V for Silicon BJT}$$

$$I_B > 0 \text{ and } I_C = \beta I_B$$

(ii) Analyze the 'linear' circuit.



(iii) If $V_{CE} > V_{CE(sat)}$ → then active region (our assumption is correct)

→ if $V_{CE} < 0$ → Probably, BJT is in saturation

→ if $I_B < 0$ → Probably, BJT is in cut-off

Rec-1H


Load line:

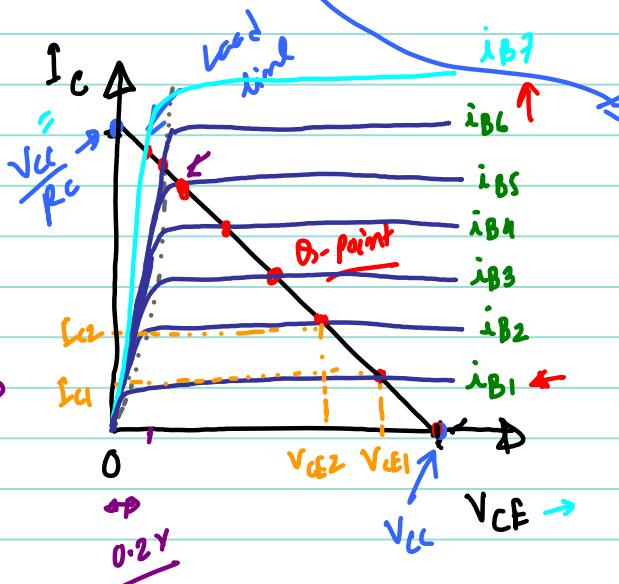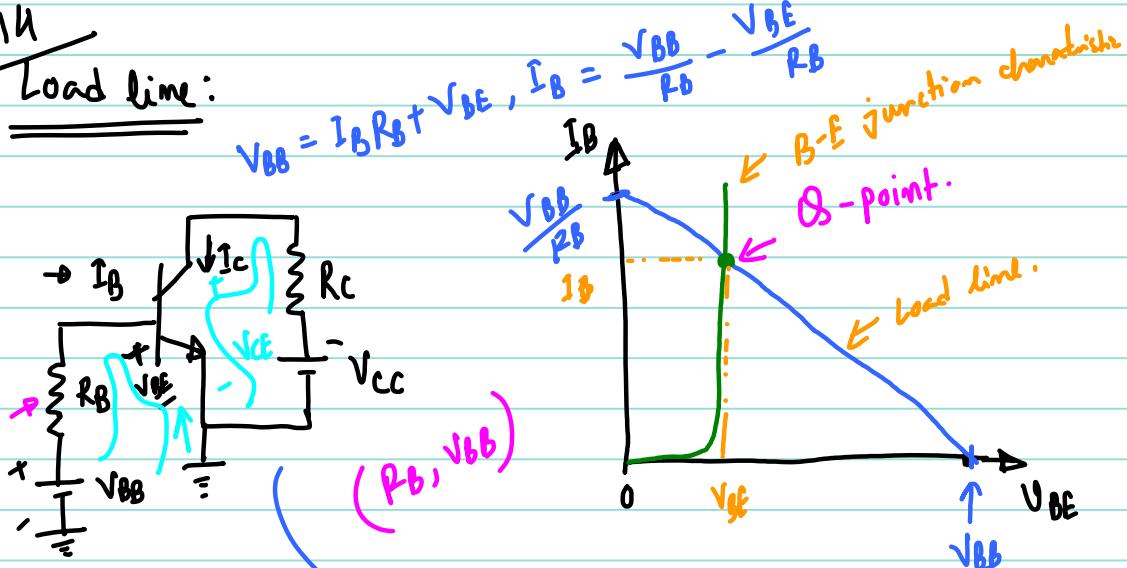

$$V_{CC} = I_C R_C + V_{CE}$$

$$I_C = \frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C}$$

Example

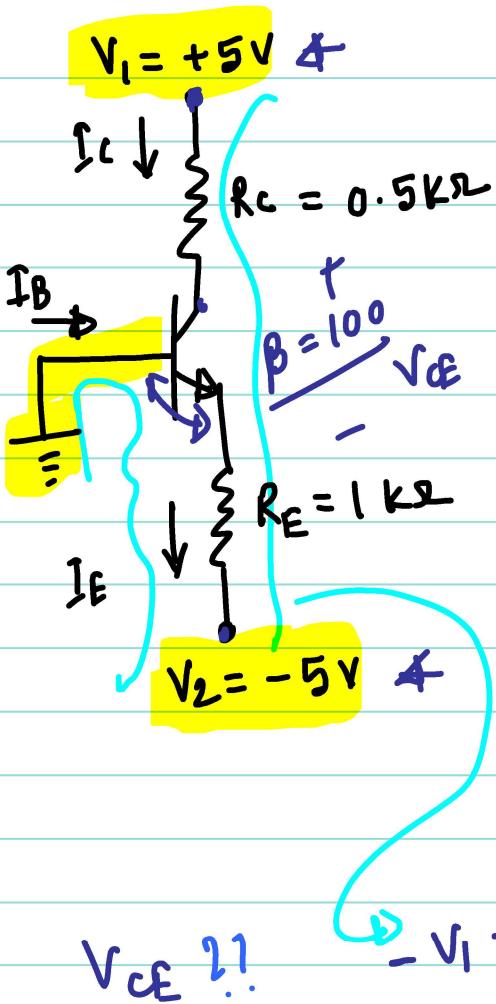

Find Q-point

$$0 = V_{BE\text{ON}} + I_E R_E - 5$$

$$I_E = 4.35 \text{ mA}$$

$$\underline{I_C = \alpha I_E}$$

$$\underline{\beta = 100, \alpha = \frac{100}{101} = 0.99}$$

$$I_C = 0.99 \times I_E$$


$$\underline{I_C = 4.307 \text{ mA}} \quad (\text{Q.})$$

$$S = I_c R_{ct} + V_{CE}$$

$$I_c = 0, \quad V_{CE} = 5V$$

Voltage Transfer Characteristics in BJT Ckts.


VTC

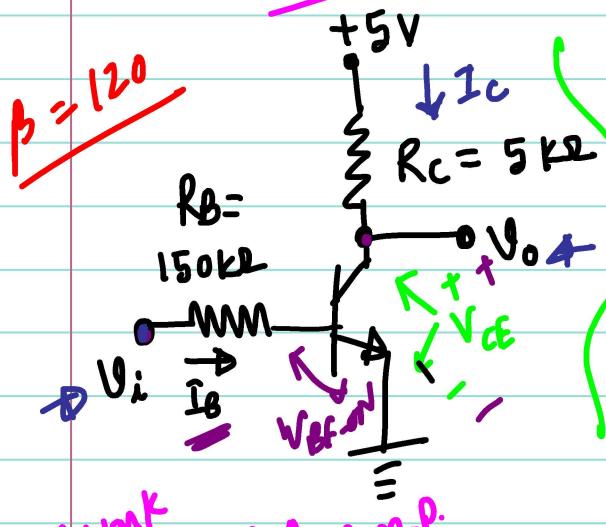

Homework
using p-n-p.

$$(i) V_i \rightarrow 0, \quad V_i < 0.7V, \quad \text{cut-off}. \quad I_c = I_B = 0$$

$$V_o = 5V$$

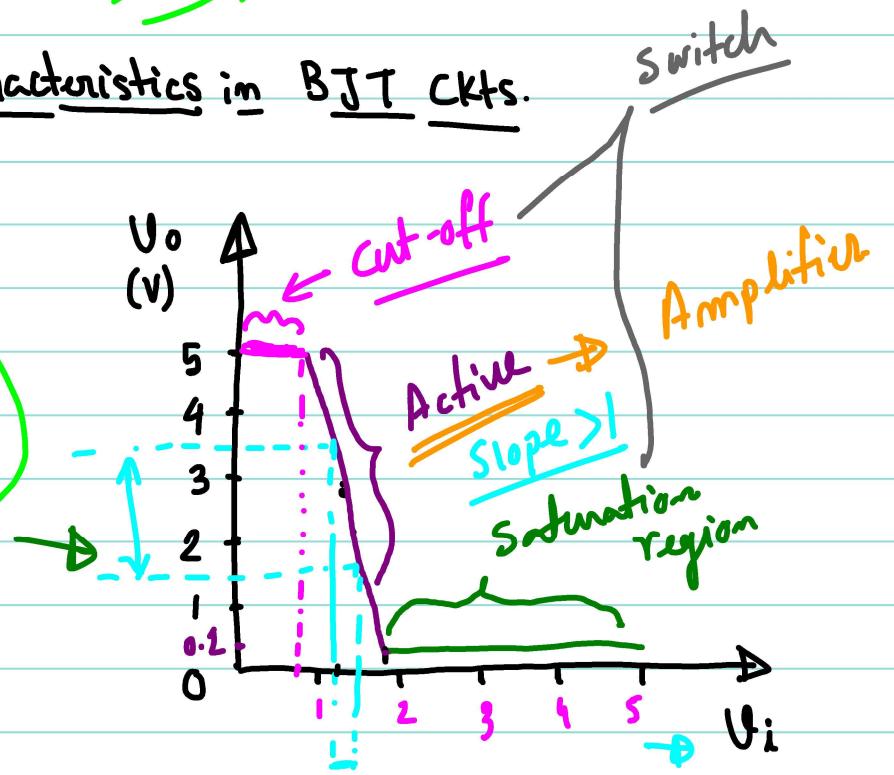

(ii) $V_i > 0.7V$, BJT is in forward Active mode,

$$\rightarrow I_B = \frac{V_i - V_{BE-ON}}{R_B}; \quad I_c = \beta \cdot I_B$$


$$I_c = \beta \cdot \frac{V_i - V_{BE-ON}}{R_B}$$

$$V_o = 5 - I_c R_c = 5 - \beta \cdot R_c \cdot \frac{V_i - V_{BE-ON}}{R_B} \quad 4$$


$$0.2 = 5 - \beta R_c \cdot \frac{V_i - V_{BE-ON}}{R_B} \quad ; \quad V_i = 1.9V \quad 4$$

$$(iii) \quad V_i > 1.9V, \quad V_o = V_{CE-sat} = 0.2V.$$

BJT as switch:

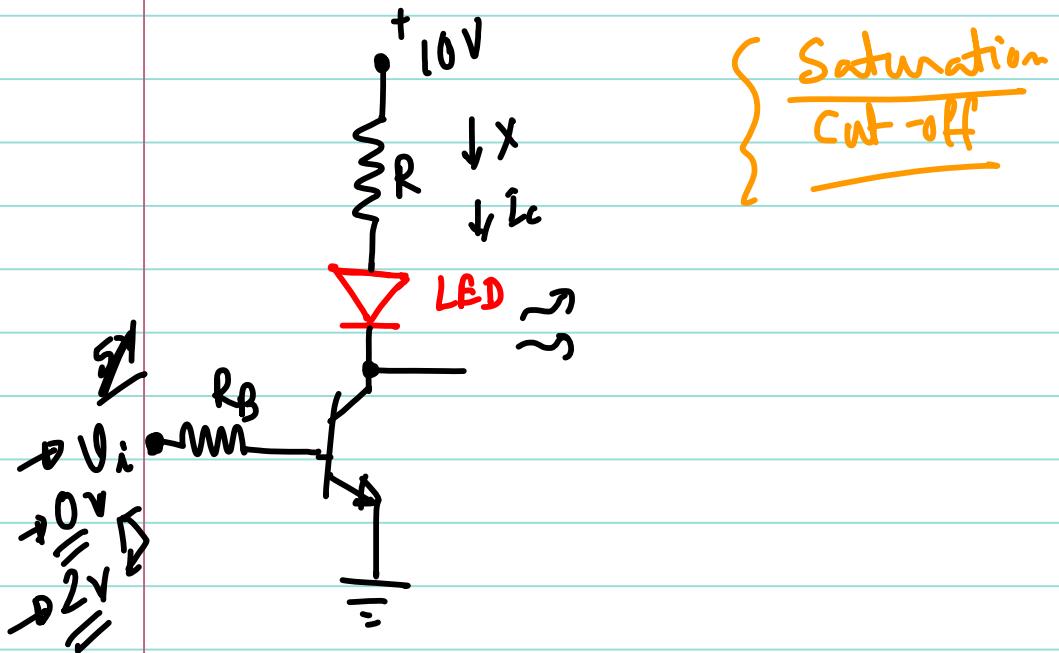

BJT as digital logic:

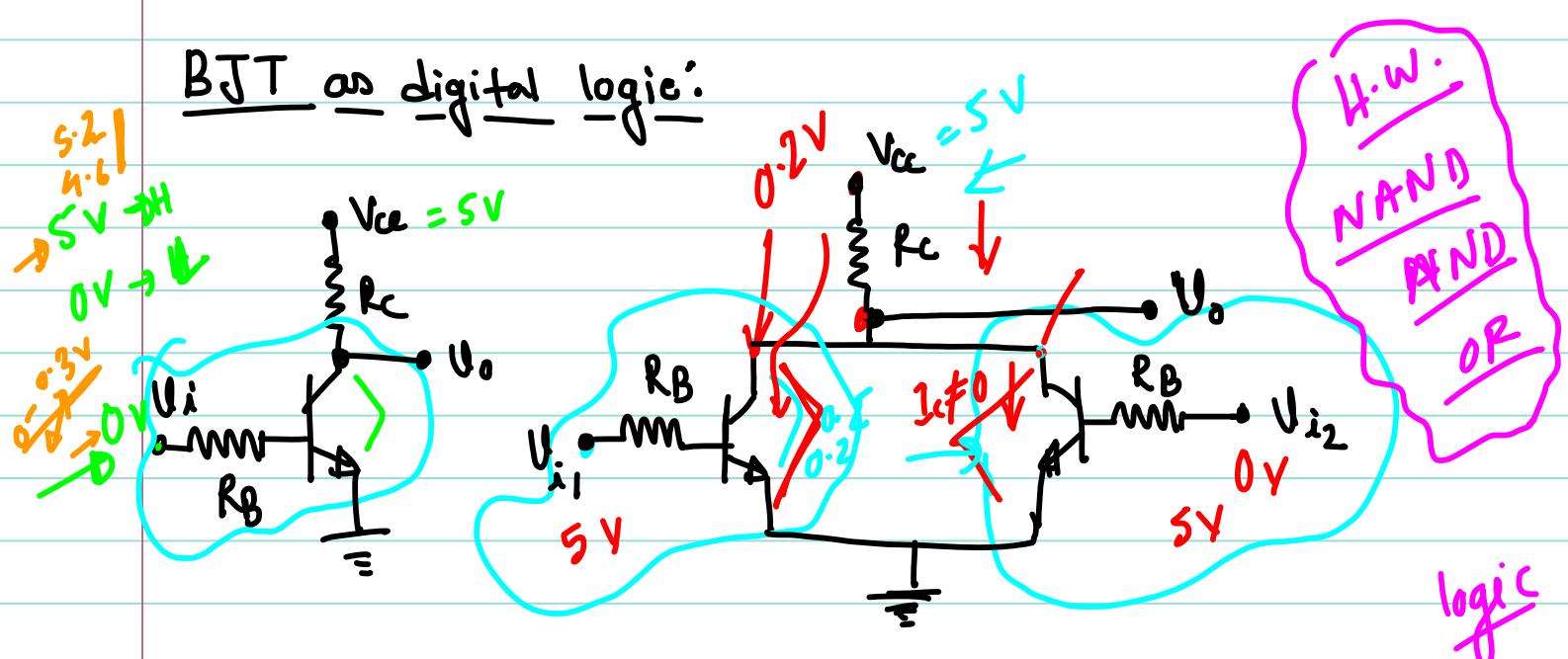

<u>Input</u>	<u>Output</u>
0V (0)	5V (1)
5V (1)	0.2V (0)

↓



NOT / Inverter

<u>Inputs</u>	<u>Output</u>
V_{i_1}	V_{i_2}
0V (0)	0V (0) \rightarrow 5V (1)
5V (1)	0V (0) \rightarrow 0.2V (0)
0V (0)	5V (1) \rightarrow 0.2V (0)
5V (1)	5V (1) \rightarrow 0.2V (0)


NOR



BJT as amplifier:

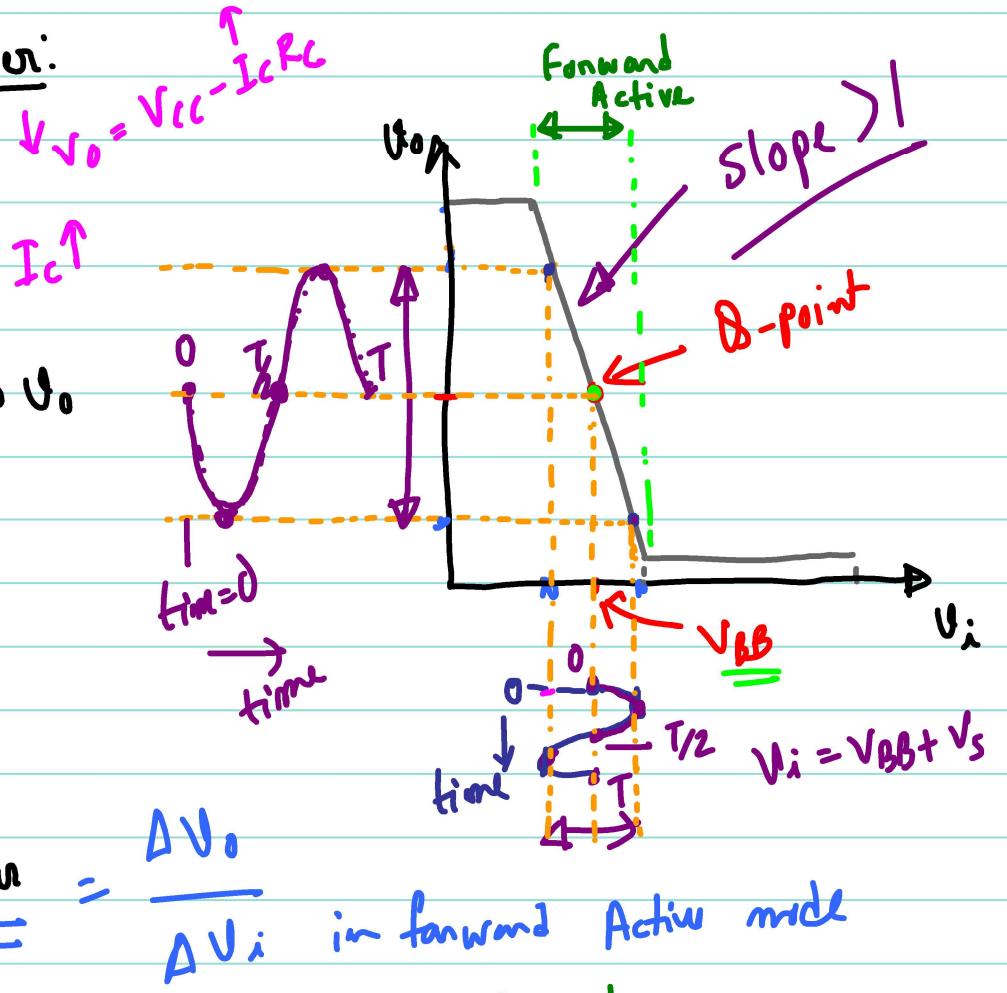
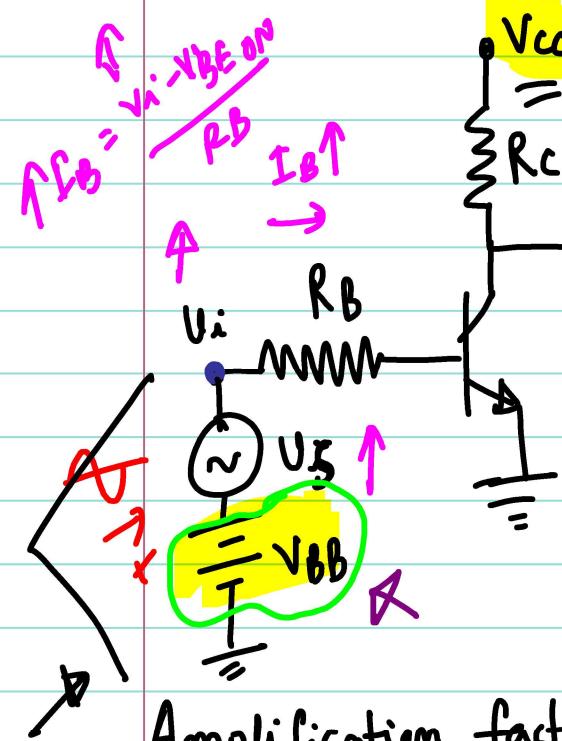


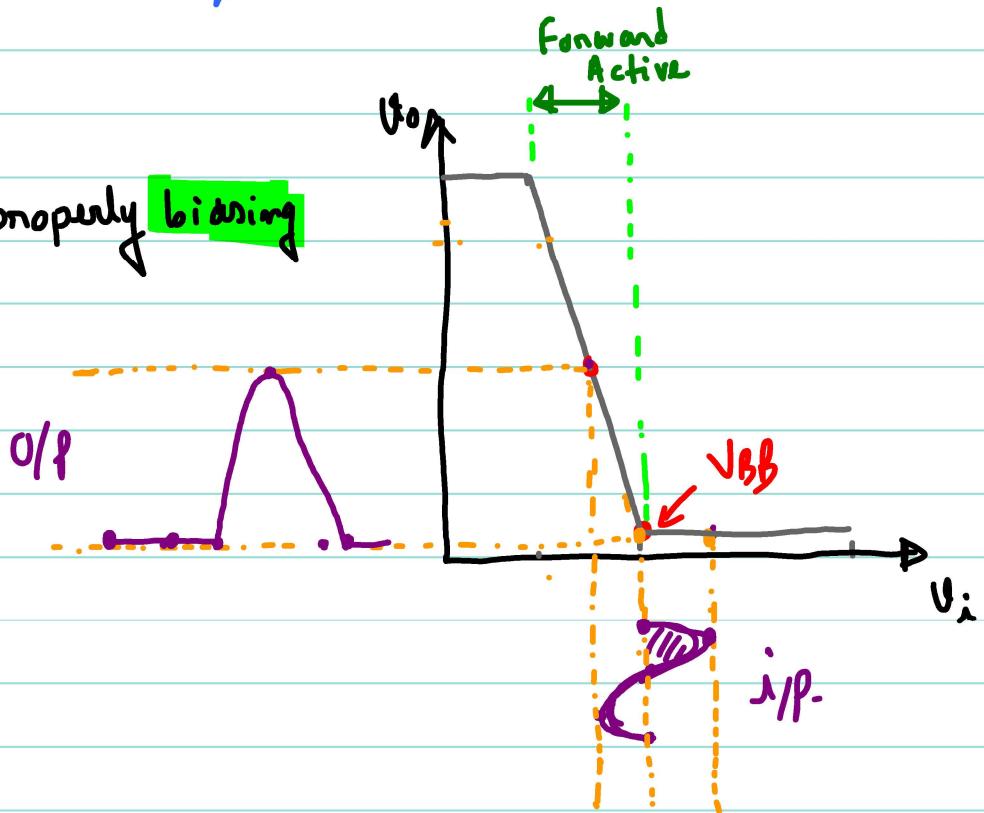→ Importance of properly biasing a transistor



Biasing of BJT:

(I) Biasing using a single resistor

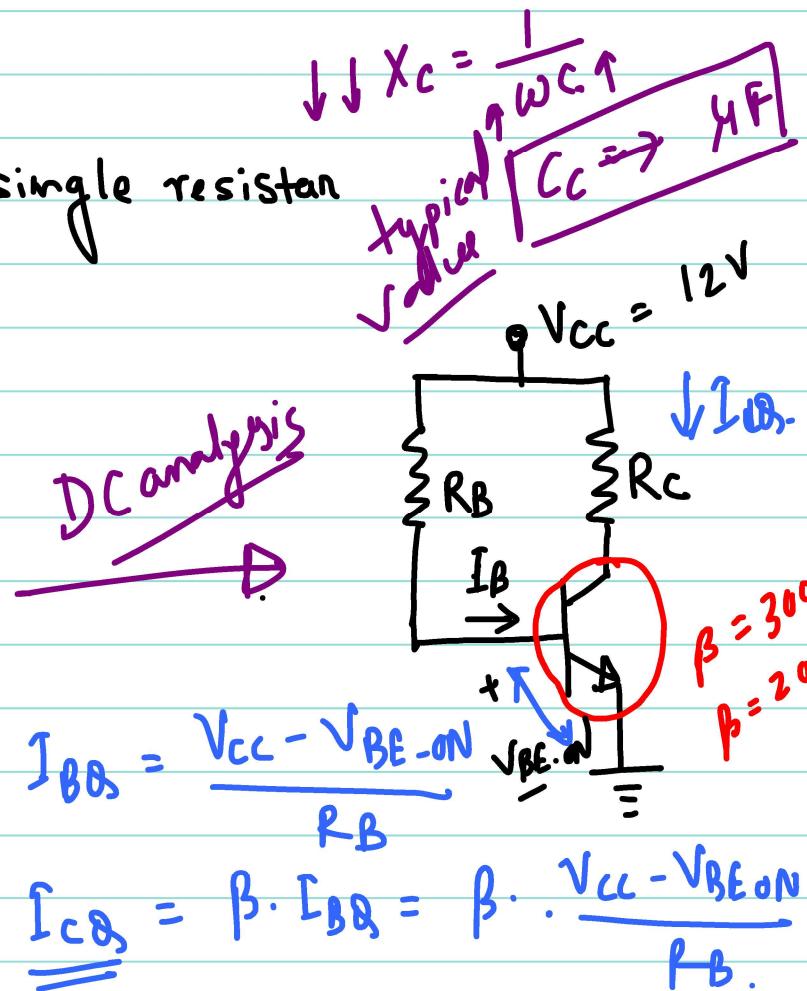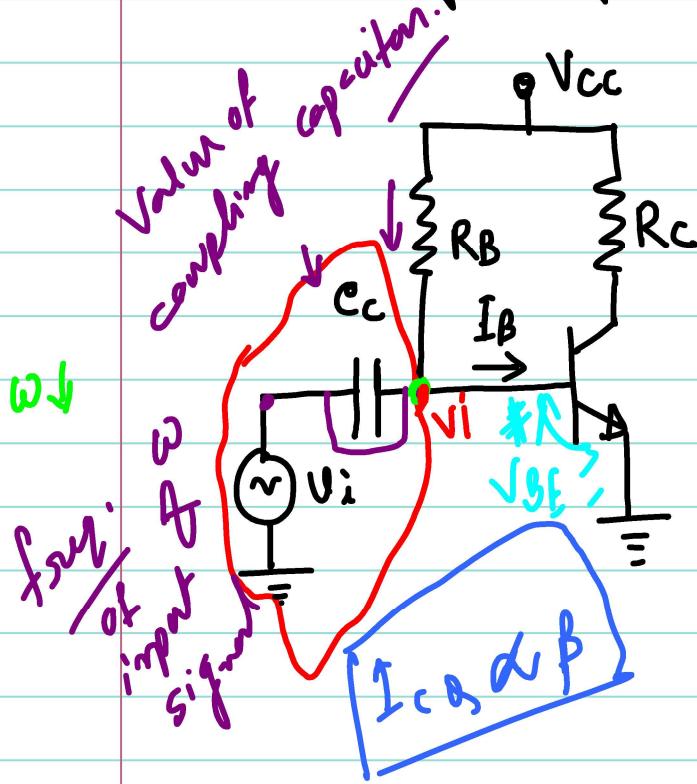


Value of \$R_B\$: typical value of \$I_B \rightarrow MA\$ (\$10 \mu A\$)


Required: $R_B = \frac{V_{CC} - V_{BE-ON}}{I_B} = 113 \times 10^4 \Omega$

Very high value difficult to implement in \$I_C\$

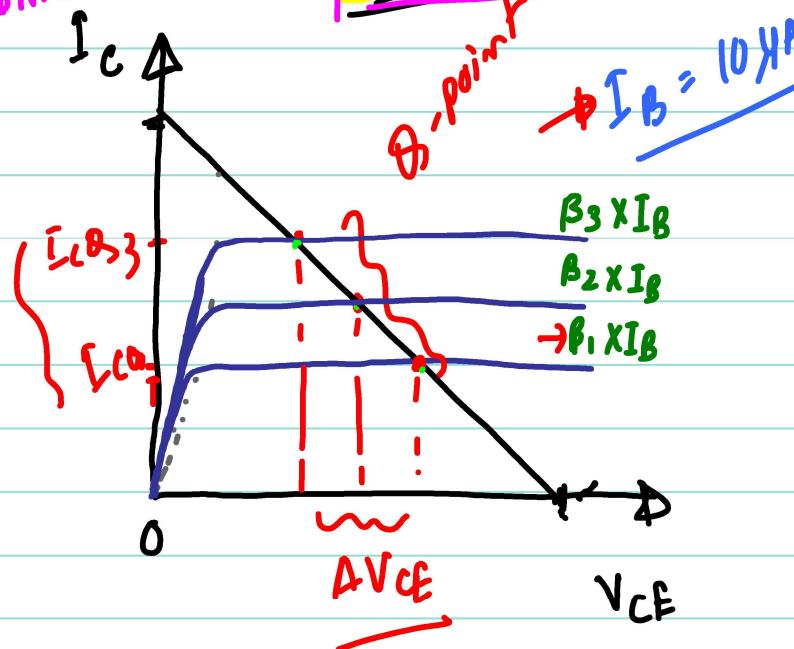Stability of Q-point:
due to change in '\$\beta\$'



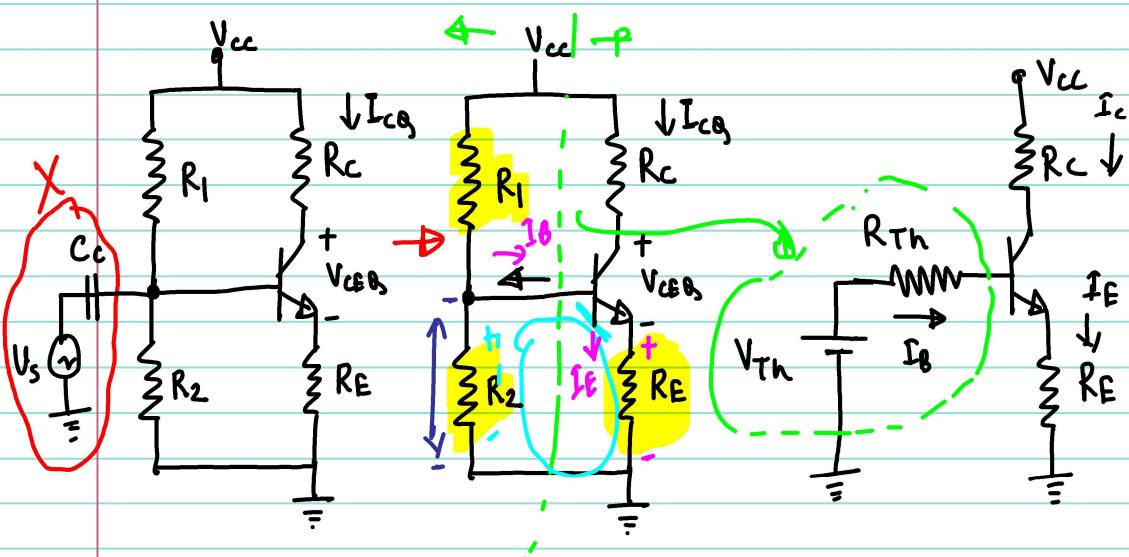(ii) Voltage divider biasing with emitter resistor:



$$V_{Th} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} ; \quad R_{Th} = R_1 \parallel R_2$$

$$V_{Th} = I_B \cdot R_{Th} + V_{BEON} + I_E R_E ; \quad I_E = (1+\beta) I_B$$

$$\begin{aligned} V_{Th} &= I_B \cdot R_{Th} + V_{BEON} + (1+\beta) I_B R_E \\ I_B &= \frac{V_{Th} - V_{BEON}}{R_{Th} + (1+\beta) R_E} ; \quad I_C = \beta I_B \\ I_C &= \beta \times \frac{V_{Th} - V_{BEON}}{R_{Th} + (1+\beta) R_E} \end{aligned}$$

$$R_{Th} \ll (1+\beta) R_E$$

$$I_C \approx \frac{\beta (V_{Th} - V_{BEON})}{(1+\beta) R_E} ; \quad \frac{\beta \gg 1}{1+\beta \approx \beta}$$

$$I_C \approx \frac{V_{Th} - V_{BEON}}{R_E} ; \quad I_C \text{ is independent of } \beta$$